

# VE215 Mid RC Part 2

Gong Yuhan

UM-SJTU JI

# Overview

Linearity Property

Superposition

Source Transformation

Thevenin's Theorem

Norton's Theorem

Maximum Power Transfer

# Linearity Property

homogeneous: if  $x \rightarrow y$ , then  $kx \rightarrow ky$

additive: if  $x_1 \rightarrow y_1$  and  $x_2 \rightarrow y_2$ , then  $x_1 + x_2 \rightarrow y_1 + y_2$

linear circuit: homogeneous and additive

## Exercise

Assume  $I_s = 1$  A and use linearity to find the actual value of  $I_o$  in the circuit of Fig. 4.4.


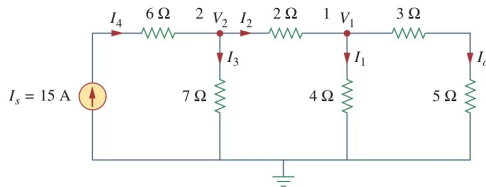


Figure 4.4

## Exercise

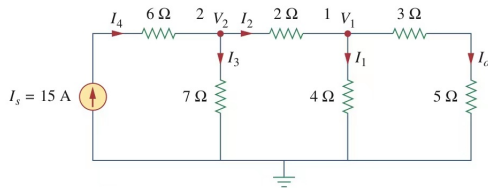

**Answer:**  $I_o = 3\text{ A}$

# Overview

Linearity Property

Superposition

Source Transformation

Thevenin's Theorem

Norton's Theorem

Maximum Power Transfer


# Superposition

## Steps




1. Only consider one **independent** source.
  - ▶ voltage source: short circuit
  - ▶ current source: open circuit
2. Use additivity.

## Exercise

Find  $i$  in the circuit.

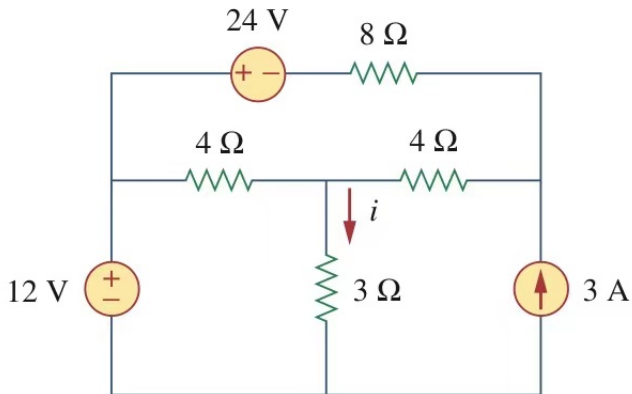

# Exercise

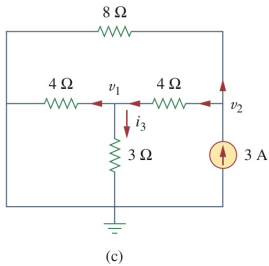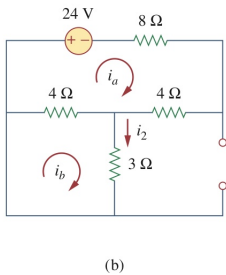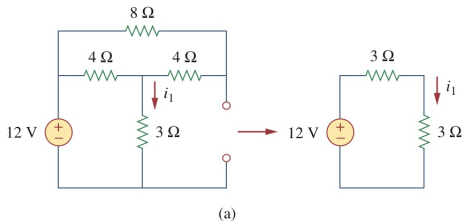

**Answer: 2A**



# Overview

Linearity Property

Superposition

Source Transformation

Thevenin's Theorem


Norton's Theorem

Maximum Power Transfer
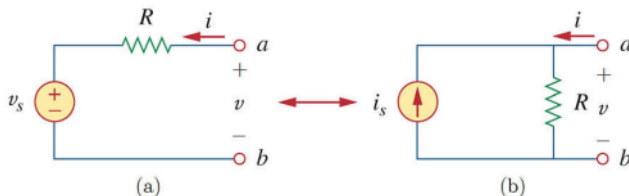
# Source Transformation

We can replace a voltage source with a resistance with a corresponding current source with the same resistance to simplify the circuit.


In the case shown below,  $v_s = i_s \times R$



For dependent sources, the source transformation is also valid.


## Exercise

Find  $i$ .

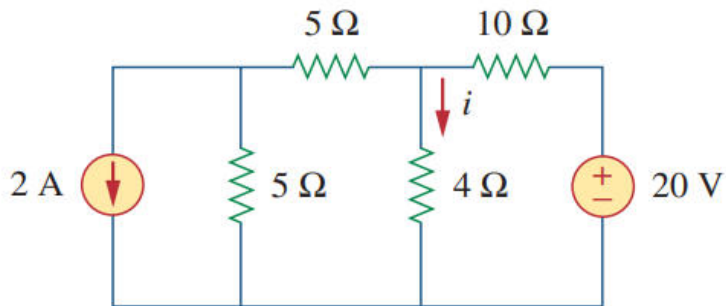

## Exercise

Find  $i$ .

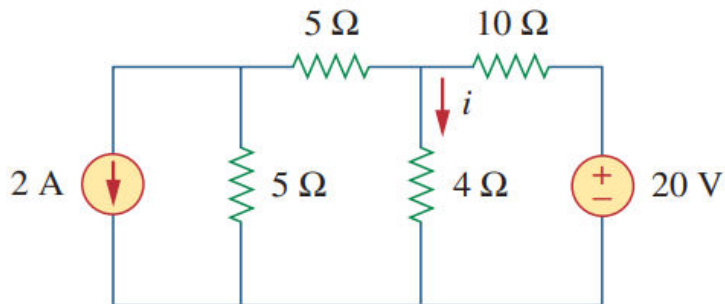

**Answer:**  $5/9\text{ A}$

# Overview

Linearity Property

Superposition

Source Transformation


Thevenin's Theorem

Norton's Theorem

Maximum Power Transfer
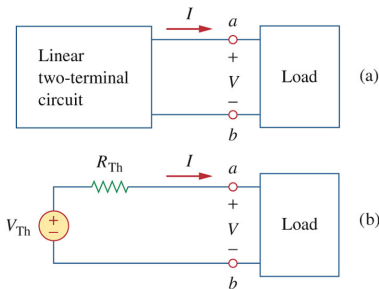
# Thevenin's Theorem


A linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source  $V_{Th}$  in series with a resistor  $R_{Th}$ .



- ▶  $V_{Th}$ : the open-circuit voltage at the terminals.
- ▶  $R_{Th}$ : the equivalent resistance at the terminals when all the **independent sources** are turned off.

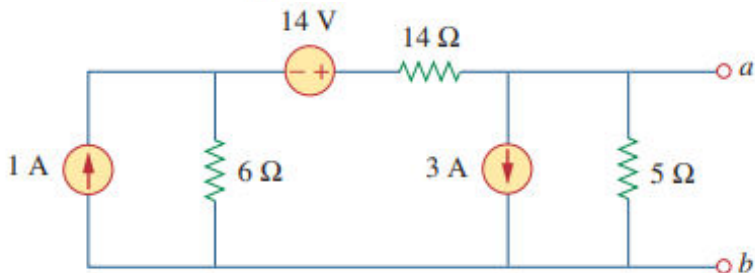
## Exercise

Obtain the Thevenin equivalent circuit of this circuit with respect to terminal a and b.


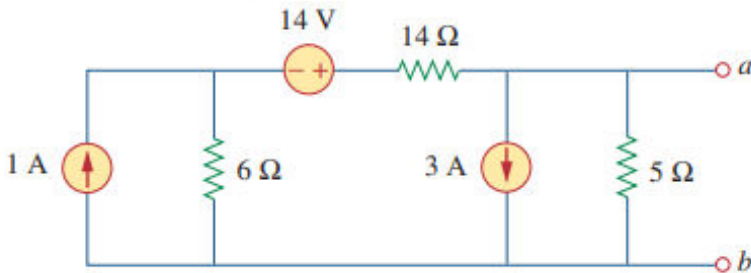
## Exercise

Obtain the Thevenin equivalent circuit of this circuit with respect to terminal a and b.



**Answer:**  $V_{Th} = -8\text{ V}$

$R_{Th} = 4\Omega$

pay attention to the sign of the voltage !



# Overview

Linearity Property

Superposition

Source Transformation


Thevenin's Theorem

**Norton's Theorem**

Maximum Power Transfer
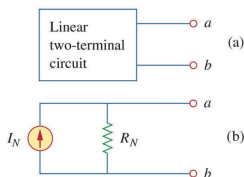
# Norton's Theorem


A linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source  $I_{Th}$  in parallel with a resistor  $R_{Th}$ .



- ▶  $I_{Th}$ : the short-circuit current at the terminals.
- ▶  $R_{Th}$ : the equivalent resistance at the terminals when all the **independent sources** are turned off.

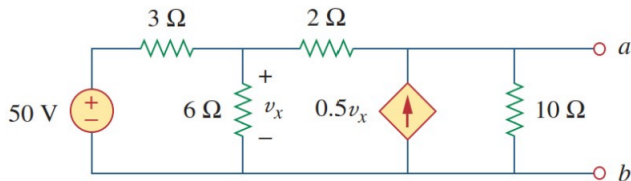
## Exercise

Obtain the Norton equivalent circuit of this circuit with respect to terminal a and b.


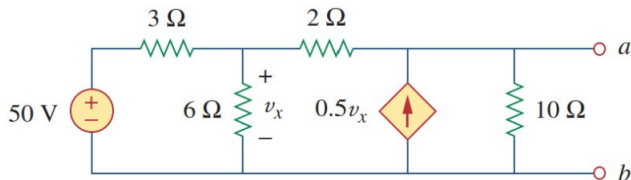
## Exercise

Obtain the Norton equivalent circuit of this circuit with respect to terminal a and b.



**Answer:**  $I_N = 16.67\text{ A}$   
 $R_N = 10\Omega$

# Overview

Linearity Property

Superposition

Source Transformation

Thevenin's Theorem

Norton's Theorem

Maximum Power Transfer


# Maximum Power Transfer

A circuit is usually designed to provide power to a load. For different kinds of circuits, we have different concerns

- ▶ **Maximum Power Efficiency:** In power utility systems, the amount of electricity is very large. Therefore, how to **increase the efficiency of power transfer** becomes an important problem.
- ▶ **Maximum Power Transfer:** In communication and instrumental systems, the amount of electricity is small so the problem of efficiency is not so important. Instead, we want to **transfer as much of power as possible to the load**.
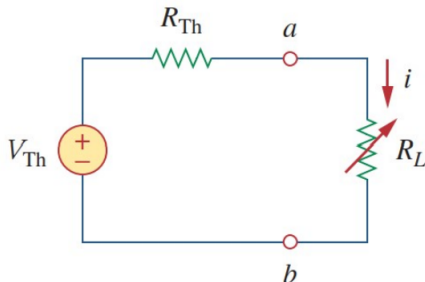
# Maximum Power Transfer

The Thevenin's equivalent circuit is useful in finding the maximum power delivered to a load. In the circuit below,  $R_L$  represents the load.



# Maximum Power Theorem

Since

$$p = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

Let  $\frac{dP}{dR_L} = V_{Th}^2 \frac{R_{Th} - R_L}{(R_{Th} + R_L)^3} = 0$ , we have  $R_L = R_{Th}$ .

And when  $R_L = R_{Th}$ ,  $\frac{d^2P}{dR_L^2} = V_{Th}^2 \frac{2R_L - 4R_{Th}}{(R_{Th} + R_L)^4} = -\frac{V_{Th}^2}{8R_{Th}^2} < 0$ .

Thus  $p$  reaches maximum at  $R_L = R_{Th}$ .  $p_{max} = \frac{V_{Th}^2}{4R_{Th}}$



# References

1. 2024 Fall VE215 slides
2. Fundamentals of Electric Circuits, 5th e, Sadiku, Matthew
3. 2023 Fall RC2 Chongye Yang

Thank you!