

ECE2150J RC3

Jierui Xu

UM-SJTU JI

October 30, 2024

Overview

Operational Amplifiers

Capacitors and Inductors

First-Order Circuit

Overview

Operational Amplifiers

Capacitors and Inductors

First-Order Circuit

Ideal Op-amp

Assumption:

- ▶ Infinite open-loop gain ($A = \infty$)
- ▶ Infinite input resistance ($R_i = \infty$)
- ▶ Zero output resistance ($R_o = 0$)
- ▶ (Does not mean that $v_o = \infty$)

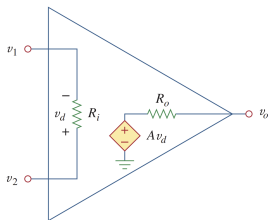


Figure: Op-amp's equivalent circuit

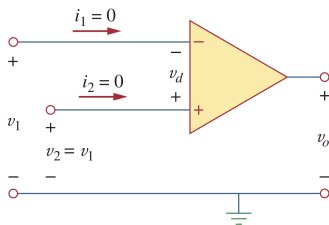


Figure: Symbol of ideal op-amp

Ideal Op-amp

Characteristics of ideal op-amp:

- ▶ Open circuit at two input terminals ($i_1 = i_2 = 0$)
- ▶ Same voltage at two input terminals ($v_1 = v_2$)
- ▶ **(Does not mean that $i_o = 0$!)**

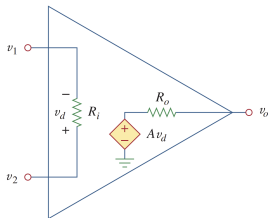


Figure: Op-amp's equivalent circuit


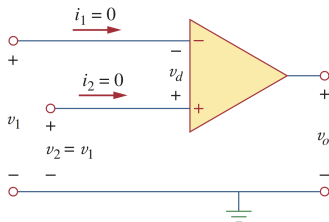



Figure: Symbol of ideal op-amp

Inverting Amplifier

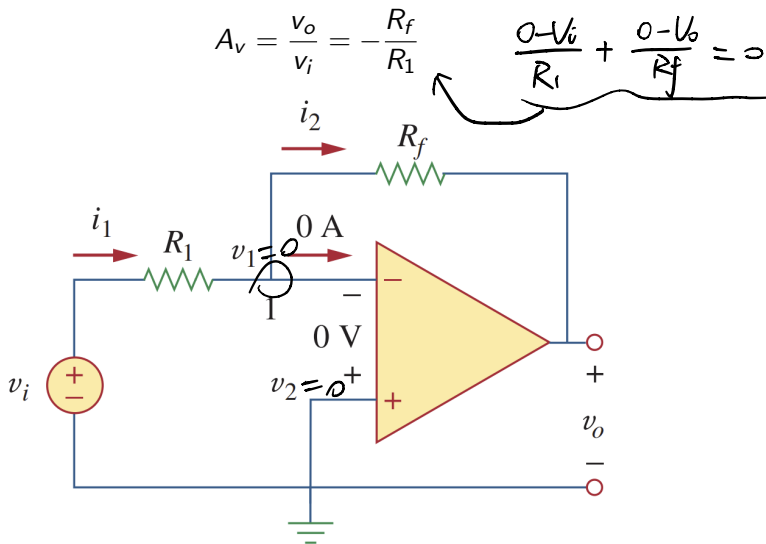


Non-inverting Amplifier
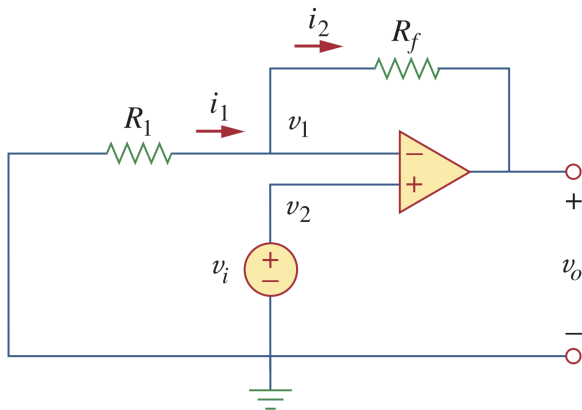
$$A_v = \frac{v_o}{v_i} = 1 + \frac{R_f}{R_1}$$



Summing Amplifier

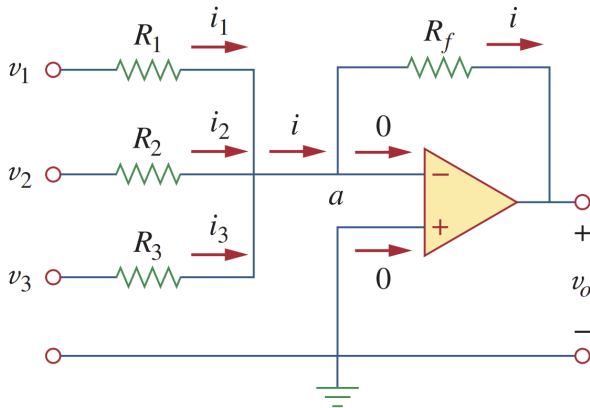
$$v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$



Difference Amplifier


Check if $R_1 = R_2$, $R_3 = R_4$
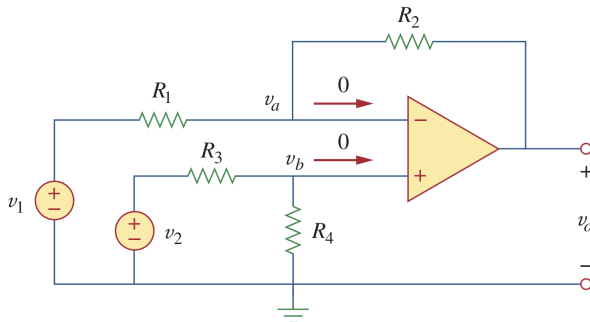
$$v_o = \left(\frac{R_2}{R_1} + 1 \right) \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} v_1$$



Cascaded Op Amps

Gain of Cascaded Op Amp

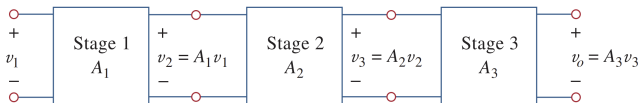

Original input signal is increased by the gain of the individual stage, and the final gain is the **product of all gains at each stage**.

$$A = \frac{v_o}{v_1} = \frac{v_2}{v_1} \cdot \frac{v_3}{v_2} \cdot \frac{v_o}{v_3} = A_1 A_2 A_3$$

Basic Op-amp Circuits: Summary

For basic op-amp circuits:


Op-amp circuits	Input-output relationship
Inverting amplifier	$A = \frac{v_o}{v_i} = -\frac{R_f}{R_1}$
Non-inverting amplifier	$A = \frac{v_o}{v_i} = 1 + \frac{R_f}{R_1}$
Summing amplifier	$v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3\right)$
Difference amplifier	$v_o = \left[\left(\frac{R_2}{R_1} + 1\right)\left(\frac{R_4/R_3}{1+R_4/R_3}\right)\right]v_2 - \left[\frac{R_2}{R_1}\right]v_1$

For complicated op-amp circuits:

- ▶ Identify basic op-amp circuits within it
- ▶ Use the formula for cascaded op-amp circuit
- ▶ Be proficient in listing nodal analysis equations to obtain v_o/v_i

Exercise 1


Find v_o .

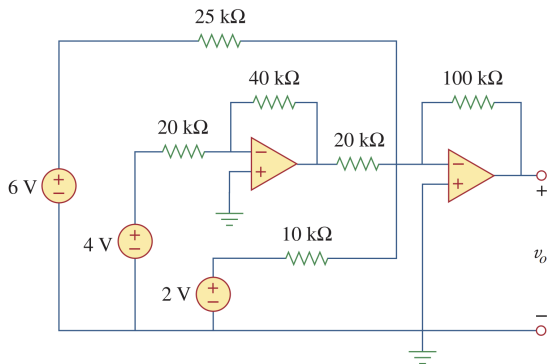

$$V_o = -\frac{100}{25} \cdot 6 - \frac{100}{20} \cdot \left(-\frac{40}{20}\right) \cdot 4 - \frac{100}{10} \cdot 2 = -24 - 20 + 40 = -4V$$

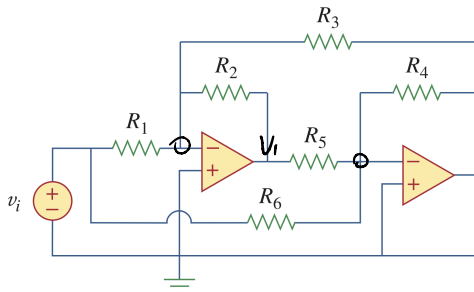Exercise 2

Determine the gain v_o/v_i of the circuit.



$$V_o = \frac{R_4}{R_5} \cdot \frac{R_2}{R_1} \cdot V_i + \frac{R_4}{R_5} \cdot \frac{R_2}{R_3} \cdot V_o - \frac{R_4}{R_6} V_i$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{\frac{R_4 R_2}{R_5 R_1} - \frac{R_4}{R_6}}{1 - \frac{R_2 R_4}{R_3 R_5}}$$

$$\frac{0-V_1}{R_2} + \frac{0-V_o}{R_3} + \frac{0-V_i}{R_1} = 0$$

$$V_1 = -\frac{R_2}{R_1} V_i - \frac{R_2}{R_3} V_o$$

$$\frac{0-V_1}{R_5} + \frac{0-V_i}{R_6} + \frac{0-V_o}{R_4} = 0$$

$$V_o = -\frac{R_4}{R_5} V_1 - \frac{R_4}{R_6} V_i$$

Overview



Operational Amplifiers

Capacitors and Inductors

First-Order Circuit

Capacitors

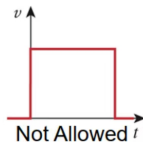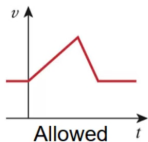1. **Open Circuit Property** When the voltage across a capacitor is not changing with time (**DC steady state**), the capacitor could be treated as an open circuit.
2. **Continuity property** The voltage on a capacitor must be continuous.




3. Capacitors IV relationship

$$i = C \frac{dv}{dt}$$

property 2 can be intuitively shown by property 3. If the voltage across the capacitor is not continuous, say $\frac{dv}{dt} = \infty$, which will cause i to be infinity.


Capacitors

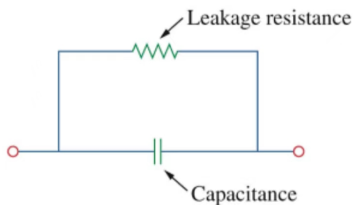1. **An ideal capacitor will not dissipate energy.** It takes power from the circuit when storing energy in its electric field and returns previously stored energy when delivering power to the circuit.
2. **A real capacitor has a large leakage resistance**



Capacitors in parallel & in series


► capacitors in parallel

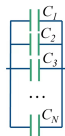

$$G(S) = \frac{1}{R}$$

$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

► capacitors in series

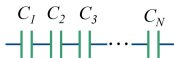

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4} + \dots + \frac{1}{C_N}$$

Energy stored in Capacitors

The instantaneous power delivered to the capacitor is

$$p = vi = v(C \frac{dv}{dt})$$

Therefore, **the total energy** stored in the capacitor is

$$w = \frac{1}{2} CV^2$$

$$\begin{aligned} W &= \int_{-\infty}^t p dt = \int_{-\infty}^t v (C \frac{dv}{dt}) dt = C \int_{v(-\infty)}^v v dv \\ &= \frac{1}{2} CV^2 \Big|_{\underbrace{v(-\infty)}_{=0}}^v = \frac{1}{2} CV^2 \end{aligned}$$


Inductors

1. **Short Circuit Property** When the current through an inductor is not changing with time (**DC steady state**), **the inductor could be treated as a short circuit in the circuit.**
2. **Continuity property** The current through a capacitor must be continuous.
3. **Inductor IV relationship**

$$v = L \frac{di}{dt}$$


Inductors

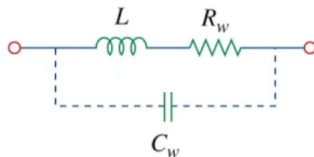1. **An ideal inductor will not dissipate energy.** It takes power from the circuit when storing energy in its magnetic field and returns previously stored energy when delivering power to the circuit.
2. **A real inductor has a significant winding resistance and a small winding capacitance**




Inductors in parallel & in series

► inductors in parallel

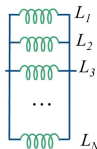

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4} + \dots + \frac{1}{L_N}$$

► inductors in series

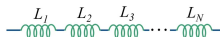

$$L_{eq} = L_1 + L_2 + L_3 + L_4 + \dots + L_N$$

Energy stored in Inductors

The instantaneous power delivered to the inductor is

$$p = vi = (L \frac{di}{dt})i$$

Therefore, **the total energy** stored in the inductor is

$$w = \frac{1}{2}Li^2$$


Summary of Capacitors and Inductors

	Capacitor	Inductor
Electric/magnetic	q	ψ
	$q=Cv$	$\psi=Li$
i-v (or v-i) relation	$i=C \times dv/dt$	$v=L \times di/dt$
energy	$1/2Cv^2$	$1/2Li^2$

Exercise 3



Y-Δ

Obtain the equivalent capacitance of the network below.

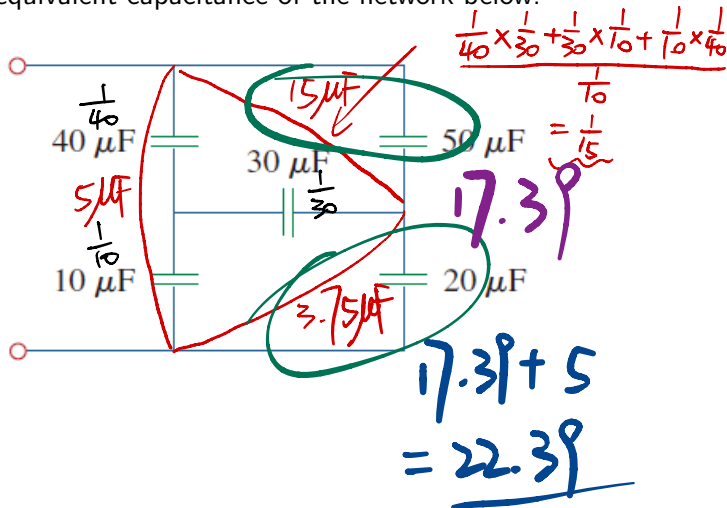

Exercise 4




The output v_o of the op amp circuit in Fig.(a) is shown in Fig.(b). Let $R_i = R_f = 1\text{ M}\Omega$ and $C = 1\text{ }\mu\text{F}$. Determine the input voltage waveform and sketch it.

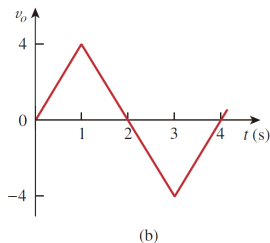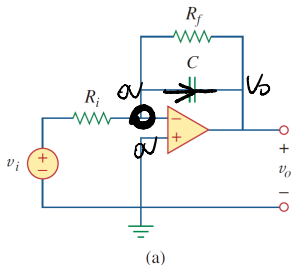

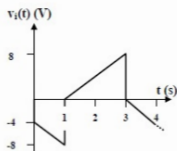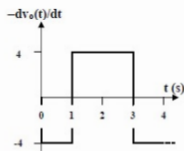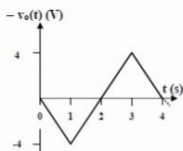Exercise 4

$$\frac{0-V_i}{R_i} + \frac{0-V_o}{R_f} + C \frac{d}{dt}(0-V_o) = 0$$

$$\Rightarrow V_i = -\left(V_o + \frac{dV_o}{dt}\right)$$



Overview


Operational Amplifiers

Capacitors and Inductors

First-Order Circuit

Source-Free Circuits (I) Response

Source-free RC

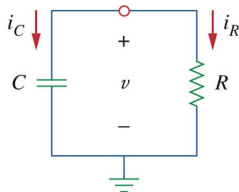

Voltage: $v = v_0 e^{-t/RC}$


Time constant: $\tau = RC$

Current: $i_R = \frac{v}{R} = \frac{v_0}{R} e^{-t/\tau}$

Power: $p = v i_R = \frac{v_0^2}{R} e^{-2t/\tau}$

Energy: $w_R = \int_0^t p dt = \frac{1}{2} C v_0^2$

Source-free RL

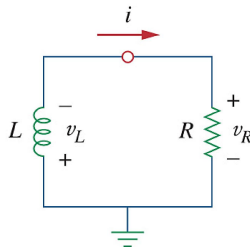

Current: $i = i_0 e^{-t/(L/R)}$


Time constant: $\tau = L/R$

Voltage: $v_R = iR = \frac{i_0 R}{R} e^{-t/\tau}$

Power: $p = v_R i = i_0^2 R e^{-2t/\tau}$

Energy: $w_R = \int_0^t p dt = \frac{1}{2} L i_0^2$

Source-Free Circuits (II) Time Constant

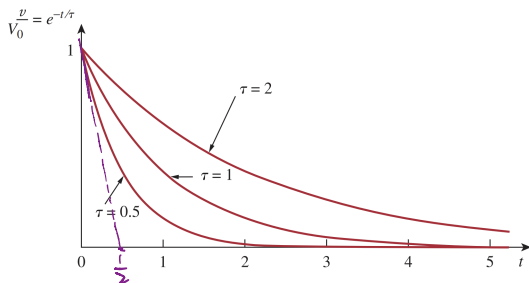




	Source-free RC	Source-free RL
Time constant	$\tau = RC$	$\tau = L/R$
Relation to initial decay rate	$\frac{d}{dt}\left(\frac{v}{v_0}\right) = -1/\tau$	$\frac{d}{dt}\left(\frac{i}{i_0}\right) = -1/\tau$

- ▶ Time required for the response to decay to a factor of $1/e$ or 36.8% of its initial value
- ▶ Indicates the initial decaying rate
- ▶ Assume complete decay after 5τ

Source-Free Circuits (III) General Steps

- ▶ Find the initial value v_0 , i_0 .
- ▶ Find the time constant, i.e., find R_{eq} . (R_{eq} is the Thevenin or Norton equivalent resistance at the capacitor and inductor terminals.)
- ▶ Use the equation in the previous slide to get results.
- ▶ You can always use Mesh/Nodal analysis to calculate if you are not familiar with the steps above.
- ▶ (Of course, you need to remember that $i = C \frac{dv}{dt}$ for capacitors and $v = L \frac{di}{dt}$ for inductors!)

Singularity Functions

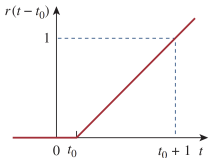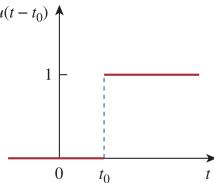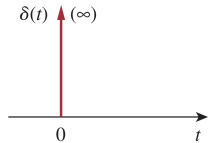Unit ramp	Unit step	Unit impulse
$r(t) = \begin{cases} 0, & t \leq 0 \\ t, & t > 0 \end{cases}$	$u(t) = \begin{cases} 0, & t \leq 0 \\ 1, & t > 0 \end{cases}$	$\delta(t) = \begin{cases} 0, & t \neq 0 \\ \text{Undef.}, & t = 0 \end{cases}$
		

Give a nice way to represent “Switch on/off” of the sources/part of circuits.

$$\delta(t) \xrightarrow{f} u(t) \xrightarrow{f} r(t)$$


Exercise 5

Please plot the function diagram of the following singular function

$$f(t) = r(t + 1) + u(t - 2) - r(t - 3)$$


and calculate
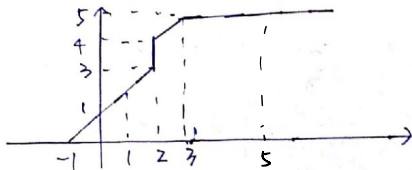
$$\int_{-\infty}^{+\infty} f'(t) \delta(t - 5) dt \\ = f'(5) = 0$$



Circuits with Step Input (I) Response

Step-input RC

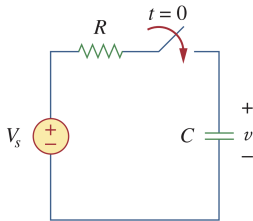


Initial condition:
 $v(0^+) = v(0^-) = V_0$

Equation:
(KVL) $(C \frac{dv}{dt} R + v = V_s)$

Response:
 $v(t) = V_s + (V_0 - V_s)e^{-t/\tau}$

Step-input RL

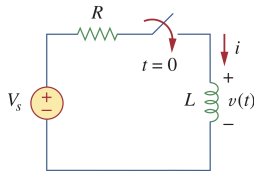

Initial condition:
 $i(0^+) = i(0^-) = I_0$

Equation:
(KCL) $iR + L \frac{di}{dt} = V_s$

Response:
 $i(t) = \frac{V_s}{R} + (I_0 - \frac{V_s}{R})e^{-t/\tau}$

Circuits with Step Input (II) General Steps

- ▶ General form: $x(t) = x(\infty) + (x(0) - x(\infty))e^{-t/\tau}$.
- ▶ Step response = natural response + forced response, where natural response is $x(0)e^{-t/\tau}$, forced response is $x(\infty)(1 - e^{-t/\tau})$.
- ▶ Step response = transient state response + steady state response, where transient response is $(x(0) - x(\infty))e^{-t/\tau}$, steady state response is $x(\infty)$.
- ▶ Steps to find step response:
 - ▶ Find $x(0)$.
 - ▶ Find $x(\infty)$.
 - ▶ Find τ .
- ▶ Still, you can find step response using mesh/nodal analysis. By solving the differential equation, you will find that natural response is the homogeneous solution of the equation, while the forced response is the particular solution.

General Formula for First-Order Circuits

General formula for RC:


$$v(t) = v(\infty) + [v(0^+) - v(\infty)] e^{-t/\tau}$$

General formula for RL:

$$i(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-t/\tau}$$

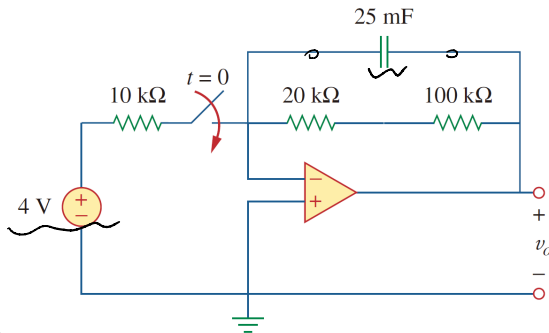Exercise 6

For the op amp circuit below, find $v_o(t)$ for $t > 0$.



① For $t < 0$, $v_o(0) = 0$

②. For $t > 0$, $v_o(\infty) = -\frac{20+100}{10} \cdot 4 = -48$

Exercise 6

$$\textcircled{3}. R_{Th} = 20 + 100 = 120 \text{ k}\Omega$$

$$\tau = R_{Th}C = (120 \times 10^3) \cdot (25 \times 10^{-3}) = 3000$$

$$\Rightarrow V_o(t) = V_o(\infty) + [V_o(0) - V_o(\infty)] \cdot e^{-t/\tau}$$

$$V_o(t) = -48(1 - e^{-t/3000}) \text{ V}$$

References

1. 2024 Fall VE215 slides, Sung-Liang Chen
2. Fundamentals of Electric Circuits, 5th e, Sadiku, Matthew
3. 2023 Summer RC3, Erdao Liang, Chongye Yang
4. 2024 Summer RC3, Runting Zhang

Thank you!