

Due Date: 23:59, Nov.18th, 2024

In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated. This assignment covers content from chapter 6 to 8.


### Exercise 3.1 (20%)

The three inductors in the circuit are connected across the terminals of a black box at  $t = 0$ . The resulting voltage for  $t > 0$  is known to be

$$v_o = 2000e^{-100t} \text{ V.}$$


If  $i_1(0) = -6 \text{ A}$  and  $i_2(0) = 1 \text{ A}$ , find

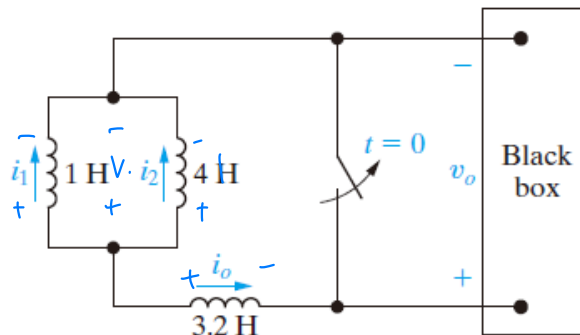- $i_o(0)$ ;
- $i_o(t)$ ,  $t \geq 0$ ; (Hint: Calculate the equivalent inductance  $L_{eq}$  first.)
- $i_1(t)$ ,  $t \geq 0$ ;
- $i_2(t)$ ,  $t \geq 0$ ;
- the initial energy stored in the three inductors;



(a)  $i_o(0) = (i_1(0) + i_2(0)) = -6\text{A} - 1\text{A} = -5\text{A}$

(b)  $t \geq 0$

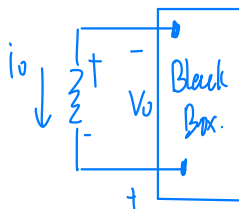

$$L_{eq} = 1/4 + 3.2 = 4 \text{ H}$$

$$V_o = -V_L = -L \frac{di_o}{dt}$$

$$di_o = -\frac{1}{L} V_o dt$$

$$i_o = -\frac{1}{4} \int 2000e^{-100t} dt = 5 \int e^{-100t} d(-100t)$$

$$= 5 e^{-100t} + C$$

$$i_o(0) = 5 \quad C=0$$

$$i_o = 5e^{-100t}$$

when  $t > 0$

(c)  $V = L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt}$

$$V - V_o - V_H = 0$$

$$V_H = L_H \cdot \frac{di_o}{dt}$$

$$= 3.2 (-500) e^{-100t}$$

$$= -1600 e^{-100t}$$

$$V = 400 e^{-100t}$$

$$i_1 = 100 \int e^{-100t} dt + C$$

$$= -4 e^{-100t} + C$$

$$i_1(0) = -4 + C = -6$$

$$i_1 = -4e^{-100t} - 2$$

(d)  $i_2 = 100 \int e^{-100t} dt + C = -e^{-100t} + C$

$$i_2(0) = -1 + C = 1$$


$$i_2(t) = -e^{-100t} + 2$$

(e)  $W = \frac{1}{2} L i^2 = \frac{1}{2} (1 + 6^2 + \frac{1}{2} 4 \cdot 1^2 + \frac{1}{2} \cdot 1 \cdot 5^2) = 60 \text{ J}$
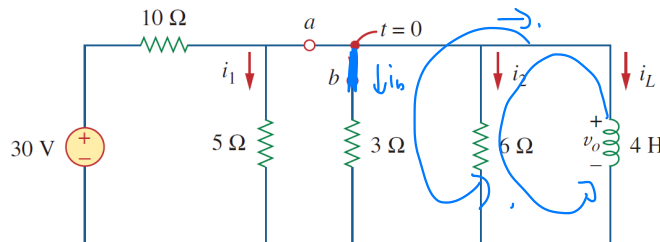
## Exercise 3.2 (20%)

In the circuit below, assume that the switch has been in position  $a$  for a long time, find:

- $i_1(0)$ ,  $i_2(0)$ , and  $v_o(0)$
- $i_L(t)$
- $i_1(\infty)$ ,  $i_2(\infty)$ , and  $v_o(\infty)$



(a)  $i_1(0) = i_2(0) = 0 \text{ A}$ ,  
 $v_o = L \cdot \frac{di}{dt} = 0 \text{ V}$ .

$i_L = e^{-\frac{1}{2}t + C}$   
 $e^C = 3$

(b)  $i_L(0) = \frac{30}{10} \text{ A} = 3 \text{ A}$ .

$i_L = 3 \cdot e^{-\frac{1}{2}t} (t \geq 0)$

$i_b + i_2 + i_L = 0$

$\frac{V}{3} + \frac{V}{6} + i_L = 0$

$\frac{4}{5} \cdot \frac{di}{dt} + \frac{2}{5} \frac{di}{dt} + i_L = 0$

$\frac{di_L}{dt} = -\frac{1}{2} i_L$

$\ln|i_L| = -\frac{1}{2}t + C$



(c)  $i_1(\infty) = \frac{30}{15} = 2 \text{ A}$ ,

$i_2(\infty) = 0 \text{ A}$

$v_o(\infty) = 0 \text{ V}$ .

## Exercise 3.3 (10+10%)

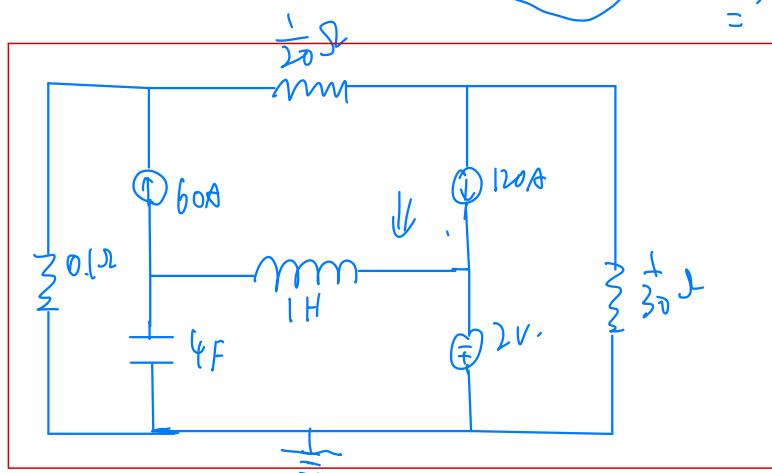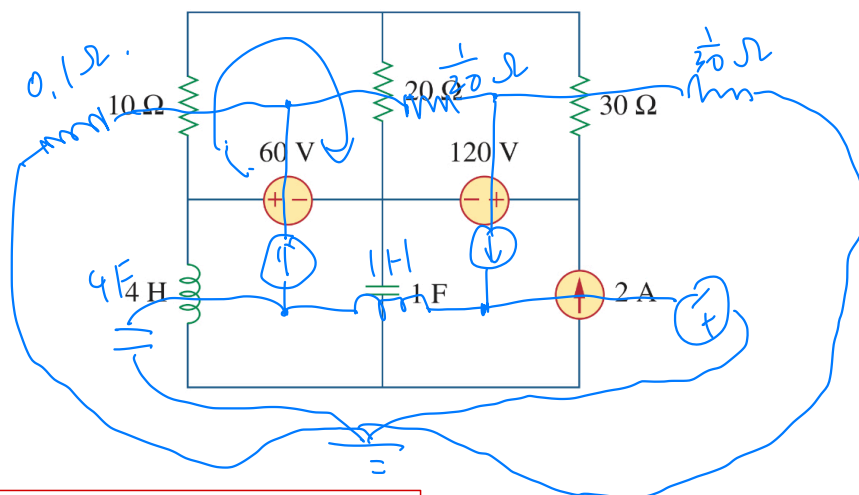(a) (10%) Find the dual of the circuit below.



# VE215 2024FA Assignment 3



JOINT INSTITUTE  
交大密西根学院

(b) (10%) For the network below, solve for  $i(t)$  for  $t > 0$ .


when  $t < 0$ .

$$\frac{45 - V_{co}}{6} + \frac{15 - V_{co}}{6} = 0.$$

$$V_{co} = 30V.$$

$$i_0 + \frac{15 - 30}{6} + \frac{15 - 45}{6} = 0.$$

$$i_0 = 7.5A.$$

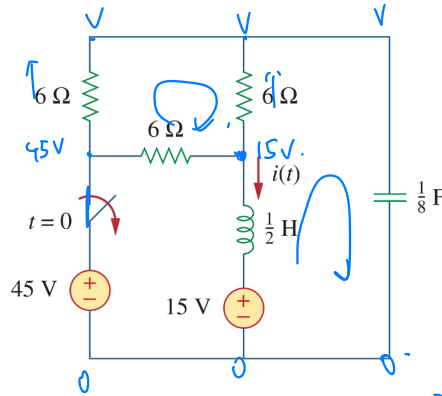

$$-15 + \frac{1}{2} i'_{10} - 30 + 30 = 0$$

$$i'_{10} = 30$$

$$i_c = 7.5e^{-4t}.$$


$$30e^{-4t} + C_1 e^{-4t} - 4C_1 t e^{-4t} = 30$$

$$C_1 e^{-4t} = 0$$

$$C_2 = 0.$$

$$i = -i_c = 7.5e^{-4t}.$$

when  $t > 0$ .

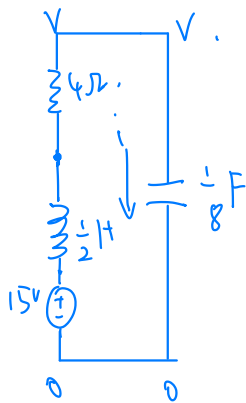

$$\begin{cases} i_c = \frac{1}{8} \frac{dv}{dt} \\ -15 + \frac{1}{2} \frac{di_c}{dt} + i_c 4 + V = 0. \end{cases}$$

$$\frac{di_c}{dt} + 8i_c + 16 \int i_c dt = 30.$$

$$\frac{d^2 i_c}{dt^2} + 8 \frac{di_c}{dt} + 16 i_c = 0.$$

$$i_c(t) = C_1 e^{-4t} + C_2 t e^{-4t}.$$


## Exercise 3.4 (20%)

In the op amp circuit of Fig. 3.5, determine  $v_o(t)$  for  $t > 0$ . Let  $v_i(t) = u(t)V$ ,  $R_1 = R_2 = 10k \text{ ohm}$ ,  $C_1 = C_2 = 100\mu F$ .

when  $t < 0$ .

$$V_o = 0.$$

when  $t > 0$ .

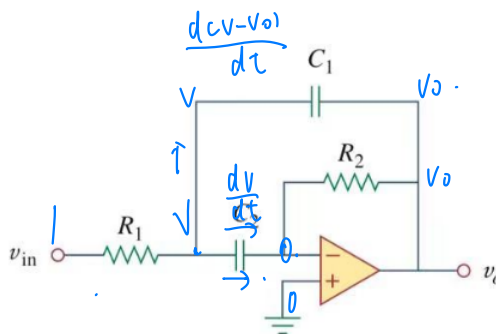

$$C_1 = 0.$$

$$-\frac{1}{R_1} - C_1 \frac{dv_o(t)}{dt} = 0.$$

$$\frac{dv_o(t)}{dt} = \frac{1}{C_1 R_1} = -1.$$

$$C_2 e^{-t} - C_2 t e^{-t} = -1.$$

$$\text{when } t \rightarrow 0.$$

$$C_2 = -1.$$

$$V_o = -te^{-t} \cdot (t > 0).$$

$$\begin{cases} \frac{V-1}{R_1} + C_1 \frac{dv}{dt} + C_2 \frac{d(v-v_o)}{dt} = 0. \\ C_1 \frac{dv}{dt} = -\frac{V_o}{R_2}. \end{cases}$$

$$V = \frac{1}{C_1 R_2} \int V_o dt.$$

$$-\frac{1}{C_2 R_1 R_2} \int V_o dt - \frac{1}{R_1} - \frac{2}{R_2} V_o - C_1 \frac{dV_o}{dt} = 0.$$

$$\frac{d^2 V_o}{dt^2} + \frac{2}{R_2 C_1} \frac{dV_o}{dt} + \frac{1}{C_1 C_2 R_1 R_2} V_o = 0$$

$$\frac{d^2 V_o}{dt^2} + 2 \frac{dV_o}{dt} + V_o = 0.$$

$$V_o = C_1 e^{-t} + C_2 t e^{-t}.$$


## Exercise 3.5 (20%)

The gap in the circuit seen in the figure below will arc over whenever the voltage across the gap reaches 30 kV. The initial current in the inductor is zero. The value of  $\beta$  is adjusted so the Thévenin equivalent resistance with respect to the terminals of the inductor is  $-4 \text{ k}\Omega$ . Now please answer the following two questions below.

(a) What is the value of  $\beta$ ?

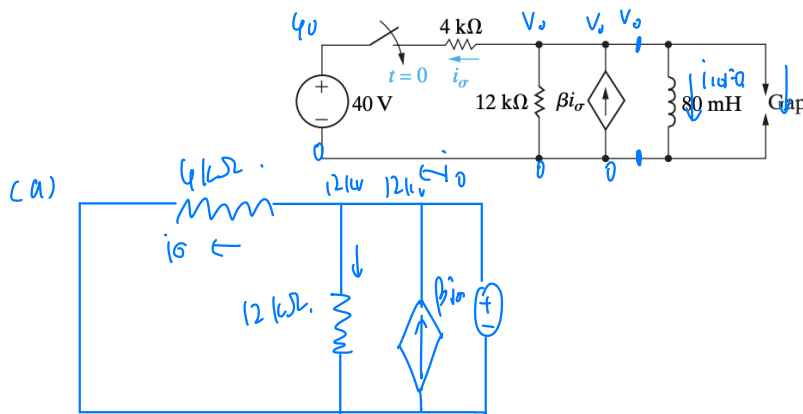(b) After the switch has been closed, how long will it take for the gap to arc over?

Tip: For this question, the gap can be treated as an open circuit before the voltage across it reaches 30 kV, and you do not need to know what "arc over" really is.



$$\begin{cases} 3 + 1 = i_0 + 3\beta \\ \frac{12k}{i_0} = -4k \end{cases}$$

$$i_0 = -3$$


$$\beta = \frac{7}{3} = 2.33$$

$$(b) \quad \frac{V_{th} - 40}{4k} + \frac{V_{Th}}{12k} = \frac{7}{3} \cdot \frac{V_{Th} - 40}{4k}$$

$$\frac{4}{3} \frac{V_{th} - 40}{4k} = \frac{V_0}{12k}$$

$$4V_{th} - 160 = V_{th}$$

$$V_{th} = \frac{160}{3} \approx 53.3V$$

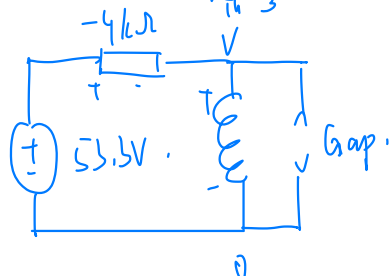

$$\begin{matrix} 50 \times 80 \\ 4000 \end{matrix}$$

$$\ln\left(\frac{i + \frac{1}{75}}{\frac{1}{75}}\right) = 5 \times 10^4 t$$

$$75(i + 1) = e^{5 \times 10^4 t}$$

$$i = \frac{1}{75} e^{5 \times 10^4 t} - \frac{1}{75}$$

$$V = L \frac{di}{dt} = 80 \times 10^{-3} \cdot \frac{5 \times 10^4}{75} e^{5 \times 10^4 t} = \frac{160}{3} e^{5 \times 10^4 t} = 30000$$

$$t = 126.6 \mu s$$

$$-533 - 4ki + 80 \cdot 10^{-3} \cdot \frac{di}{dt} = 0$$

$$\frac{di}{dt} = 4k - \frac{1}{8} \cdot 10^3 i + \frac{160}{3} \cdot \frac{1}{8} \cdot 10^2$$

$$\int_{i + \frac{1}{75}}^{i_0} \frac{di}{dt} = \int_0^t 5 \times 10^4 dt$$