




JOINT INSTITUTE
交大密西根学院

ECE2150J Introduction to Circuits

Chapter 1 Basic Concepts


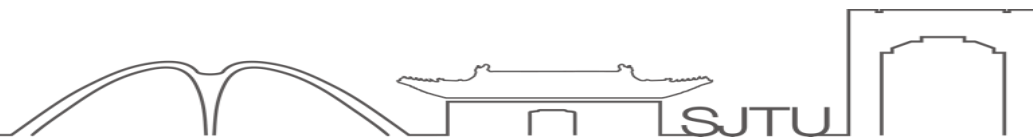
Yuljae Cho, PhD
Associate Professor
UM-SJTU Joint Institute, SJTU



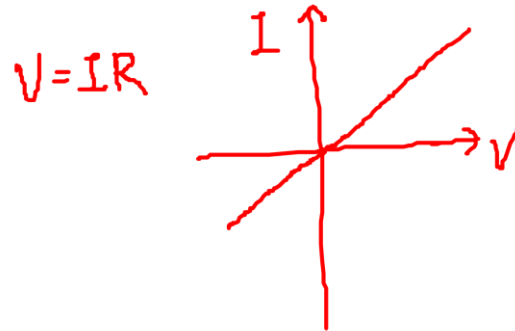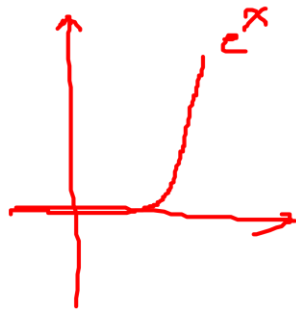1.1 Introduction


- **Electric circuit theory** and **electromagnetic theory** are the two fundamental theories upon which all branches of electrical engineering are built.
- The basic electric circuit theory course is the most important course for an electrical engineering student, and always an excellent starting point for a beginning student in electrical engineering education.
- Circuit theory is also valuable to students specializing in other branches.

- In electrical engineering, we are often interested in **transferring energy** from one point to another.
- This requires an **interconnection of electrical devices**. Such interconnection is referred to as an **electric circuit**, and each component of the circuit is known as an **element**.




Our major concern in this course is the **analysis of the circuits.**

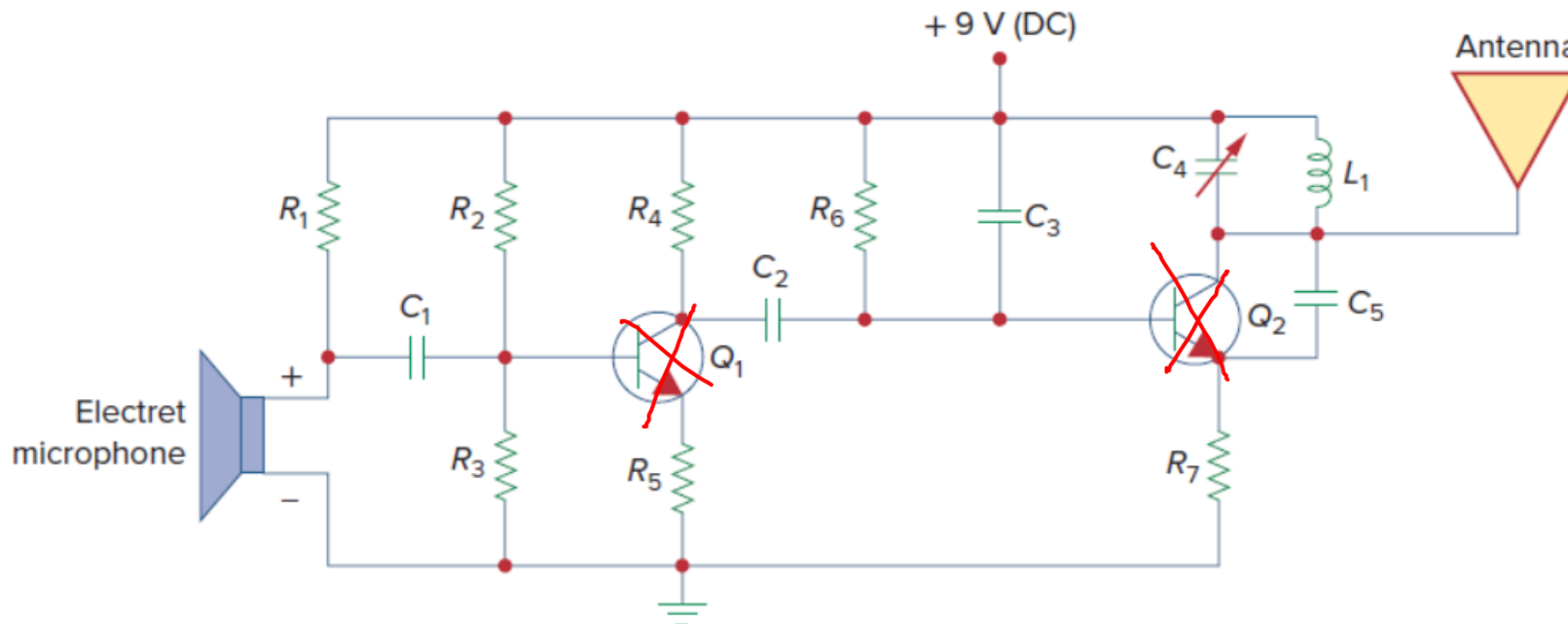- How does it respond to a given input?
- How do the interconnected elements and devices in the circuit interact?



1.3 Charge and Current

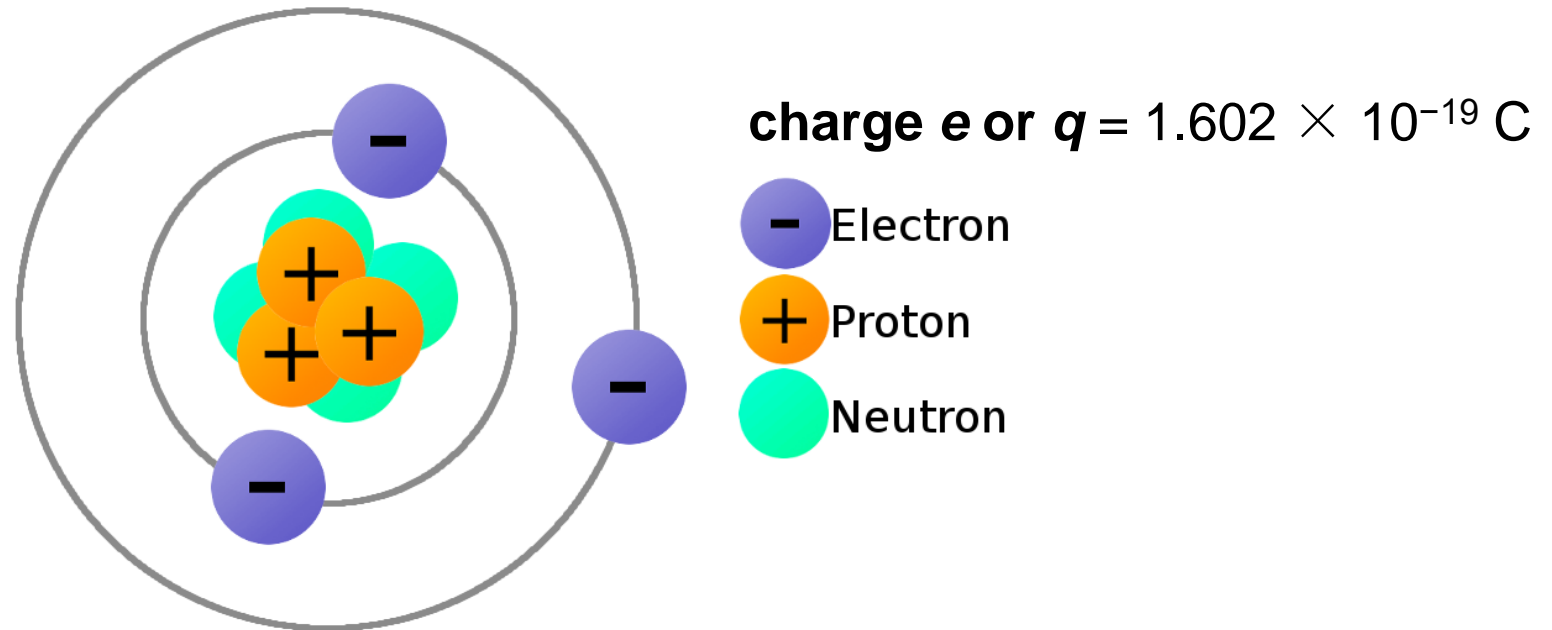


- The concept of electric charge is the underlying principle for explaining all electrical phenomena.
- The most basic quantity in an electric circuit is the **electric charge**.

- Charge is **an electrical property of the atomic particles** of which matter consists, measured in coulombs (C)

$$1 \text{ C } (6.24 \times 10^{18} \text{ electrons}) = 1 \text{ A} \times 1 \text{ s.}$$

- The **law of conservation** of charge states that charge can **neither be created nor destroyed**, only transferred. Thus the algebraic sum of the electric charges in a system does not change.

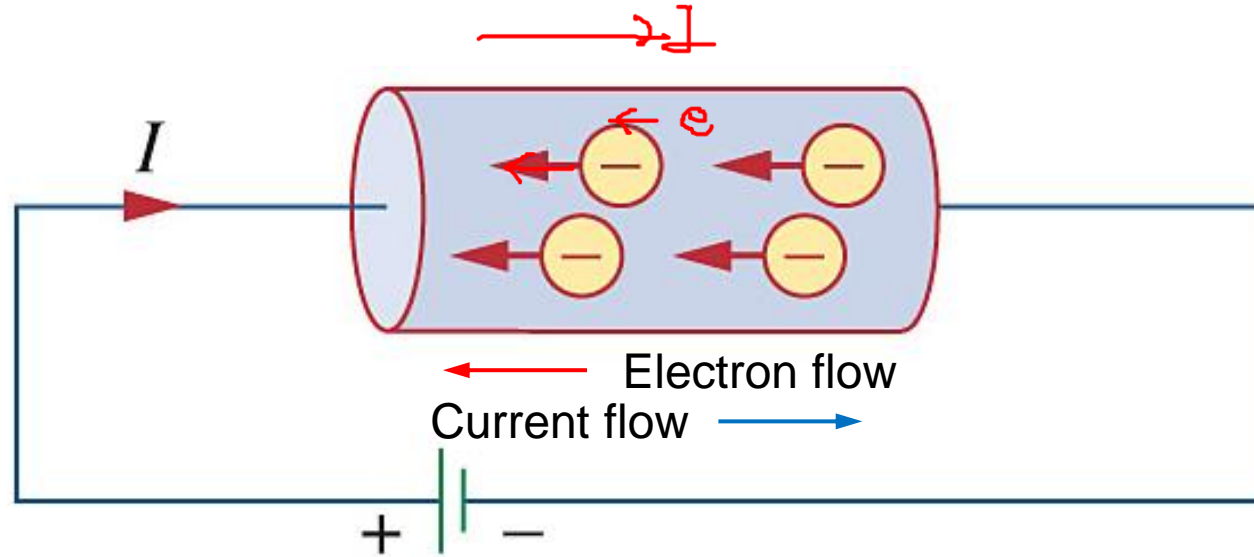- **Electric current is a flow of electric charge** through a conductive medium.



Electric conduction is **due to negatively charged electrons**. However, we follow the universally accepted convention **that current is the net flow of positive charges**.

Electric current (i) is the **time rate of change of charge**, measured in amperes (A).

Mathematically, the relationship between current i [amperes (A)], charge q , and time t



$$i \triangleq \frac{dq}{dt}$$

*1 A = 1 C/sec

The charge transferred between time t_0 and t is obtained by integrating both sides


$$Q \triangleq \int_{t_0}^t i \, dt$$

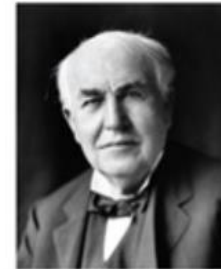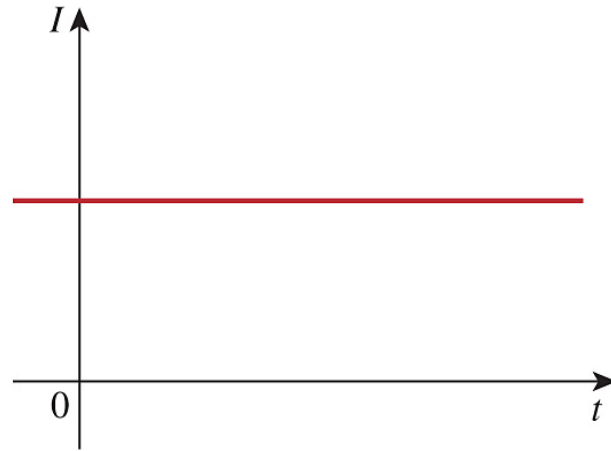- *Direct current* (DC) is the unidirectional flow of electric charge, i.e. a current that remains constant with time.




Thomas
Edison
1847-1931

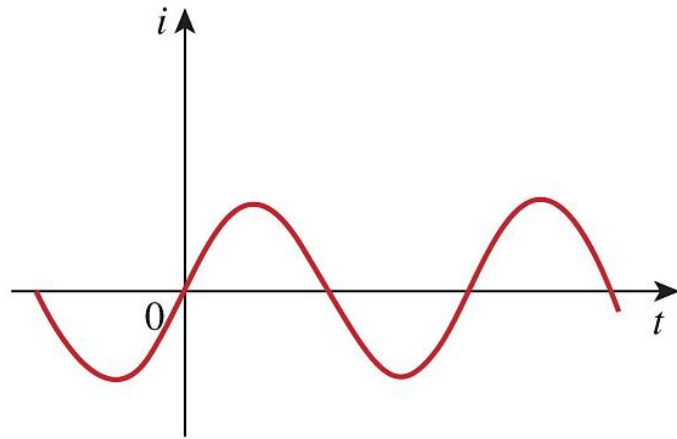- In *alternating current* (AC), the movement of electric charge periodically reverses direction, i.e. a current that varies sinusoidally with time.




George
Westinghouse
1846-1914

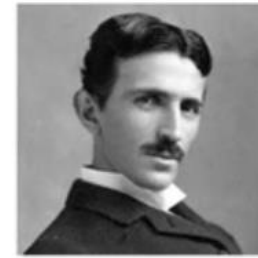

Nikola
Tesla
1856-1943

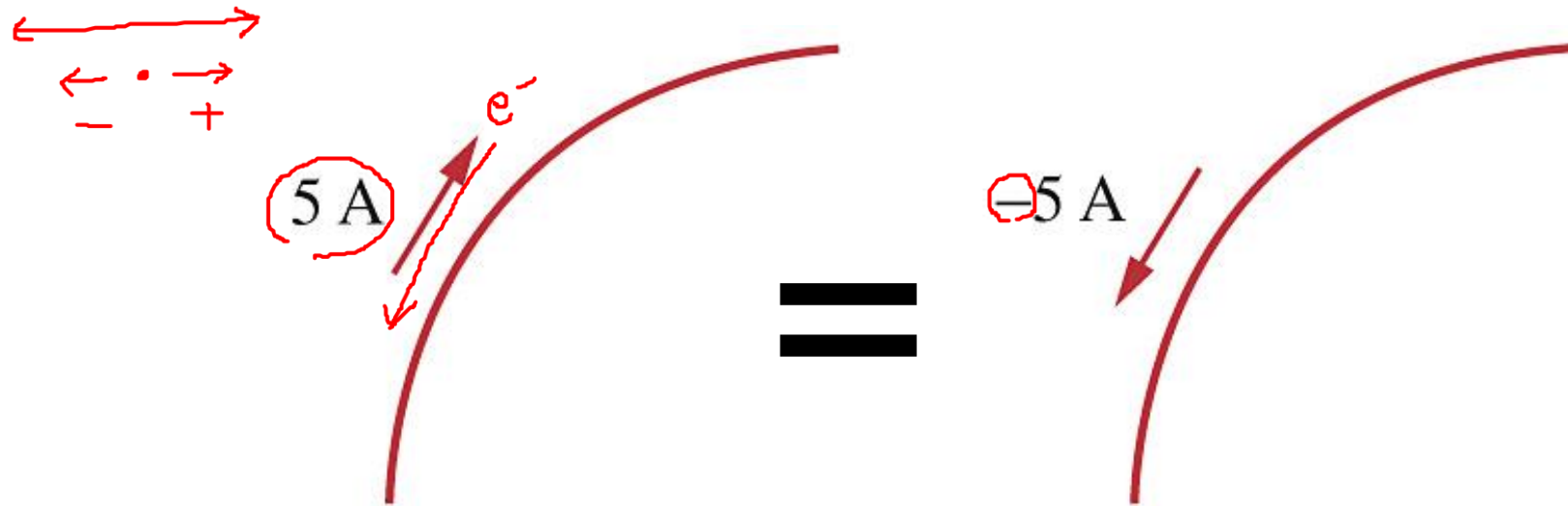- The direction of current is conventionally taken as the direction of **positive charge** movement.



5 A of current is flowing clockwise =
-5 A of current is flowing counter-clockwise

Practice Problem 1.3 The current flowing through an element is

$$i = \begin{cases} 2 \text{ A}, & 0 < t < 1 \text{ s} \\ 2t^2 \text{ A}, & t > 1 \text{ s} \end{cases}$$

Calculate the charge entering the element from $t = 0$ to $t = 2$ s.

Solution :

$$\begin{aligned} Q &= \int_0^2 i dt = \int_0^1 2 dt + \int_1^2 2t^2 dt = 2t \Big|_0^1 + 2 \frac{t^3}{3} \Big|_1^2 \\ &= 2 + \frac{14}{3} \approx 6.667 \text{ (C)} \end{aligned}$$

1.4 Voltage


- Voltage (or potential difference) is the **energy (or work) required** to move a unit charge through an element, measured in volts (V).

Mathematically, the voltage between two points a and b in an electric circuit is

$$v_{ab} \triangleq \frac{dw}{dq} \quad \text{where } w \text{ is energy in joules (J) and } q \text{ is charge in coulombs (C)}$$

$$1 \text{ volt} = 1 \text{ joule/coulomb} = 1 \text{ newton-meter/coulomb}$$

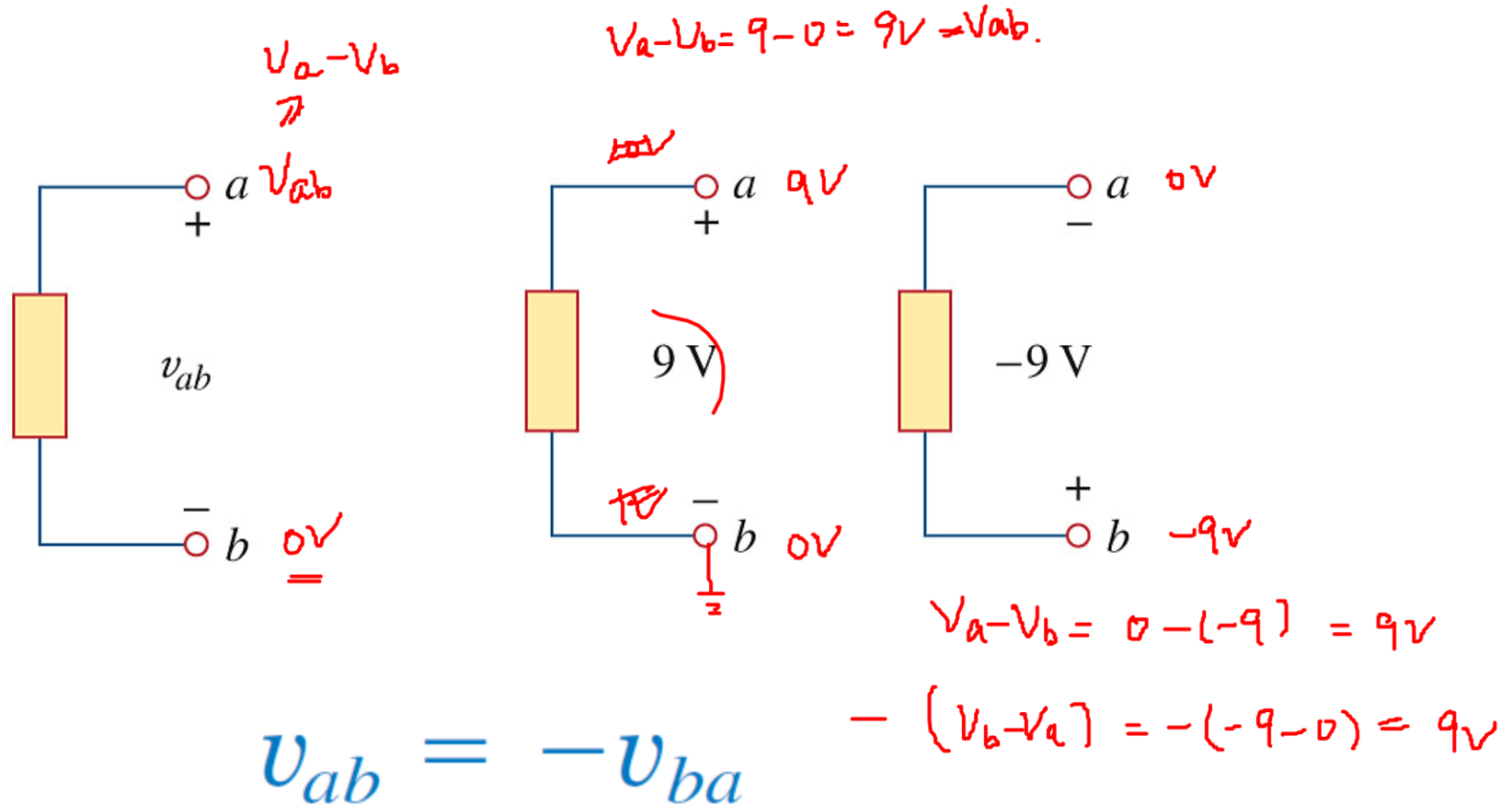- The plus (+) and minus (-) signs are used to define **reference direction or polarity** of the voltage.




- Current and voltage are the two basic variables in electric circuits. The common term, **signal**, is used for an electric quantity such as a current or a voltage (or even electromagnetic wave) when it is used for conveying information.

1.5 Power and Energy

- **Power** is the time rate of expending or absorbing energy, measured in **watts (W)**.
- The power $p = v i$ is a **time-varying** quantity and is called the instantaneous power.


$$p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi$$

w is energy in joules (J)

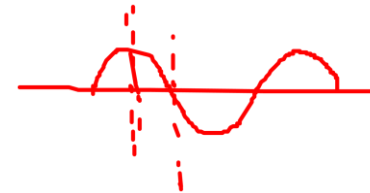


Passive sign convention:

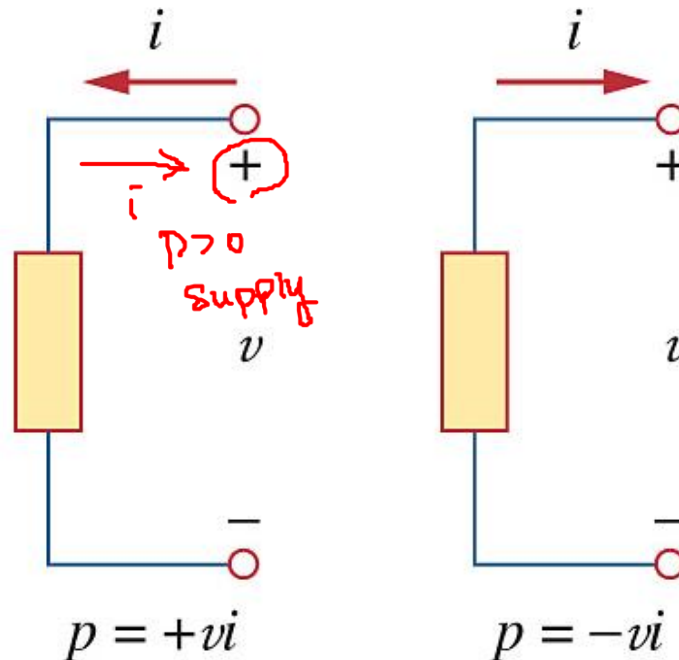- When the current enters through the positive terminal of an element
- $p = +vi > 0$ implies that the element is **consuming power**.
- $p = -vi < 0$ implies that the element is **supplying power**.



*Unless otherwise stated, we **follow the passive sign convention** from now on.


example

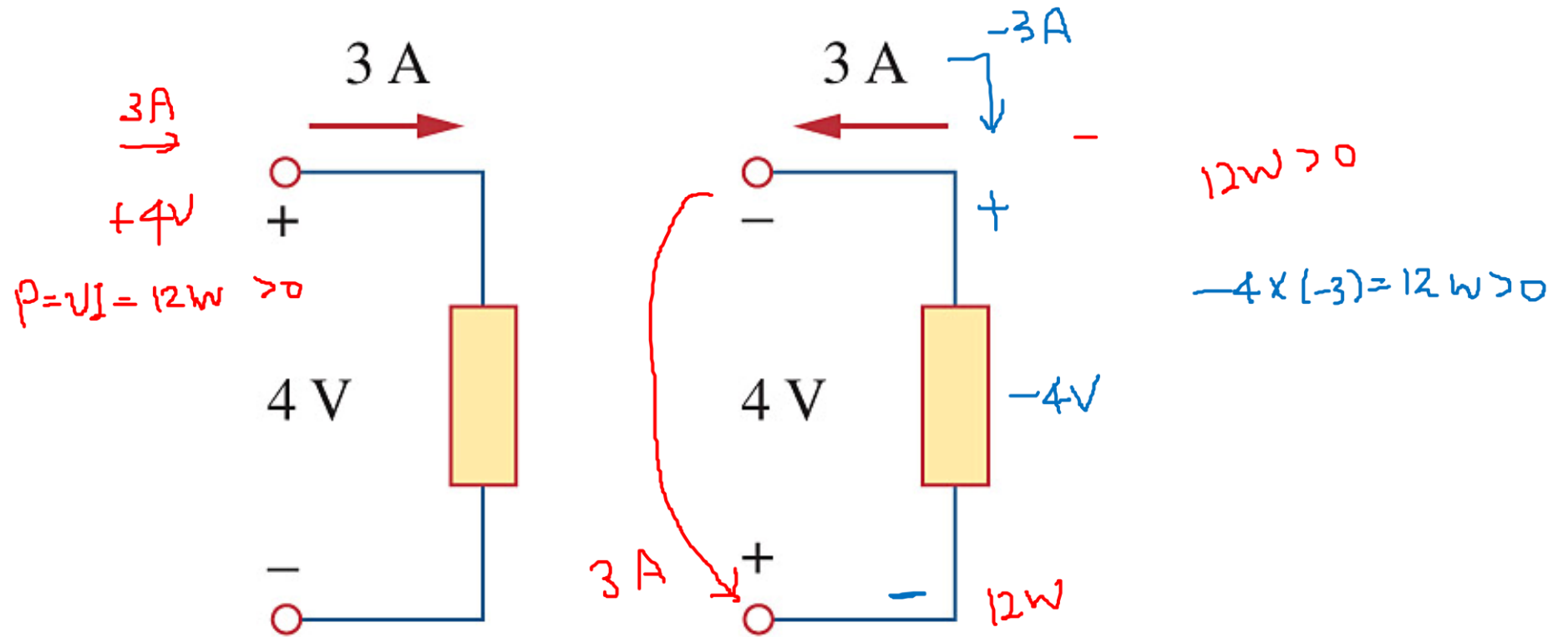

✓
(a) Absorbing power
(b) Supplying power

✓
(a) Absorbing power
(b) Supplying power

example

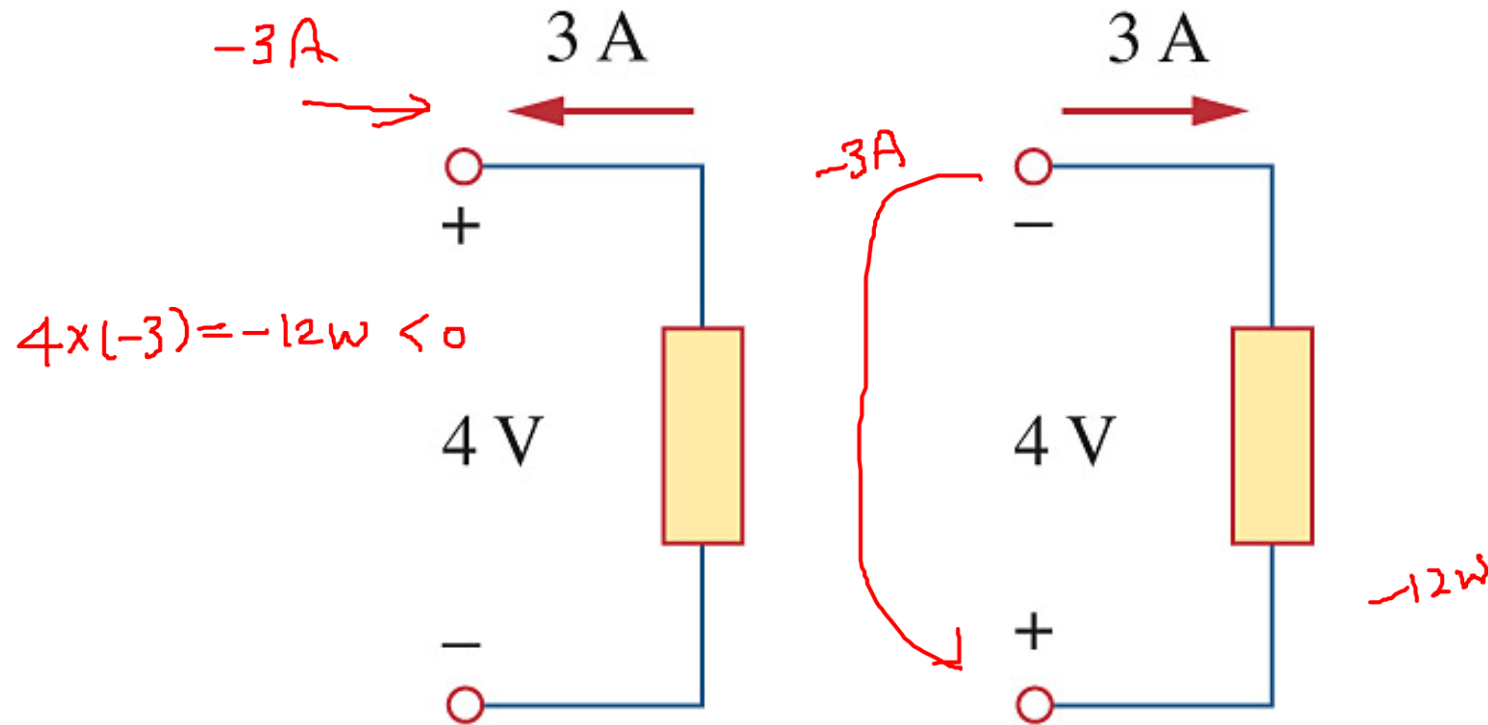

- (a) Absorbing power
- ✓ (b) Supplying power

- (a) Absorbing power
- ✓ (b) Supplying power

- In fact, the law of conservation of energy must be obeyed in any electric circuit. For this reason, **the algebraic sum of power** in a circuit, at any instant of time, **must be zero**:

$$\sum p = 0$$

- **Energy** is the capacity to do work, measured in **joules (J)**.

The energy absorbed by an element from time t_0 to time t is

$$w = \int_{t_0}^t p dt = \int_{t_0}^t v i dt$$

Practice Problem 1.5 Find the power delivered to an element at $t = 5$ ms if the current entering its positive terminal is

$$i = 5 \cos 60\pi t \text{ A}$$

and the voltage is (a) $v = 2i$ V, (b) $v =$

$$\left(10 + 5 \int_0^t i dt \right) \text{ V}.$$

Hint: $p = vi$

Solution :

(a) The power delivered to (or absorbed by) the element is 17.27 W:

$$\begin{aligned} p &= vi = 2i^2 = 2(5 \cos 60\pi t)^2 = 50 \cos^2 60\pi t \\ &= 50 \cos^2 (60\pi \times 5 \times 10^{-3}) \approx 17.27 \text{ (W)} \end{aligned}$$

(b) The power delivered to the element is 29.70 W:


$$\begin{aligned}
v &= 10 + 5 \int_0^t i dt = 10 + 5 \int_0^t 5 \cos 60\pi t dt \\
&= 10 + \frac{25}{60\pi} \sin 60\pi t \Big|_0^t = 10 + \frac{5}{12\pi} \sin 60\pi t \\
&= 10 + \frac{5}{12\pi} \sin(60\pi \times 5 \times 10^{-3}) \approx 10.1073 \text{ (V)} \\
i &= 5 \cos 60\pi t = 5 \cos(60\pi \times 5 \times 10^{-3}) \\
&\approx 2.9389 \text{ (A)} \\
p &= vi = 10.1073 \times 2.9389 \approx 29.70 \text{ (W)}
\end{aligned}$$

1.6 Circuit Elements

- There are two types of elements found in electric circuits
 - **Passive elements:** devices that cannot generate electric energy, such as, resistors, capacitors, inductors.
 - **Active elements:** devices capable of generating electric energy, such as, generators, batteries, operational amplifiers.

- The most **important active elements** are **voltage or current sources**. There are two kinds of sources

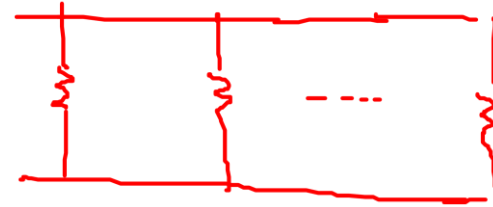- Independent sources
- Dependent sources



- An ideal independent **voltage/current source** is an active element that provides a **specified voltage/current** that is completely independent of other circuit elements.

Independent voltage source

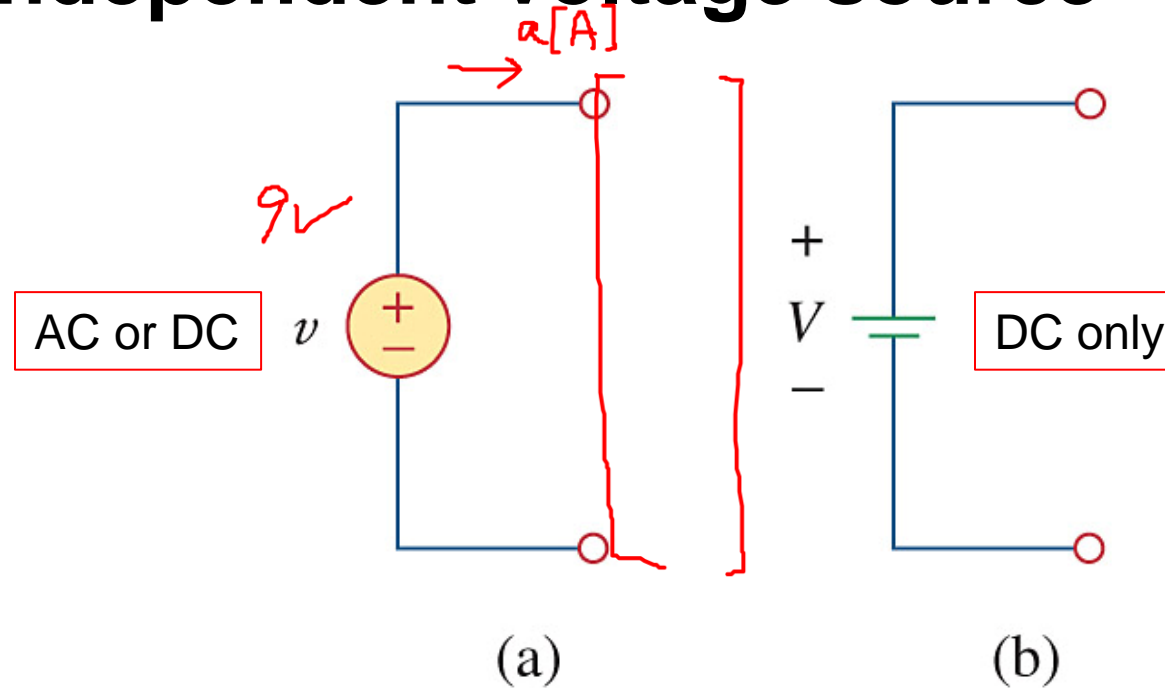


Figure 1.11 Symbols for independent voltage sources:
(a) used for constant or time-varying voltage source,
(b) used for constant voltage source.

v is fixed at a specified value, i can be any value

Independent current source


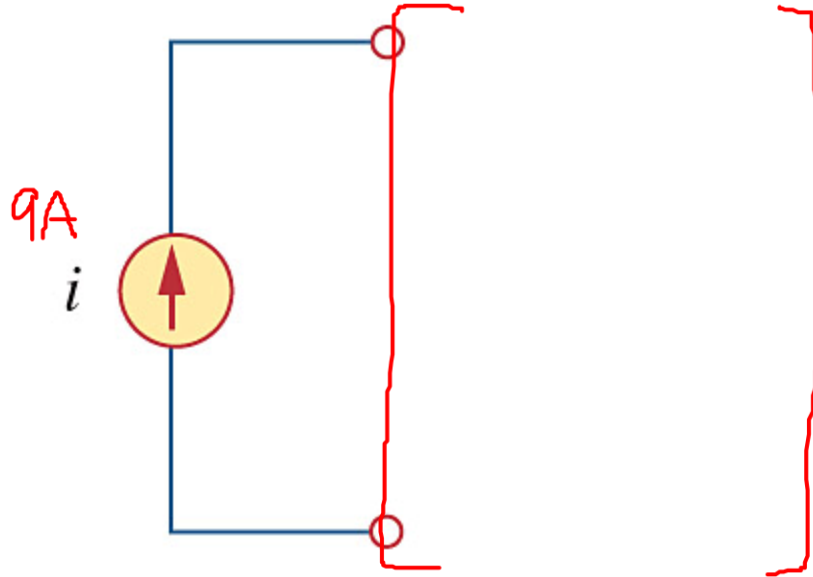


Figure 1.12 Symbols for independent current source.


i is fixed at a specified value, v can be any value

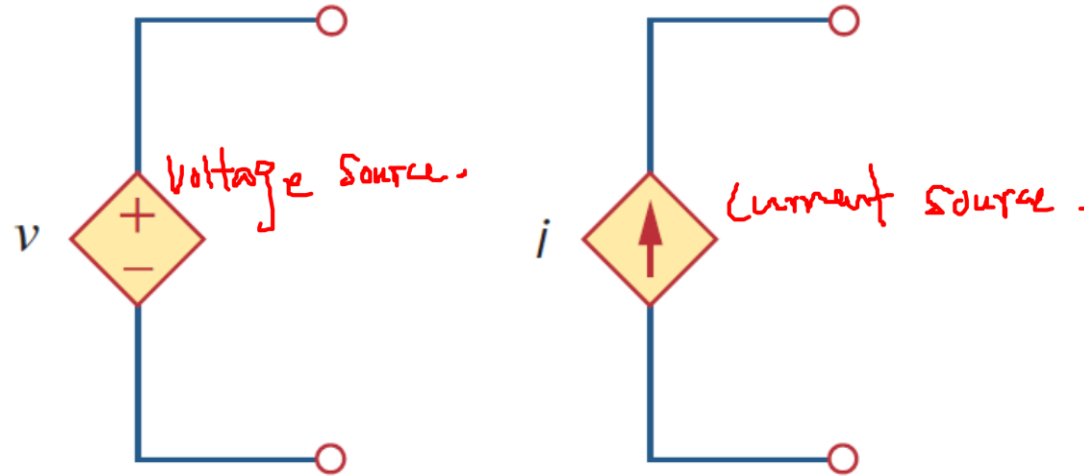- **An ideal dependent (or controlled) source** is an active element in which the source quantity is **controlled by another voltage or current**, for example, the value of a voltage or current elsewhere in the circuit. e.g., op-amp, transformers, transistors, etc.



- There are four possible types of dependent sources
 - A voltage-controlled voltage source (VCVS)
 - A current-controlled voltage source (CCVS)
 - A voltage-controlled current source (VCCS)
 - A current-controlled current source (CCCS)

Example

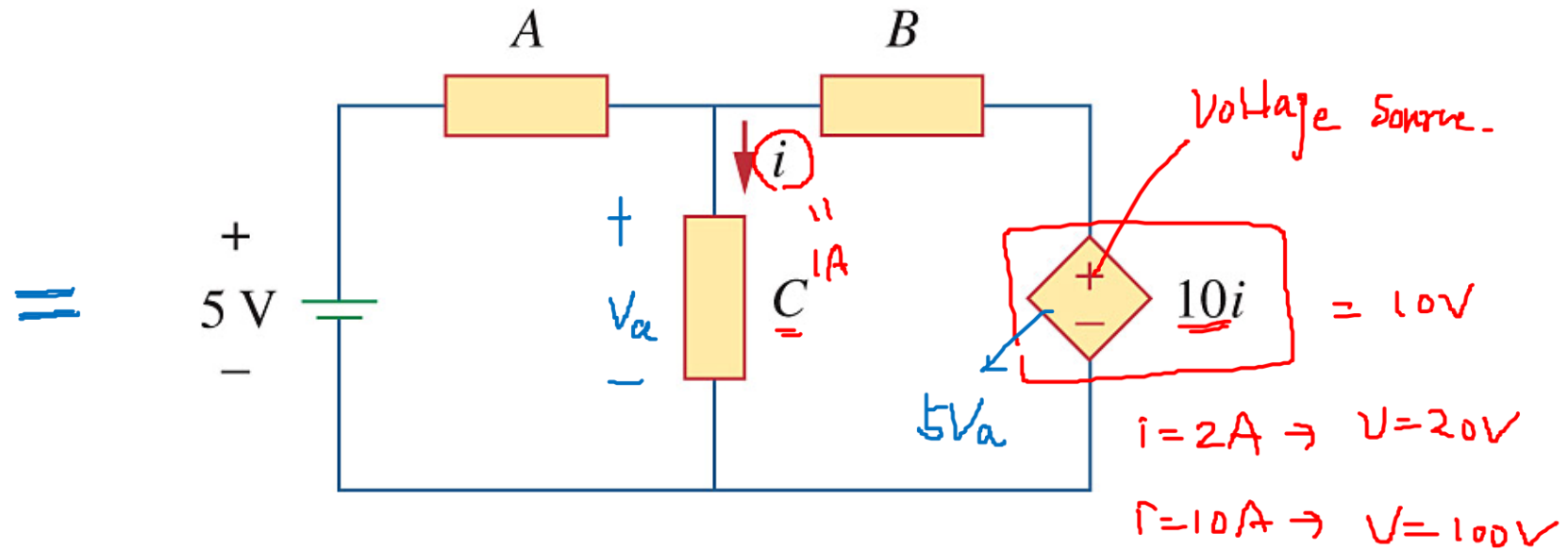

- (a) A voltage-controlled voltage source (VCVS)
- ☒ (b) A current-controlled voltage source (CCVS)
- (c) A voltage-controlled current source (VCCS)
- (d) A current-controlled current source (CCCS)

Practice Problem 1.7 Compute the power absorbed or supplied by each component of the circuit Figure 1.16.

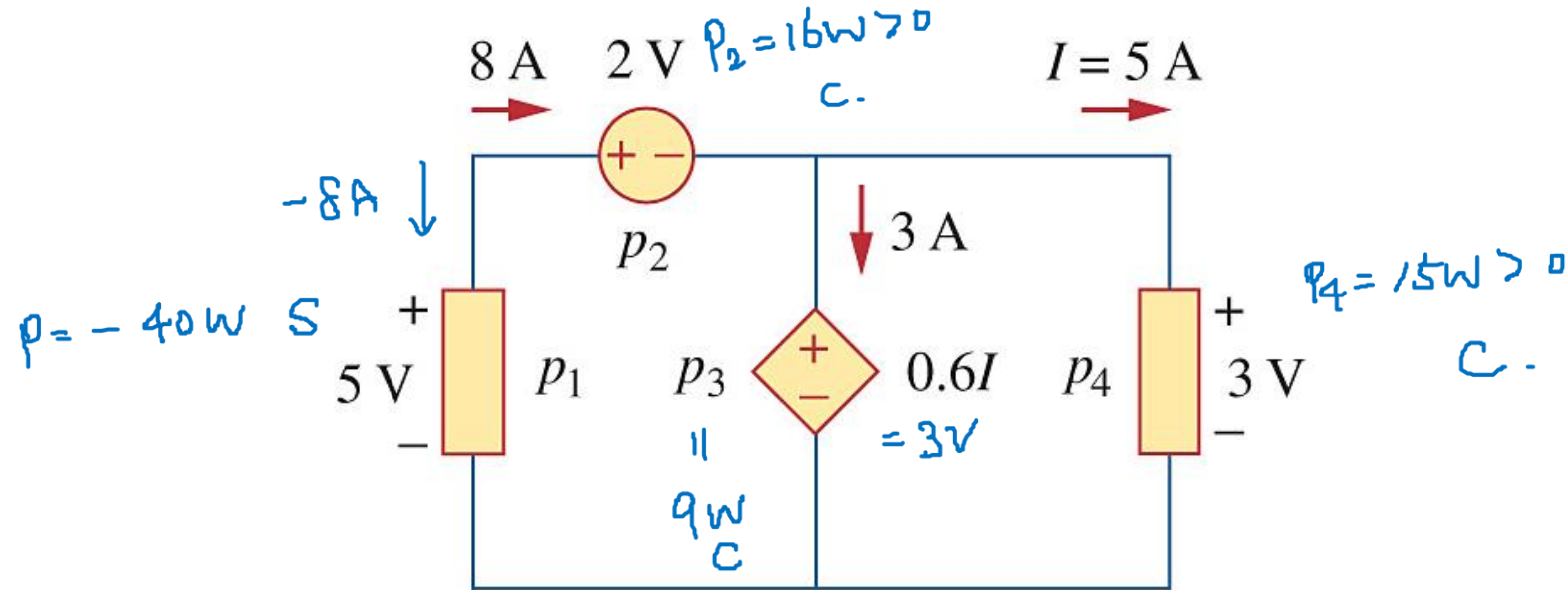


Figure 1.16

Solution : We apply the passive sign convention.

$$p_1 = 5 \times (-8) = -40 \text{ (W)}$$

$$p_2 = 2 \times 8 = 16 \text{ (W)}$$

$$p_3 = (0.6 \times 5) \times 3 = 9 \text{ (W)}$$

$$p_4 = 3 \times 5 = 15 \text{ (W)}$$