

$$V_{5} = (R_{1}+jX_{1}+R_{2})I_{1}-R_{2}I_{2}-jX_{m}I_{2}$$

$$(jX_{12}-jX_{1}+R_{3}+R_{2})I_{2}-R_{2}I_{1}-jX_{m}I_{1}=0$$

$$V_{5} = (J_{0}+jI_{5})I_{1}-(J_{1}+J_{2})I_{2}$$

$$(jI_{1}-J_{1}+J_{5})I_{2}-(J_{1}+J_{2})I_{1}=0$$


$$I_{2} = \frac{J+J_{2}}{|J_{1}+J_{1}|^{2}-J_{1}}I_{1}$$

$$I_1 = (0.0286 - j0.0492) V_5 = 0.569 / -14.83^{\circ}$$

$$I_2 = (-9.372 \times 10^{-5} - j0.0125) V_5 = 0.125 / -45.43^{\circ}$$

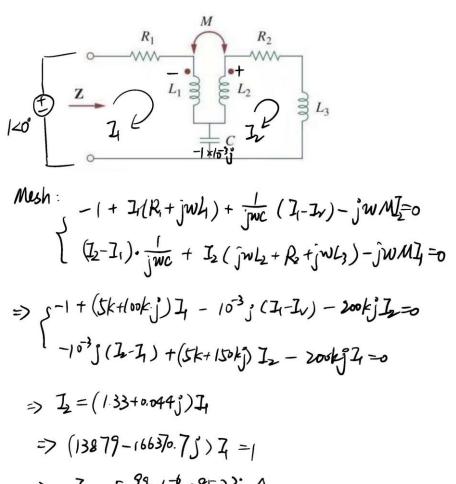Q2 All RMS


*correction $\omega = 10k \text{ rad/s}, \text{ not Hz}.$



$$\Rightarrow I = 5.99 \times 10^{-6} \times 23^{\circ} A$$


$$\Rightarrow Z = \frac{(20)}{4} = 1.67 \times 10^{5} \times -85.23^{\circ} J2$$

Q3

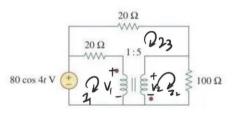

Mesh :
$$0 - 80 + 20 (1-13) + V_1 = 0$$

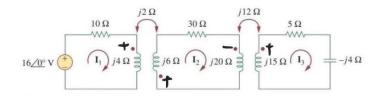3
$$40l_3-20l_1+1/2-1/1=0$$
For transformers: $6=-5V_1$
 $1_1-1_3=-5(1_2-1_3)$



Much:

$$\begin{cases}
1b = (10+j4) \frac{1}{4} + j212 \\
0 = j21 + (30+j26) \frac{1}{4} - j013 \\
0 = -j014 + (5+j11) \frac{1}{4}
\end{cases}$$

$$\begin{array}{c} 1 = 1475 \ 2-21.41^{\circ} \ A \\ 1 = 77.5 \ 2-134.85^{\circ} \ mA \\ 1 = 772-110.40^{\circ} \ mA \end{array}$$