

上海交通大学试卷

(2024~2025~1 Academic Year/Fall Semester)

Class No. _____ Name in English or Pinyin: _____

Student ID No. _____ Name in Hanzi(if applicable): _____

ECE2150J and Intro to Circuits

Mid-term Exam

12th November 10:00 – 11:40 am

The exam paper has 13 pages in total.

You are to abide by the University of Michigan-Shanghai Jiao Tong University Joint Institute (UM-SJTU JI) honor code. Please sign below to signify that you have kept the honor code pledge.

THE UM-SJTU JI HONOR CODE

I accept the letter and spirit of the honor code:



I have neither given nor received unauthorized aid on this examination, nor have I concealed any violations of the Honor Code by myself or others.

Signature: _____

Please enter grades here:

Exercises No. 题号	Points 得分	Grader’s Signature 流水批阅人签名
1		
2		
3		
4		
5		
6		
Total 总分		

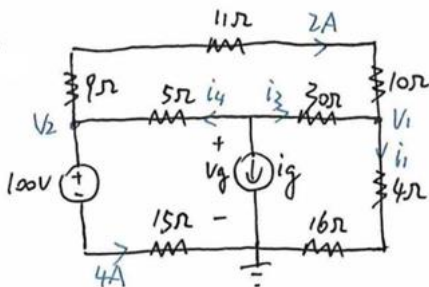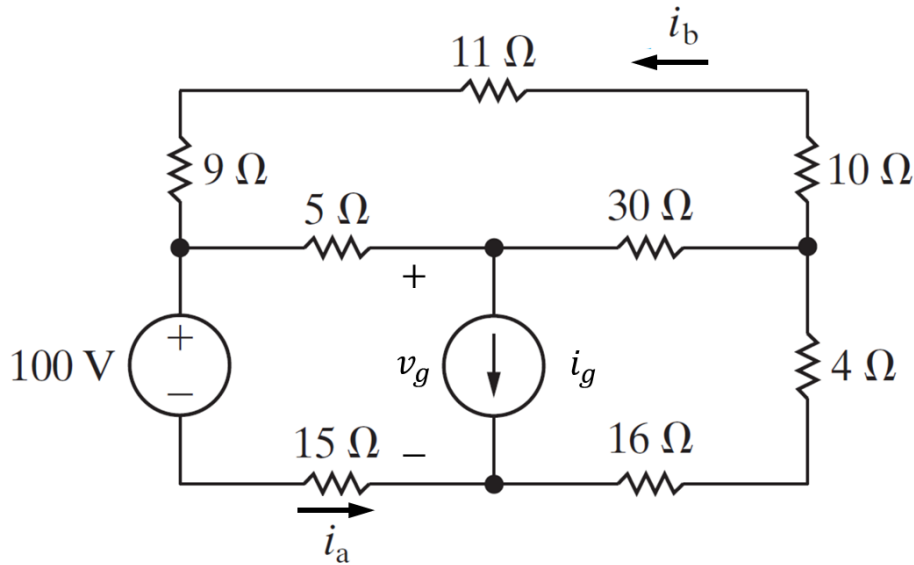1. The currents i_a and i_b in the circuit are 4 A and -2 A respectively. Find i_g and v_g . [8 points]



$$V_2 = 100 + 4 \times 15 = 160 \text{ V} \quad 1'$$

$$V_1 = 160 - (9 + 11 + 10) \times 2 = 100 \text{ V} \quad 1'$$

$$i_1 = \frac{V_1}{4 + 16} = \frac{100}{20} = 5 \text{ A} \quad 1'$$


$$i_3 = i_1 - 2 = 5 - 2 = 3 \text{ A} \quad 1'$$

$$V_g = V_1 + 30 i_3 = 100 + 30 \times 3 = 190 \text{ V} \quad 2'$$

$$i_4 = \frac{V_g - V_2}{5} = \frac{190 - 160}{5} = 6 \text{ A}$$

$$i_g = -i_4 - i_3 = -6 - 3 = -9 \text{ A} \quad 2'$$

or mesh analysis:

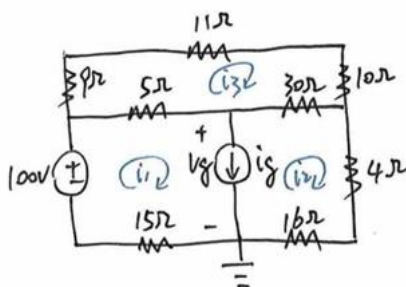

$$\begin{cases} i_1 = -4 \text{ A}, i_3 = 2 \text{ A} \end{cases}$$

$$15 i_1 + 5(i_1 - i_3) + V_g = 100 \quad 1'$$


$$(4 + 16) i_2 + 30(i_2 - i_3) = V_g \quad 1'$$


$$(9 + 11 + 10) i_3 + 30(i_3 - i_2) + 5(i_3 - i_1) = 0 \quad 1'$$

$$i_g = i_1 - i_2 \quad 1'$$

$$V_g = 190 \text{ V} \quad 2' \quad i_g = -9 \text{ A} \quad 2'$$

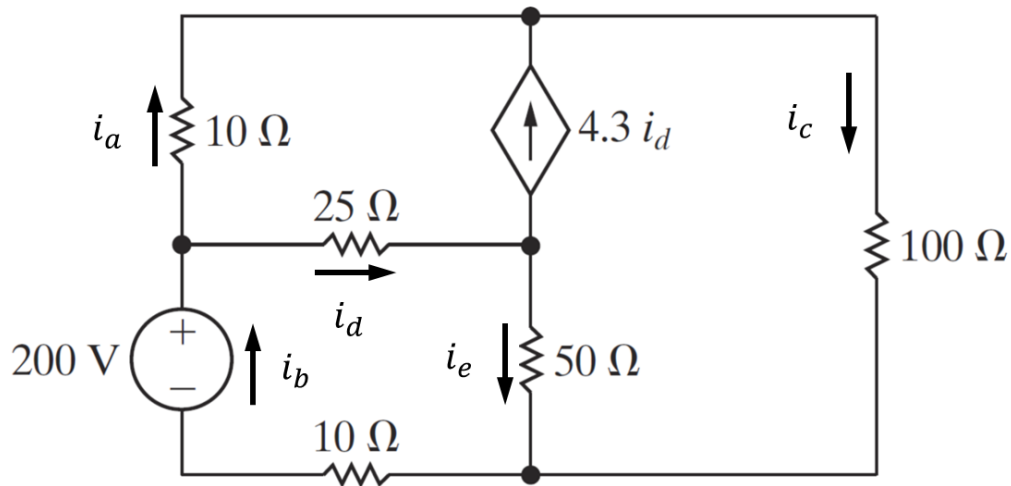2. (a) Use the mesh-current method to find the branch currents in $i_a \sim i_e$ in the circuit below. [8 points]
- (b) Check your solution by showing that the total power generated in the circuit equals the total power consumed. [8 points]



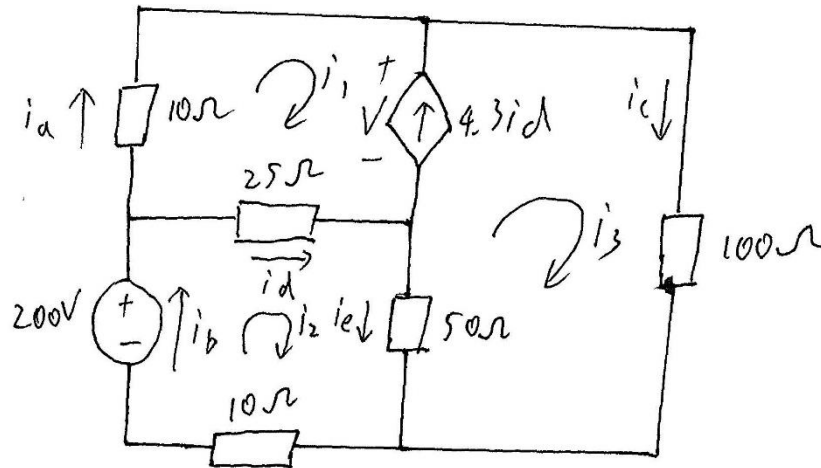

(a) $i_a = i_1$ $i_b = i_2$ $i_c = i_3$ $i_e = i_2 - i_3$ $i_d = i_2 - i_1$ (1pts)

Mesh analysis

(1)
$$\begin{cases} 200 - 25(i_2 - i_1) - 50(i_2 - i_3) - 10i_2 = 0 \\ i_3 - i_1 = 4.3i_d \\ i_d = i_2 - i_1 \\ 200 - 10i_1 - 100i_3 - i_2 \cdot 10 = 0 \text{ (outer loop)} \end{cases} \quad (4 \text{ pt})$$

(2)
$$\begin{cases} 200 - 25(i_2 - i_1) - 50(i_2 - i_3) - 10i_2 = 0 \\ i_3 - i_1 = 4.3i_d \\ i_d = i_2 - i_1 \\ 10i_1 + 100i_3 - (i_2 - i_3) \cdot 50 - 25(i_2 - i_1) = 0 \text{ (super mesh)} \end{cases}$$

\Rightarrow (1)
$$\begin{cases} 25i_1 - 85i_2 + 50i_3 = -200 \\ 3.3i_1 - 4.3i_2 + i_3 = 0 \\ 10i_1 + 10i_2 + 100i_3 = 200 \end{cases} \Rightarrow \begin{cases} i_1 = 5.7A \\ i_2 = 4.6A \\ i_3 = 0.97A \end{cases} \quad (1 \text{ pt})$$

(2)
$$\begin{cases} 25i_1 - 85i_2 + 50i_3 = -200 \\ 3.3i_1 - 4.3i_2 + i_3 = 0 \\ 35i_1 - 75i_2 + 150i_3 = 0 \end{cases}$$

$\Rightarrow i_a = 5.7A$ $i_b = 4.6A$ $i_c = 0.97A$ $i_d = -1.1A$ $i_e = 3.63A$ (2pts)

(b) Power develop \Rightarrow Voltage source, Current source

Power Dissipate \Rightarrow All resistor (2pts with formula)

$$\sum P_{dis} = \sum I^2 R = (5.7)^2 10 + (1.1)^2 25 + (0.97)^2 100 + (4.6)^2 10 + (3.63)^2 50 = \underline{\underline{1319.685 \text{ W}}} \quad (2pts)$$

$$P_{voltage} = -(200 \cdot i_b) = -920 \text{ W} \quad (2pts)$$

$$10 i_a + V_{current} + 25(1.1) = 0 \Rightarrow V_{current} = 84.5 \text{ V} \quad (1pt)$$


$$P_{current} = -VI = -399.685 \text{ W} \quad (2pts)$$


$$P_{dev} = P_{voltage} + P_{current} = 1319.685 \text{ W} = P_{dis}$$

3. The variable resistor (R_O) in the circuit is adjusted until it absorbs maximum power from the circuit.

(a) Find the value of R_O . [12 points]

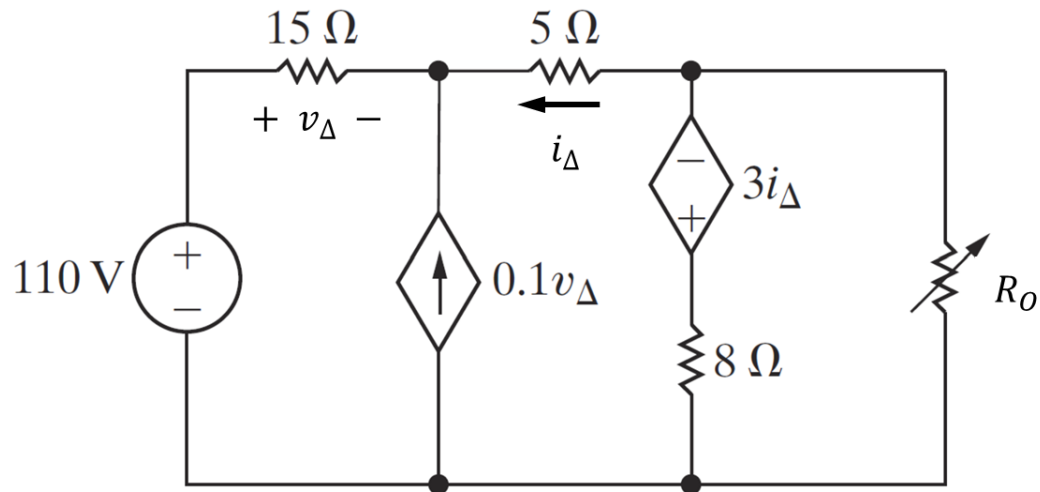(b) Find the maximum power delivered to R_O . [4 points]



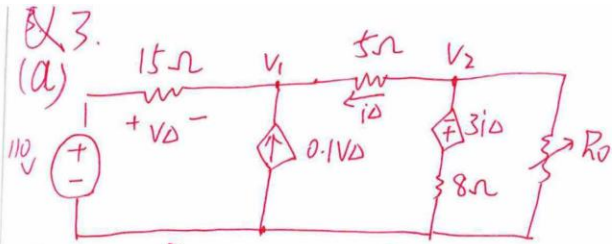

Suppose R_0 is open: $R_0 \rightarrow \infty$

$$\frac{V_\Delta}{15} + 0.1V_\Delta + i_\Delta = 0 \quad |'$$


$$\begin{cases} V_\Delta = 110 - V_1 \\ 5i_\Delta = V_2 - V_1 \\ \frac{V_2 - V_1}{5} + \frac{V_2 + 3i_\Delta}{8} = 0 \end{cases} \quad |'$$

$$\Rightarrow \begin{cases} V_1 = 80V \\ V_2 = 55V = V_{Th} \end{cases} \quad 3'$$

Now, calculate R_{th}

Recall that P_{max} is achieved when $R_0 = R_{th}$. $|'$

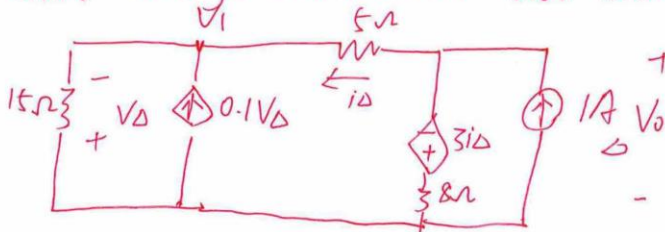Short voltage source, add test source $i = 1A$



$$\begin{cases} 1 = i_\Delta + \frac{V_0 + 3i_\Delta}{8} \\ \frac{V_\Delta}{15} + 0.1V_\Delta + i_\Delta = 0 \\ V_0 - 5i_\Delta = -V_\Delta \\ V_\Delta = -V_1 \end{cases} \quad |'$$

$$V_0 = 4V \quad R_{th} = \frac{V_0}{1} = 4\Omega$$

$$\Rightarrow R_0 = R_{th} = 4\Omega \quad 4'$$



$$P_{max} = \frac{(27.5V)^2}{R_0} = \frac{V_{Th}^2}{4R_0} = 189.0625 W.$$

PS: 第一问若只求了 R_0

结果对: $R_0 = 4\Omega$ 直接2' 第2问

不对: 给 R_0 过程分

看第二问是否求了 V_{th}

相应的在第二问给分

If one gets full mark in (a)

we do not offer credit

in (b) for V_{th} calculation.

full mark is offered for each


of the sub-question


as long as the result is correct

4. Show that if $\Delta R \ll R$, the output voltage of the op amp is approximately

$$v_o \approx \frac{R_f(R + R_f)}{R^2(R + 2R_f)}(-\Delta R)v_{in}$$

for the circuit below. [20 points]

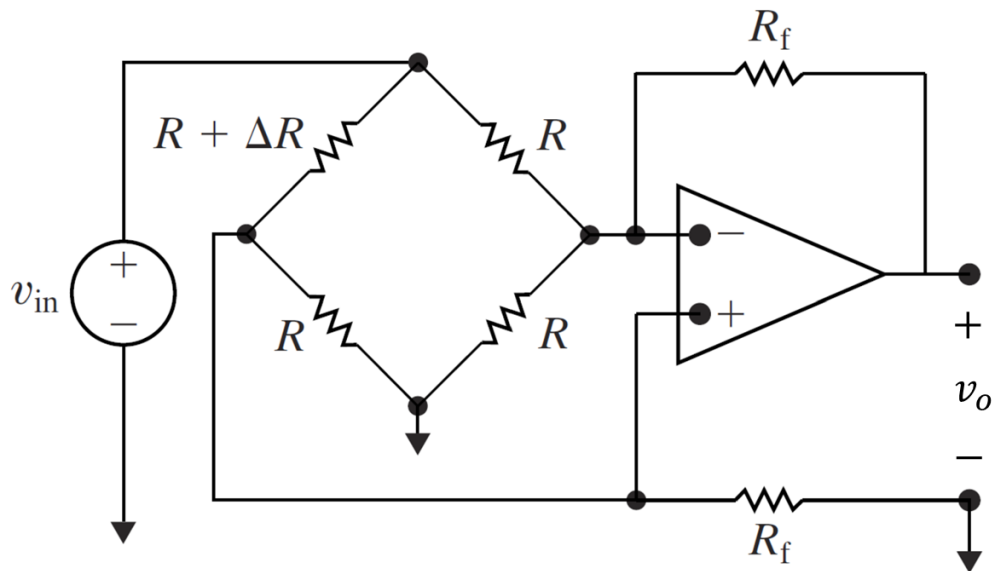

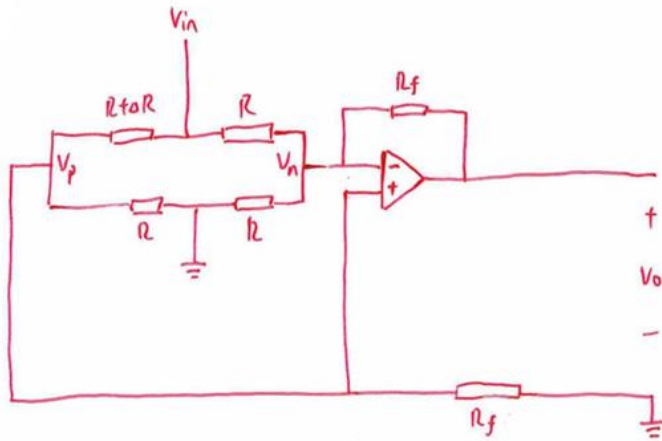

$$\frac{V_p}{R_f} + \frac{V_p}{R} + \frac{V_p - V_{in}}{R + \Delta R} = 0 \quad (KCL) \quad \dots \quad 2'$$

$$V_p \left(\frac{1}{R_f} + \frac{1}{R} + \frac{1}{R + \Delta R} \right) = V_{in} \frac{1}{R + \Delta R}$$

$$\frac{V_n}{R} + \frac{V_n - V_{in}}{R} + \frac{V_n - V_o}{R_f} = 0 \quad (KCL) \quad \dots \quad 2'$$

$$V_n \left(\frac{1}{R} + \frac{1}{R} \right) - \frac{1}{R_f} V_o = \frac{1}{R} V_{in}$$

$$V_n \left(\frac{1}{R} + \frac{1}{R_f} \right) - \frac{1}{R} V_{in} = \frac{1}{R_f} V_o$$

$$V_p = V_n \quad (\text{property of op amp}) \quad \dots \quad 1'$$

$$V_p = V_{in} \frac{\frac{1}{R + \Delta R}}{\frac{1}{R_f} + \frac{1}{R} + \frac{1}{R + \Delta R}}$$

$$= \frac{1}{\frac{R + \Delta R}{R_f} + \frac{R + \Delta R}{R} + 1} V_{in}$$

$$= \frac{R_f R}{R^2 + R \Delta R + 2 R R_f + R_f \Delta R} V_{in} \quad \dots \quad 2'$$

$$\frac{R_f R}{R^2 + R \Delta R + 2 R R_f + R_f \Delta R} \times \frac{2 R_f + R}{R R_f} V_{in} - \frac{1}{R} V_{in} = \frac{1}{R_f} V_o$$


$$\left(\frac{2 R_f + R}{R^2 + R \Delta R + 2 R R_f + R_f \Delta R} - \frac{1}{R} \right) V_{in} = \frac{1}{R_f} V_o$$

$$\frac{-R \Delta R - R_f \Delta R}{R (R^2 + R \Delta R + 2 R R_f + R_f \Delta R)} V_{in} = \frac{1}{R_f} V_o \quad \dots \quad 6'$$


$$V_o = \frac{-\Delta R R_f (R + R_f)}{R (R^2 + R \Delta R + 2 R R_f + R_f \Delta R)} V_{in} \approx \frac{-\Delta R R_f (R + R_f)}{R (R^2 + 2 R R_f)} V_{in} = \frac{-\Delta R R_f (R + R_f)}{R^2 (R + 2 R_f)} V_{in} \quad \dots \quad 2'$$

5. The switch in the circuit below has been closed for a long time. The maximum voltage rating of the $1.6 \mu\text{F}$ capacitor is 14.4 kV . How long after the switch is opened does the voltage across the capacitor reach the maximum voltage rating? Please follow steps below.

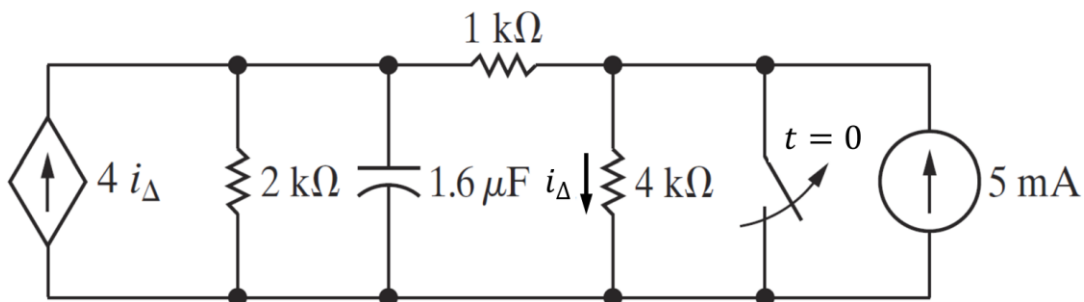
- (a) Find Thevenin equivalent circuit seen from the capacitor. [10 points]
- (b) Derive a capacitor voltage in the Thevenin circuit, i.e. RC circuit. [6 points]
- (c) Find time for the capacitor to reach the maximum voltage rating. [4 points]



1a) after opening the switch

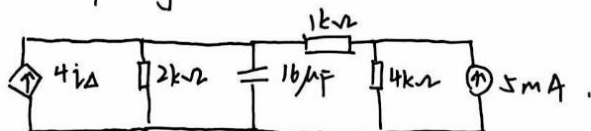


① V_{TH} :

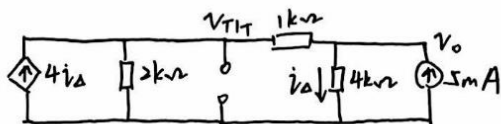

$$\begin{cases} -4i_A + \frac{V_{TH}}{2000} + \frac{V_{TH} - V_o}{1000} = 0 & 1' \\ \frac{V_o - V_{TH}}{1000} + i_A - 5 \times 10^{-3} = 0 & 1' \\ i_A = \frac{V_o}{4000} & 1' \end{cases} \Rightarrow \begin{aligned} V_o &= -60V \\ V_{TH} &= -80V & 2' \end{aligned}$$


② R_{TH} :

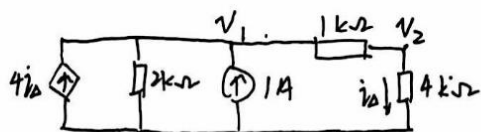

we add a 1A current source here.

$$\begin{cases} -4i_A + \frac{V_1}{2000} - 1 + \frac{V_1 - V_2}{1000} = 0 & 1' \\ \frac{V_2 - V_1}{1000} + \frac{V_2}{4000} = 0 & 1' \\ i_A = \frac{V_2}{4000} \end{cases} \Rightarrow \begin{aligned} V_1 &= -10kV \\ V_2 &= -8kV \\ R_{TH} &= \frac{V_1}{1A} = -10k\Omega & 2' \end{aligned}$$

Thevenin equivalent:

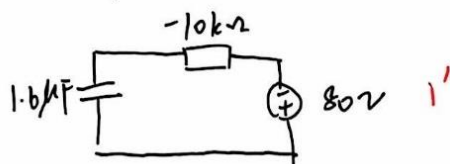

$$(b) \quad v_c(0) = 0 \quad v_c(\infty) = -80V.$$

$$\tau = RC = -10000 \times 1.6 \times 10^{-6} = -16 \text{ ms}.$$

$$\frac{1}{\tau} = -62.5.$$

$$\begin{aligned} v_c(t) &= v_c(\infty) + [v_c(0^+) - v_c(\infty)] e^{-t/\tau} \\ &= -80 + 80 e^{62.5t} \end{aligned}$$


$$(c) \quad v_c(t_0) = 144 \text{ V}.$$


$$e^{62.5t} = 181$$

$$62.5t = \ln 181$$

$$t = 83.04 \text{ ms}.$$

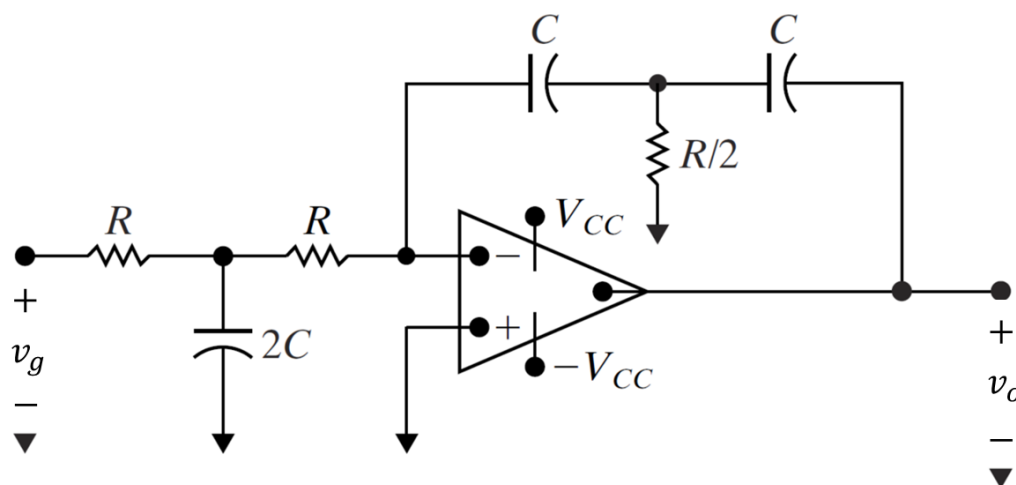6. Derive the differential equation that relates the output voltage to the input voltage for the circuit shown below. [20 points]



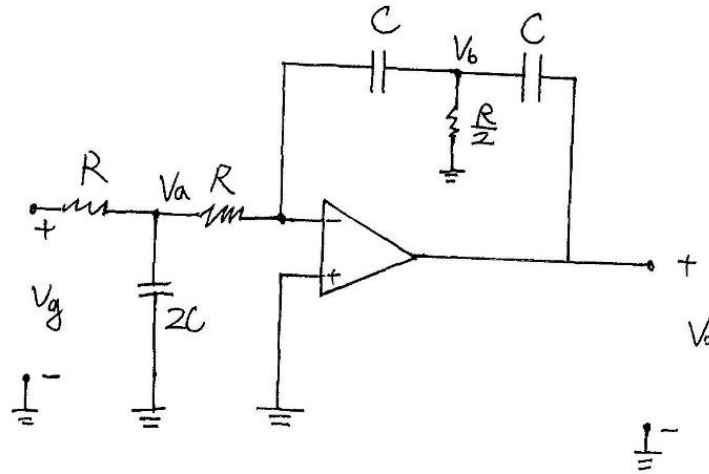

$$\frac{V_g - V_a}{R} = 2C \frac{dV_a}{dt} + \frac{V_a}{R} \quad \textcircled{1} \quad 3'$$

$$\frac{V_a}{R} = C \frac{d(-V_b)}{dt} \quad \textcircled{2} \quad 3'$$

$$C \frac{d(-V_b)}{dt} = \frac{V_b}{\frac{R}{2}} + C \frac{d(V_b - V_b)}{dt} \quad \textcircled{3} \quad 3'$$

$$\text{from } \textcircled{1}, V_g = 2RC \frac{dV_a}{dt} + 2V_a \quad \textcircled{4} \quad 2'$$

$$\text{from } \textcircled{2}, V_a = -RC \frac{dV_b}{dt} \quad \textcircled{5} \quad 2'$$

$$\text{from } \textcircled{3}, \frac{dV_b}{dt} = 2 \frac{dV_b}{dt} + \frac{2V_b}{RC} \Rightarrow \frac{d^2 V_b}{dt^2} = 2 \frac{d^2 V_b}{dt^2} + \frac{2dV_b}{dt} \frac{1}{RC} \quad 2'$$

$$\Rightarrow \frac{d^2 V_b}{dt^2} = -\frac{2}{RC} \frac{dV_a}{dt} + \frac{V_a}{-RC} \frac{2}{RC}$$

$$= -\frac{1}{(RC)^2} \left[2 \frac{dV_a}{dt} + 2V_a \right] \left[2RC \frac{dV_a}{dt} + 2V_a \right]$$

$$= -\frac{V_g}{R^2 C^2} \quad 5'$$

$$\Rightarrow \boxed{\frac{d^2 V_b}{dt^2} = -\frac{V_g}{R^2 C^2}}$$