

ECE2150J Homework 4

Deadline: 7th December 2024

Problem 1

- (a) (10%) Obtain the equivalent admittance Y_{in} of the circuit at $\omega = 100 \text{ rad/s}$.
- (b) (10%) Obtain the equivalent impedance Z_{in} of the circuit.
- (c) (10%) Obtain the equivalent impedance Z_{ab} of the circuit.

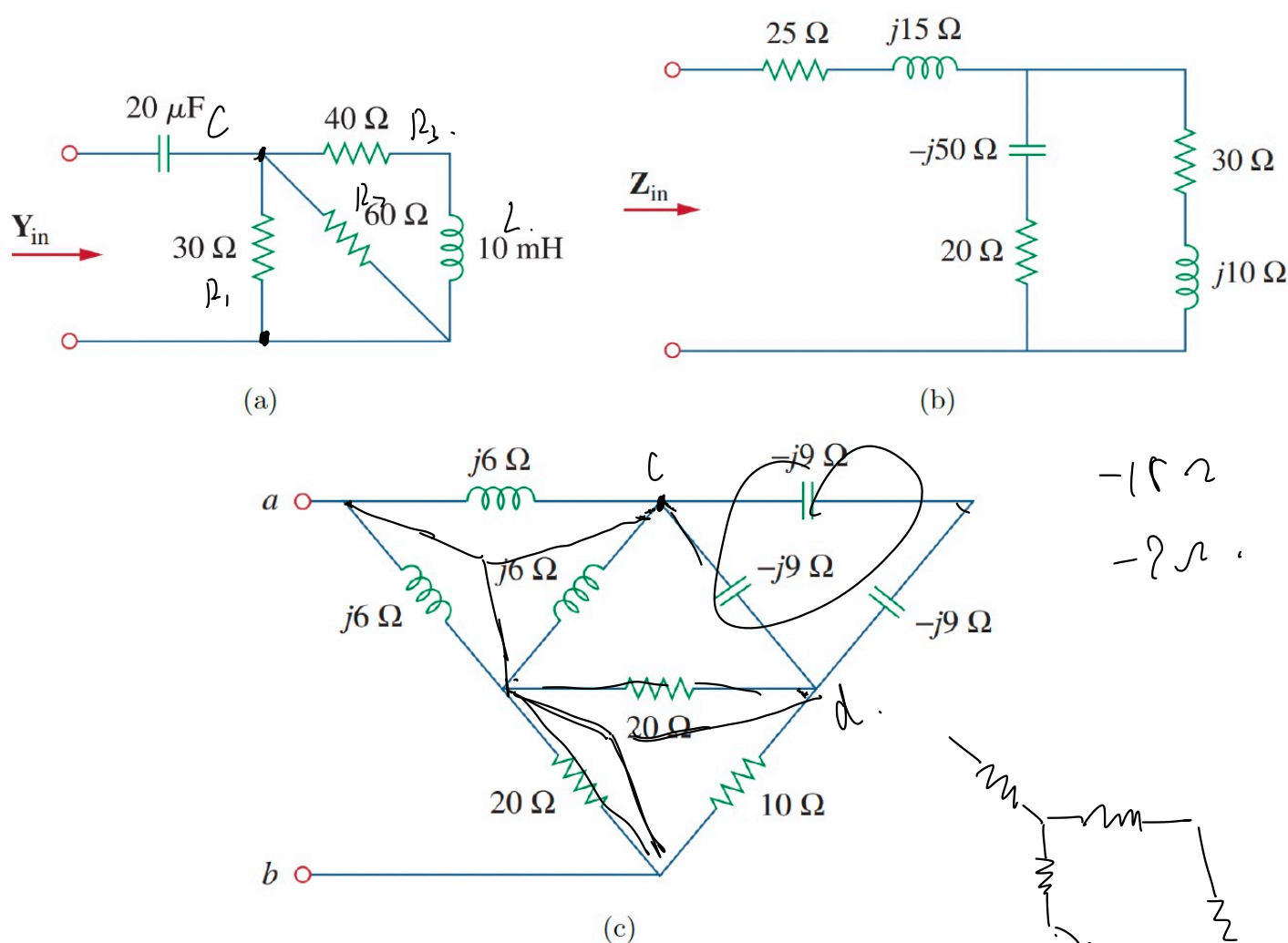


Figure 1: Circuit for Problem 1

(a)

$$C = \frac{1}{20 \times 10^{-6} \times 10^2 j} = -500 j \Omega.$$

$$L = 10 \times 10^3 \times 10^{-3} j = 10 j \Omega.$$


$$Z = -500 j + \frac{1}{\frac{1}{50} + \frac{1}{60} + \frac{1}{40 + j}} = 13.3 - 499.9 j \Omega.$$

$$Y = \frac{1}{Z} = 5.3 \times 10^{-3} + 2.0 \times 10^{-3} j \Omega.$$

(b) $Z = 25 + 15 j + \frac{1}{\frac{1}{20 - 50 j} + \frac{1}{20 + 10 j}}$

$$= 51.1 + 9.9 j \Omega.$$

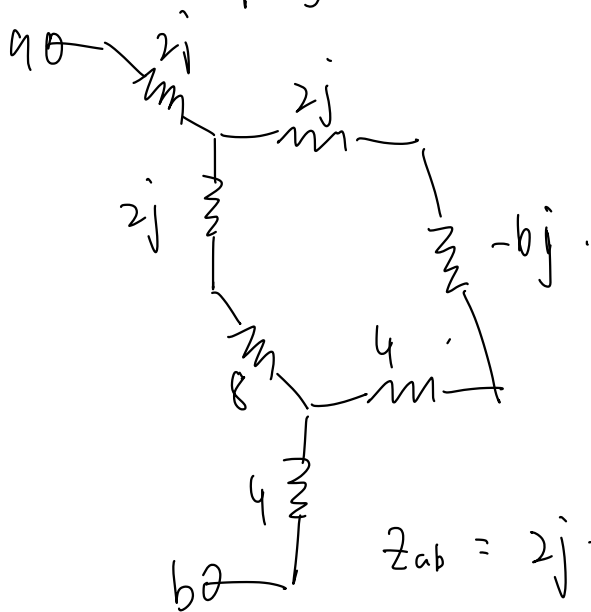(c) Apply Y- Δ , we can get the equivalent circuit.



$$Z_{ab} = 2j + \frac{1}{\frac{1}{8 + 2j} + \frac{1}{4 - 4j}} + 4 = (7.57 + 0.6j) \Omega.$$

Problem 2

- (a) (30%) Please find the Thevenin equivalent circuits between terminal a and b under $\omega = 2000 \text{ rad/s}$ and $\omega = 4000 \text{ rad/s}$.
- **Hint:** Consider whether to turn on or turn off the voltage source and current source based on the frequency you choose.
- (b) (10%) Please draw two phasor diagrams of the two Thevenin equivalent impedances under the two frequencies ($\omega = 2000 \text{ rad/s}$ and $\omega = 4000 \text{ rad/s}$).


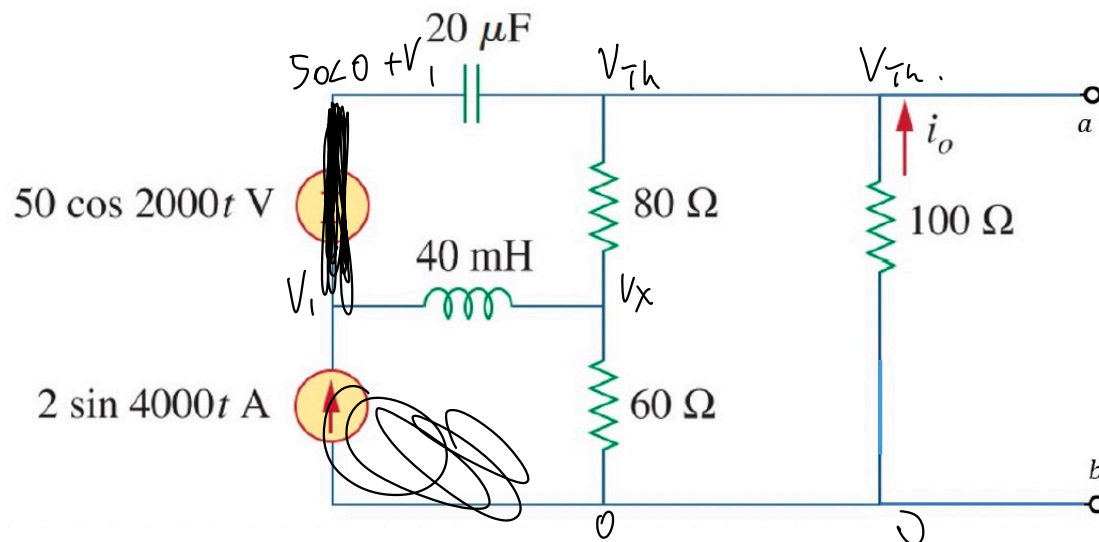


Figure 2: Circuit for Problem 2

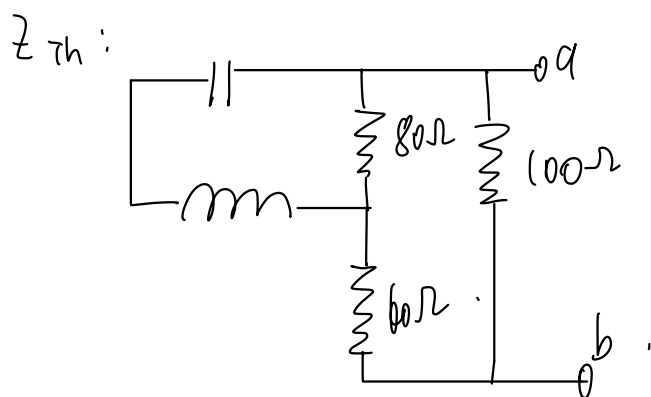

When $\omega = 2000$

$$C = 20 \times 10^{-6} \times 2 \times 10^3 \text{ j} = -25 \text{ j} \Omega$$

$$L = 40 \times 10^{-3} \times 2 \times 10^3 \text{ j} = 80 \text{ j} \Omega$$

$$Z_1 = \frac{1}{\frac{1}{80} + \frac{1}{80 \text{ j} - 25 \text{ j}}} = 25.67 + 37.35 \text{ j} \Omega$$

$$Z_{Th} = \frac{1}{\frac{1}{50} + \frac{1}{25.67 + 37.35 \text{ j}}} = 48.24 + 10.4 \text{ j} \Omega$$

$$\frac{V_x - V_1}{80 \text{ j}} + \frac{V_x}{60} + \frac{V_x - V_{Th}}{80} = 0$$

$$\frac{V_{Th} - 50 \angle 0^\circ - V_1}{-25 \text{ j}} + \frac{V_{Th} - V_x}{80} + \frac{V_{Th}}{100} = 0$$

$$\frac{V_1 - V_x}{80 \text{ j}} + \frac{V_1 + 50 \angle 0^\circ - V_{Th}}{-25 \text{ j}} = 0$$

$$V_{Th} = 21.75 \angle -45.9^\circ$$

$$V_{Th} = 21.75 \cos(2000t - 0.8)$$

when $\omega = 4000$.

$$C = -12.5j, L = 160j.$$

$$Z'_1 = \frac{1}{\frac{1}{80} + \frac{1}{160j - 12.5j}} = 61.8 + 33.5j.$$

$$Z_{Th} = \frac{1}{\frac{1}{100} + \frac{1}{61.8 + 33.5j + 60}} = 55.9 + 6.65j.$$

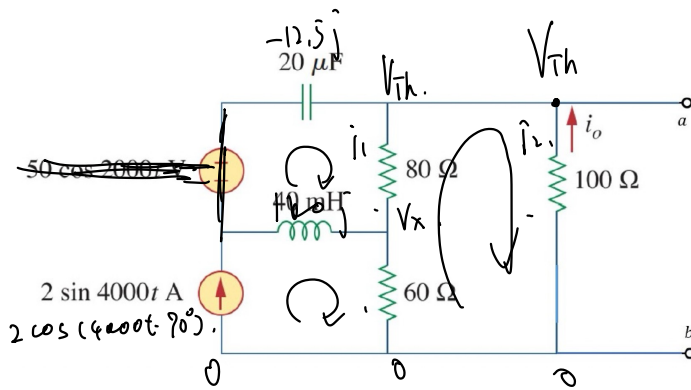


Figure 2: Circuit for Problem 2

$$\begin{cases} i_1(-12.5j) + (i_1 - i_2) \cdot 80 + (i_1 - 2 \angle -90^\circ) \cdot 160j = 0 \\ 80(i_2 - i_1) + 100i_2 + (i_2 - 2 \angle -90^\circ) \cdot 60 = 0 \end{cases}$$

$$(80 + 141.5j) i_1 - 80i_2 = 320$$

$$-80i_1 + 240i_2 = -120j$$

$$i_1 = 0.43 - 2j$$

$$i_2 = 0.15 - 1.17j$$

$$= 1.17 \angle -82.6^\circ$$

$$V_{Th} = 117 \cos(4000t - 1.44)$$

Problem 3

Given the circuit below, calculate the equivalent impedance in each of the blocks. Also find I_o and the overall complex power supplied.

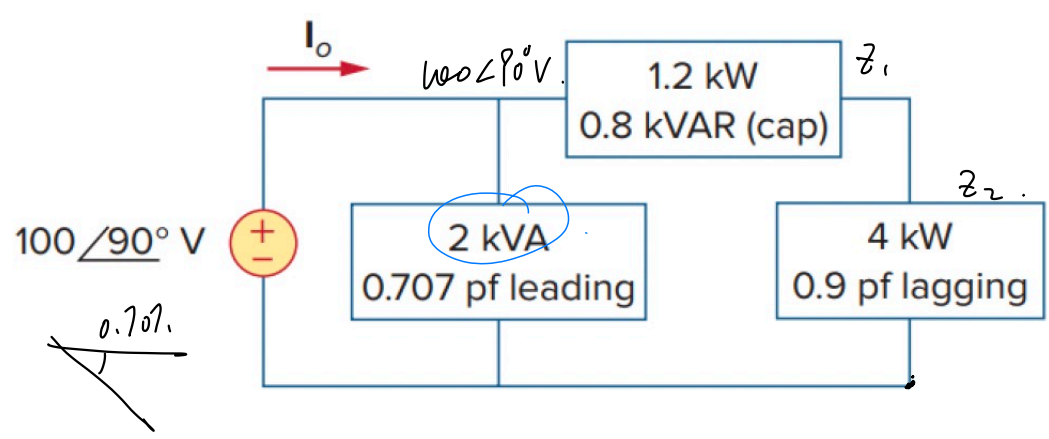


Figure 3: Circuit for Problem 3

Block 1.




$V_{rms} \cdot I_{rms}$
 $P = 1.414 \text{ kW}$
 $Q = -1.414 \text{ VAR}$
 $P = Q \Rightarrow \theta = 45^\circ$

$\tilde{V}_{rms} = 100 \angle 90^\circ$

$\tilde{I}_{rms}^* = \frac{S}{\tilde{V}_{rms}} = \frac{2 \text{ k} \angle -45^\circ}{100 \angle 90^\circ} = 20 \angle -135^\circ \text{ A}$


$Z = \frac{\tilde{V}_{rms}}{\tilde{I}_{rms}} = \frac{100 \angle 90^\circ}{20 \angle -135^\circ} = 5 \angle 45^\circ \Omega$

Block 2.

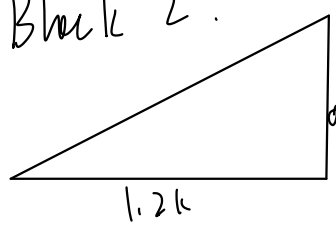

$I_{rms}^2 \cdot R_2 = 1.2 \text{ k}$
 $I_{rms}^2 \cdot X_2 = j0.8 \text{ k}$

Block 3

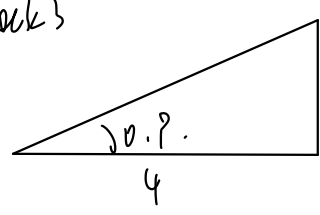

$I_{rms}^2 \cdot R_3 = 4 \text{ k}$
 $I_{rms}^2 \cdot X_3 = j1.94 \text{ k}$

$S = 5.2 \text{ k} + j2.74 \text{ k} = 5.9 \text{ k} \angle 27.8^\circ$

$\tilde{I}_{rms}^* = \frac{S}{\tilde{V}_{rms}} = \frac{5.9 \times 10^3 \angle 27.8^\circ}{100 \angle 90^\circ} = 59 \angle -62.2^\circ$

$\tilde{I}_{rms} = 59 \angle 62.2^\circ$

$$Z_{ms}^2 = 3481.$$

$$R_2 = 0.34 \Omega \quad X_2 = j 0.23 \Omega.$$

$$Z_2 = 0.41 \angle 34.0^\circ \Omega.$$

$$R_3 = 1.15 \Omega \quad X_3 = j 0.56 \Omega.$$

$$Z_3 = 1.28 \angle 25.9^\circ \Omega.$$

$$I_o: \quad \tilde{I}_{rms} + \tilde{I}_{Lrms} = 67.7 \angle 78.6^\circ A.$$

$$S = 1.614 + j1.33 \text{ (kVA)}.$$