
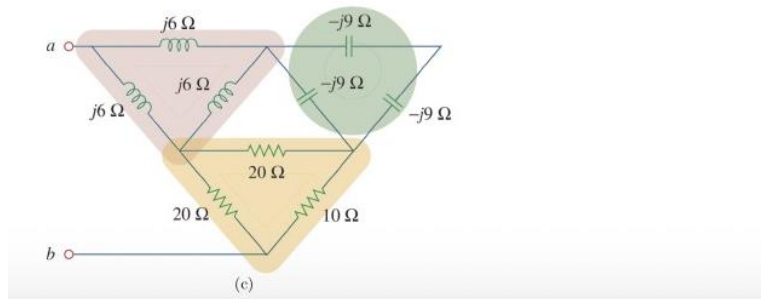
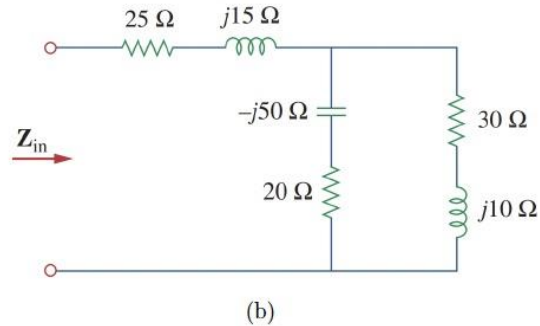


**Exercise 4.1 (30%)**

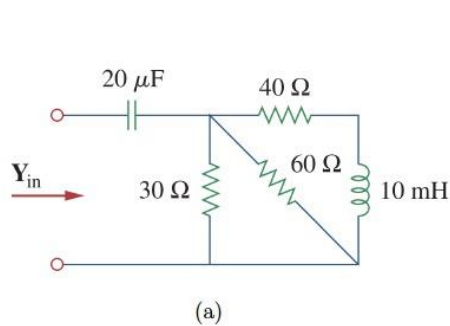- (a) (10%) Obtain the equivalent admittance  $Y_{in}$  of the circuit at  $\omega = 100 \text{ rad/s}$ .  
 (b) (10%) Obtain the equivalent impedance  $Z_{in}$  of the circuit.  
 (c) (10%) Obtain the equivalent impedance  $Z_{ab}$  of the circuit.



(a)

$$10 \text{ mH} \rightarrow j\omega L = j \times 100 \times (10 \times 10^{-3}) = j \quad (2')$$

$$20 \mu\text{F} \rightarrow \frac{1}{j\omega C} = \frac{1}{j \times 100 \times (20 \times 10^{-6})} = -500j \quad (2')$$

$$30 \parallel 60 = 20 \Omega$$

$$Z_{in} = -500j + 20 \parallel (40 + j) \quad (2')$$

$$= -500j + (13.36 + 0.11j)$$

$$= 13.36 - 499.89j \Omega \text{ (or } 500.07 \angle -88.47^\circ \Omega) \quad (2')$$


$$Y_{in} = \frac{1}{Z_{in}} = 5.33 \times 10^{-5} + 2.00 \times 10^{-3}j \text{ S (or } 2.00 \times 10^{-3} \angle 88.47^\circ) \quad (2')$$

(b)


$$Z_{in} = (20 + 15j) + (20 - 50j) \parallel (30 + 10j) \quad (3')$$

$$= (20 + 15j) + (26.10 - 5.12j) \quad (3')$$
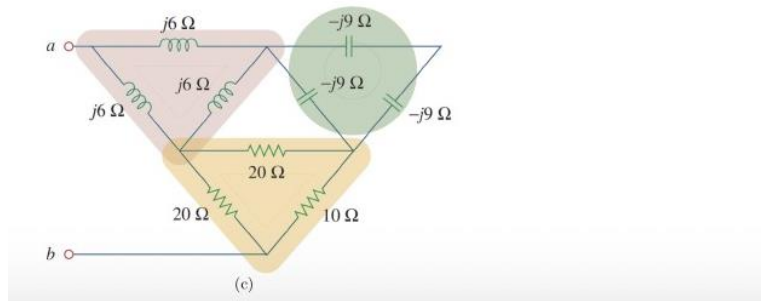
$$= 46.10 + 9.88j \, \Omega \quad (\text{or } 47.15 \angle 12.10^\circ \, \Omega) \quad (4')$$



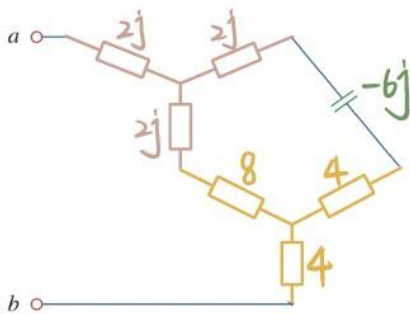$\nabla \rightarrow Y$   
 $\nabla \rightarrow Y$



$$(-9j - 9j) \parallel (-9j) = -6j$$

$$\frac{6j \times 6j}{6j + 6j + 6j} = 2j$$


$$\frac{20 \times 20}{20 + 20 + 10} = 8 \quad \frac{20 \times 10}{20 + 20 + 10} = 4$$

$$Z_{ab} = 2j + (2j - 6j + 4) \parallel (2j + 8) + 4$$

$$= 2j + (3.57 - 1.41j) + 4$$

$$= 7.57 + 0.59j \, \Omega \quad (\text{or } 7.59 \angle 4.49^\circ \, \Omega) \quad (10')$$

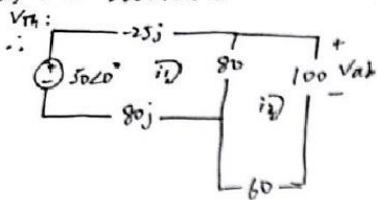(a)  $\omega = 2000 \text{ rad/s} \quad \therefore Z_C = -25j \Omega, Z_L = 80j \Omega \quad (2')$




$$\therefore \begin{cases} (80 + 55j)i_1 - 80j i_2 = 50 \angle 0^\circ \\ 240i_2 - 80i_1 = 0 \end{cases}$$


$$\therefore i_2 = \frac{320}{2113} - \frac{330}{2113}j = 0.1514 - 0.1562j = 0.2175 \angle -45.88^\circ$$

$$\therefore V_{ab} = 21.755 \angle -45.88^\circ \text{ V} = (15.174 - 15.618j) \text{ V} = V_{Th} \quad (10')$$

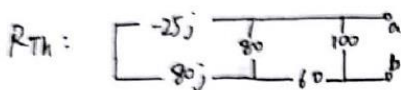
$$(V_{Th} = 21.755 \cos(2000t - 45.88^\circ) \text{ V 电压})$$


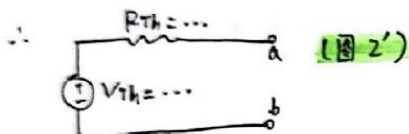
$$\therefore R_{Th} = 100 \parallel (60 + 80j/55j) = (48.237 + 10.4117j) \Omega \quad (3')$$



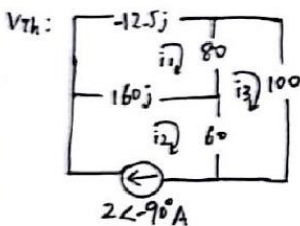$\omega = 4000 \text{ rad/s} \quad \therefore Z_C = -12.5j \Omega, Z_L = 160j \Omega \quad (2')$




$$\therefore \begin{cases} (80 + 147.5j)i_1 - 160j i_2 - 80i_3 = 0 \\ i_2 = 2 \angle -90^\circ \\ 240i_3 - 80i_1 - 60i_2 = 0 \end{cases}$$


$$\therefore i_3 = 1.178 \angle -82.62^\circ \text{ A} = (0.1513 - 1.1685j) \text{ A}$$


$$V_{Th} = V_{ab} = 100i_3 = 117.821 \angle -82.62^\circ \text{ V} = (15.13 - 116.85j) \text{ V} \quad (10')$$
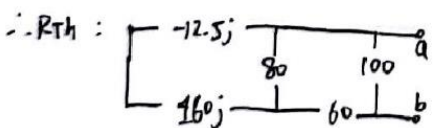
$$(V_{Th} = 117.821 \cos(4000t - 82.62^\circ) \text{ V 电压})$$


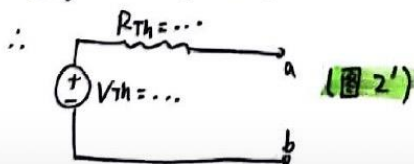
$$\therefore R_{Th} = 100 \parallel (60 + 80 \parallel 147.5j) = (55.9245 + 6.6620j) \Omega \quad (3')$$



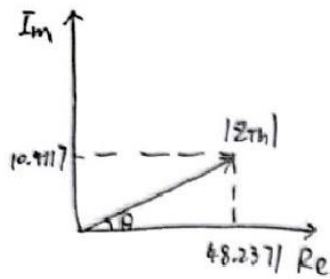

$$\therefore 1' \quad \omega = 2000 \text{ rad/s}$$

$$\therefore R_{Th} = (48.2371 + 10.4117j) \Omega (= 49.348 \angle 12.18^\circ)$$

$$\therefore |Z_{Th}| = 49.348 \Omega, \theta = 12.18^\circ$$

(同上 Re, Im 坐标 2x1')

$|Z_{Th}|$  值 1'

$\theta$  值 1'


同上有  $|Z_{Th}|$  和  $\theta$  标注 1'

$$2' \quad \omega = 4000 \text{ rad/s}$$

$$\therefore R_{Th} = (55.9245 + 6.6620j) \Omega (= 56.3199 \angle 6.79^\circ)$$


$$\therefore |Z_{Th}| = 56.3199 \Omega, \theta = 6.79^\circ$$

(同上)

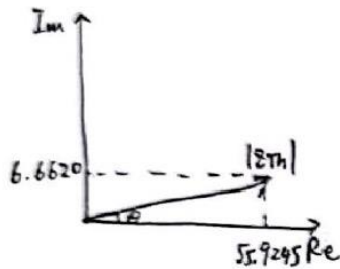

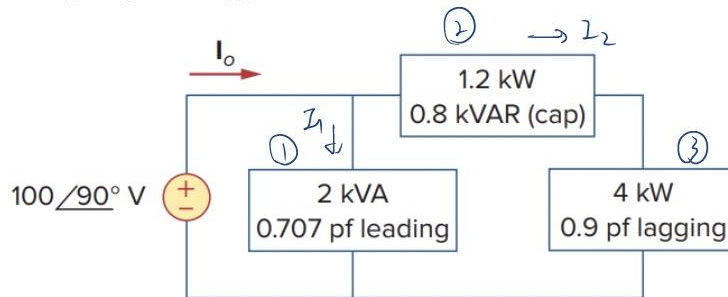**Exercise 6.3 (30%)**

Given the circuit below, calculate the equivalent impedance in each of the blocks. Also find  $I_o$  and the overall complex power supplied.



$$S_1 = 1.414 - 1.414j \text{ kVA} \quad (2')$$

$$S_2 = 1.2 - 0.8j \text{ kVA} \quad (2')$$

$$S_3 = 4 + j4 \tan(\cos^{-1}(0.9)) = 4 + 1.937j \text{ kVA} \quad (2')$$

$$I_1^* = \frac{S_1}{V} = \frac{1.414 - 1.414j \text{ k}}{j100} = -14.14 - 14.14j \text{ A} \Rightarrow I_1 = -14.14 + 14.14j \quad (2')$$

$$I_2^* = \frac{S_2 + S_3}{V} = 11.37 - 52j \text{ A} \Rightarrow I_2 = 11.37 + 52j \quad (2')$$

$$I_0 = I_1 + I_2 = -2.77 + 66.14j = 66.198 \angle 92.398 \text{ A} \quad (4')$$

$$S = S_1 + S_2 + S_3 = 6.614 - 0.277j \text{ kVA} \quad (4')$$

$$Z_1 = \frac{V}{I_1} = 3.54 - 3.54j = 5 \angle -45^\circ \Omega \quad (4')$$

$$Z_2 = \frac{S_2}{|I_2|^2} = 0.424 - 0.282j = 0.509 \angle -33.69^\circ \Omega \quad (4')$$

$$Z_3 = \frac{S_3}{|I_2|^2} = 1.412 + 0.684j = 1.569 \angle 25.839^\circ \Omega \quad (4')$$