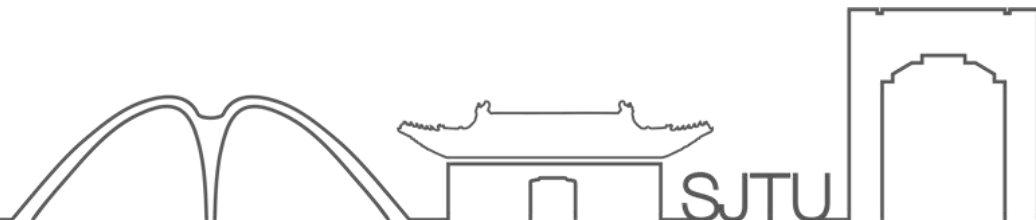




JOINT INSTITUTE
交大密西根学院

VE215 RC WEEK 10

Jiang Naicheng姜乃成
2024/11/6



Contents

Sinusoids and Phasors

Sinusoidal steady-state analysis



JOINT INSTITUTE
交大密西根学院

Alternating Current(AC) Circuits:

Circuits driven by sinusoidal current or voltage sources

$$v(t) = V_m \sin(\omega t + \phi)$$


where

V_m : amplitude

ω : angular frequency

ϕ : initial phase

Leads & Lags:

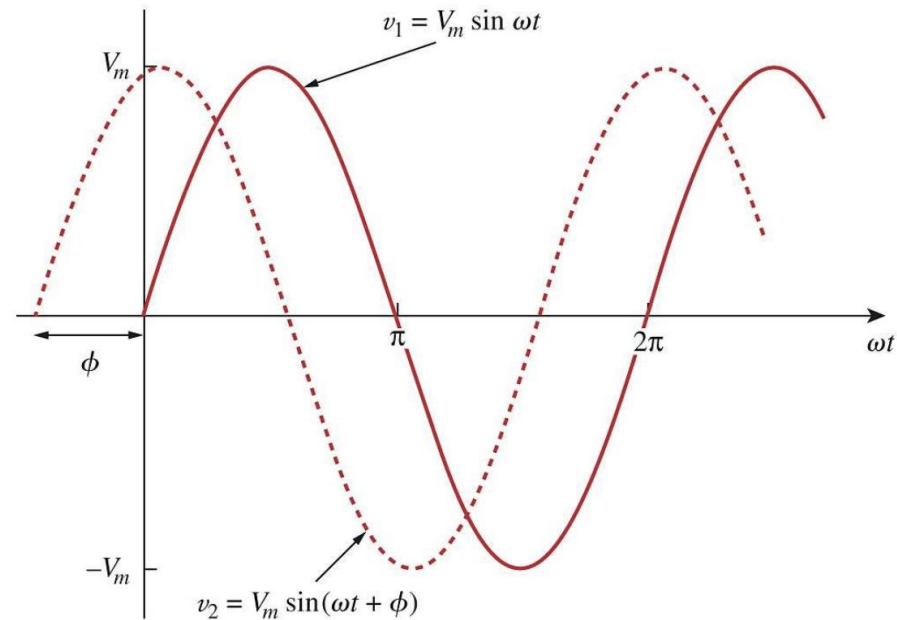

Phasors:

$$v(t) = V_m \cos(\omega t + \phi) = \text{Re}(\tilde{V} e^{j\omega t})$$

where

$$\tilde{V} = V_m e^{j\phi} = V_m \angle \phi$$

is the phasor representation of the sinusoidal signal

Phasor Diagram:

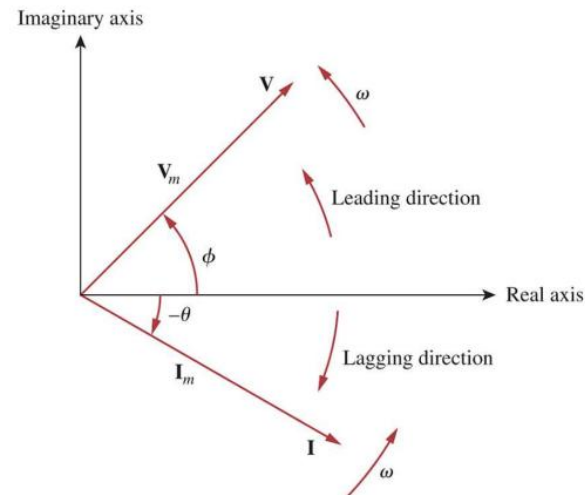


Figure 9.8 A phasor diagram.

$$v(t) = V_m \cos(\omega t + \phi) \Leftrightarrow \tilde{V} = V_m \angle \phi$$

TABLE 9.2

Summary of voltage - current relationships

Element	Time domain	Frequency domain
R	$v = Ri$	$\tilde{V} = R\tilde{I}$
L	$v = L \frac{di}{dt}$	$\tilde{V} = j\omega L\tilde{I}$
C	$i = C \frac{dv}{dt}$	$\tilde{V} = \frac{1}{j\omega C}\tilde{I}$

About admittance and impedance:

$$Y = \frac{\tilde{I}}{\tilde{V}} = \frac{1}{Z}$$

$$Z = R + jX = |Z| \angle \theta$$

where

R : resistance

X : reactance

If $X > 0$, we say that the impedance is inductive or lagging since current lags voltage; If $X < 0$, we say that the impedance is capacitive or leading because current leads voltage.

The impedance, resistance, and reactance are all measured in ohms.

TABLE 9.2

Summary of voltage - current relationships

Element	Time domain	Frequency domain
R	$v = Ri$	$\tilde{V} = R\tilde{I}$
L	$v = L \frac{di}{dt}$	$\tilde{V} = j\omega L\tilde{I}$
C	$i = C \frac{dv}{dt}$	$\tilde{V} = \frac{1}{j\omega C}\tilde{I}$

The admittance can be written as

$$Y = G + jB$$

where

G : conductance

B : susceptance

The admittance, conductance, and susceptance are all measured in siemens.

About admittance and impedance:

$$Y = \frac{\tilde{I}}{\tilde{V}} = \frac{1}{Z}$$

Equivalence Circuits

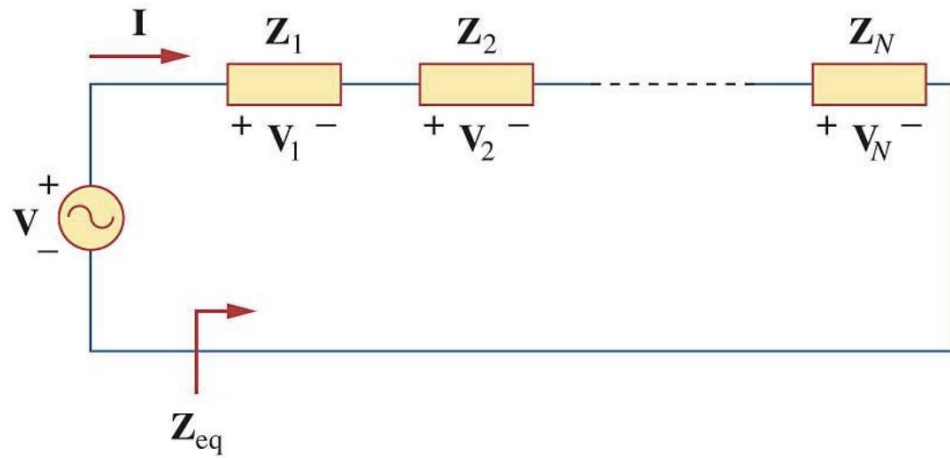


Figure 9.18 N impedances in series.

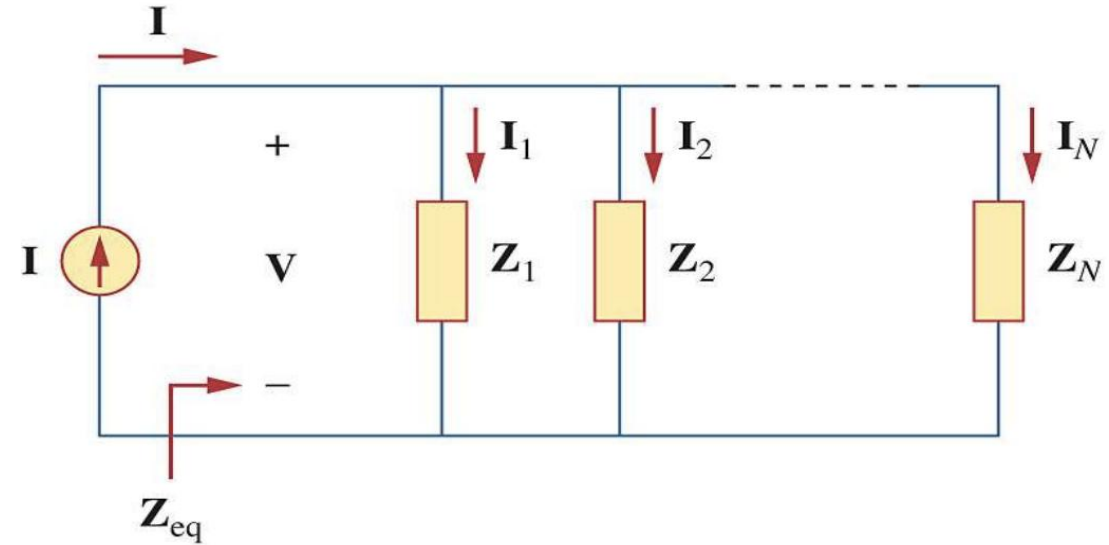


Figure 9.20 N impedances in parallel.


$$Z_{eq} = \frac{\tilde{V}}{\tilde{I}} = \frac{\overset{\text{KVL}}{\sum_{i=1}^N \tilde{V}_i}}{\tilde{I}} = \sum_{i=1}^N \frac{\tilde{V}_i}{\tilde{I}} = \sum_{i=1}^N Z_i$$

$$Y_{eq} = \frac{\tilde{I}}{\tilde{V}} = \frac{\overset{\text{KCL}}{\sum_{i=1}^N \tilde{I}_i}}{\tilde{V}} = \sum_{i=1}^N \frac{\tilde{I}_i}{\tilde{V}} = \sum_{i=1}^N Y_i$$

Exercise 1

9.23 Find the admittance Y_{ab} in the circuit seen in Fig. P9.23. Express Y_{ab} in both polar and rectangular form. Give the value of Y_{ab} in millisiemens.

Figure P9.23

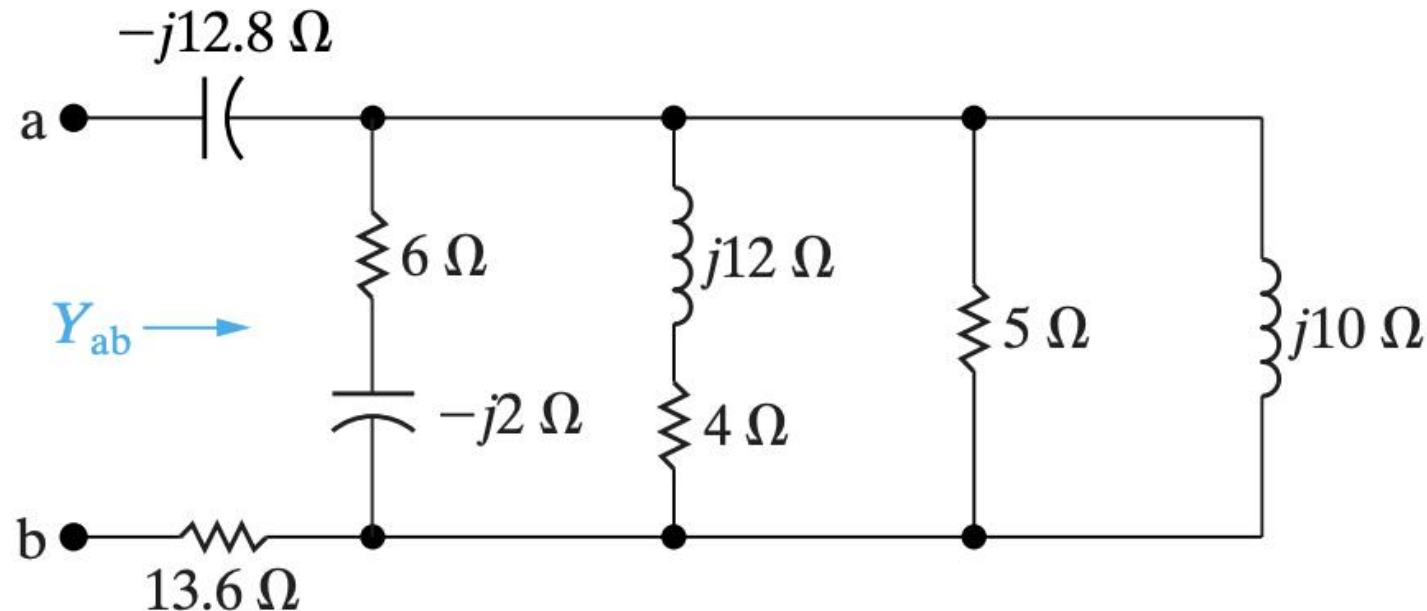

First, find the admittance of parallel branches

$$Y_P = \frac{1}{6-2j} + \frac{1}{4+12j} + \frac{1}{5} + \frac{1}{10j} = 0.375 - 0.125j \text{ (S)}$$

$$Z_P = \frac{1}{Y_P} = 2.4 + 0.8j \text{ (}\Omega\text{)}$$

$$Z_{ab} = Z_P - 12.8j + 13.6 = 16 - 12j \text{ (}\Omega\text{)}$$

$$Y_{ab} = \frac{1}{Z_{ab}} = [16 - 12j \text{ (}\Omega\text{)}]^{-1} = 0.04 + 0.03j \text{ (S)}$$

$$= 50 \angle 36.87^\circ \text{ (mS)}$$

be careful with units

Exercise 2

Suppose we have following elements: $600\ \Omega$ resistors, $0.1\mu\text{F}$ capacitances, 10mH inductances. Please use the above elements to create an impedance of $300 - 400j\ \Omega$ at a frequency of $10,000\text{ rad/s}$. The number of each elements is adequate.


$$R = 300 \Omega = \frac{600^2}{600+600} \Omega$$

$$\omega L - \frac{1}{\omega C} = 10000 L - \frac{1}{10^4 C} = -400$$

$$L = 10 \text{ mH}$$

$$\Rightarrow \frac{1}{10^4 C} = 100 + 400$$
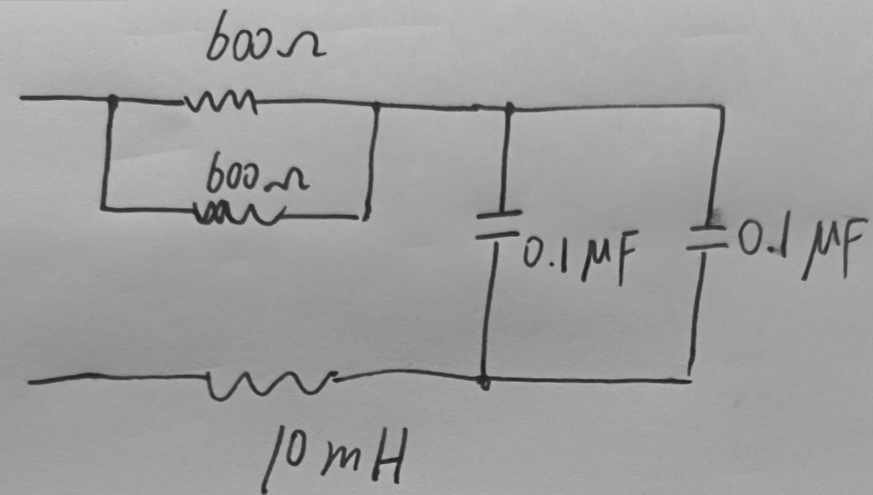
$$\Rightarrow C = 0.2 \mu\text{F}, \text{ two } 0.1 \mu\text{F} \text{ in parallel.}$$



Superposition in AC Circuits:

1. For DC voltage/current sources: take capacitance as an open and inductance as a short circuit.
2. For AC voltage/current sources: transform capacitance and inductance into impedance in frequency domain.
3. In AC circuit, when analyzing one specific source:
 - (1) Handle the capacitance and inductance following 1.&2. above, based on what type of the source is being analyzed.
 - (2) Then, take other voltage sources as a short circuit while other current sources as an open circuit.

Source Transformation and Equivalence Circuit:


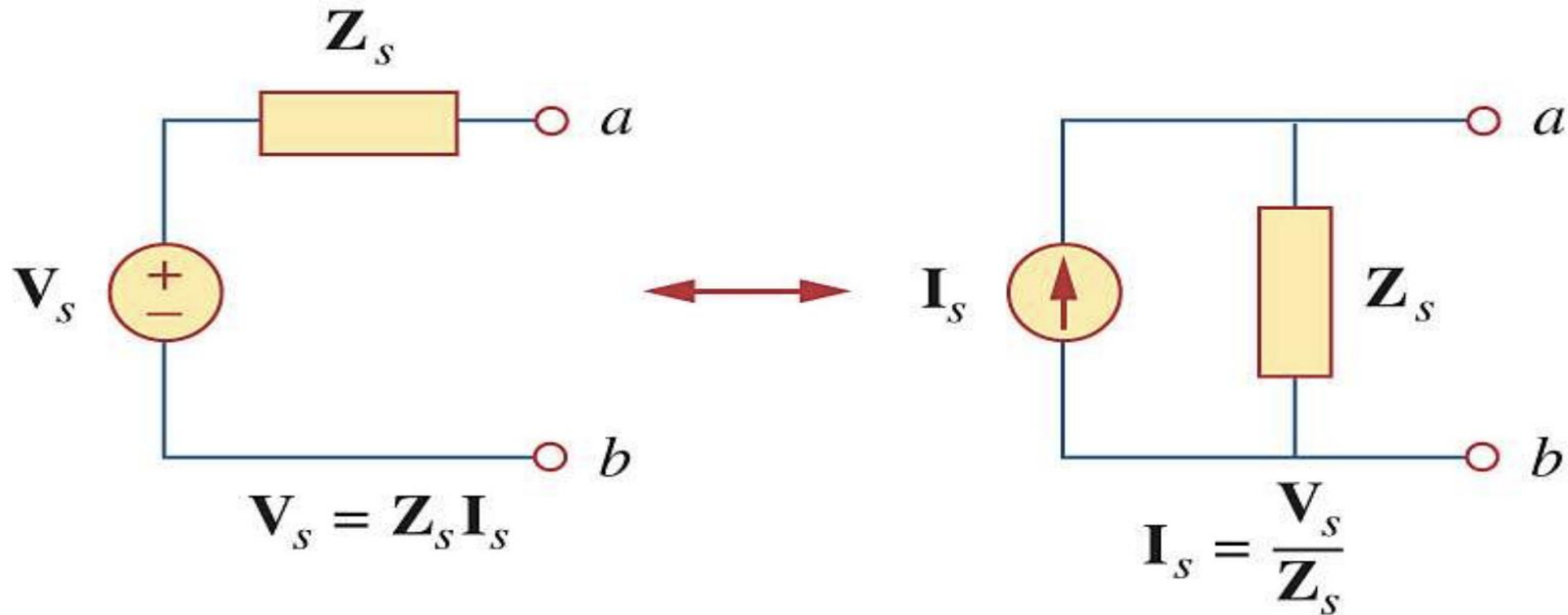


Figure 10.16 Source transformation.


Exercise 3

Find the Norton equivalent circuit with respect to the terminals a,b for the circuit shown in Fig. P9.50 when $\mathbf{V}_s = 5\angle 0^\circ \text{ V}$.

Figure P9.50

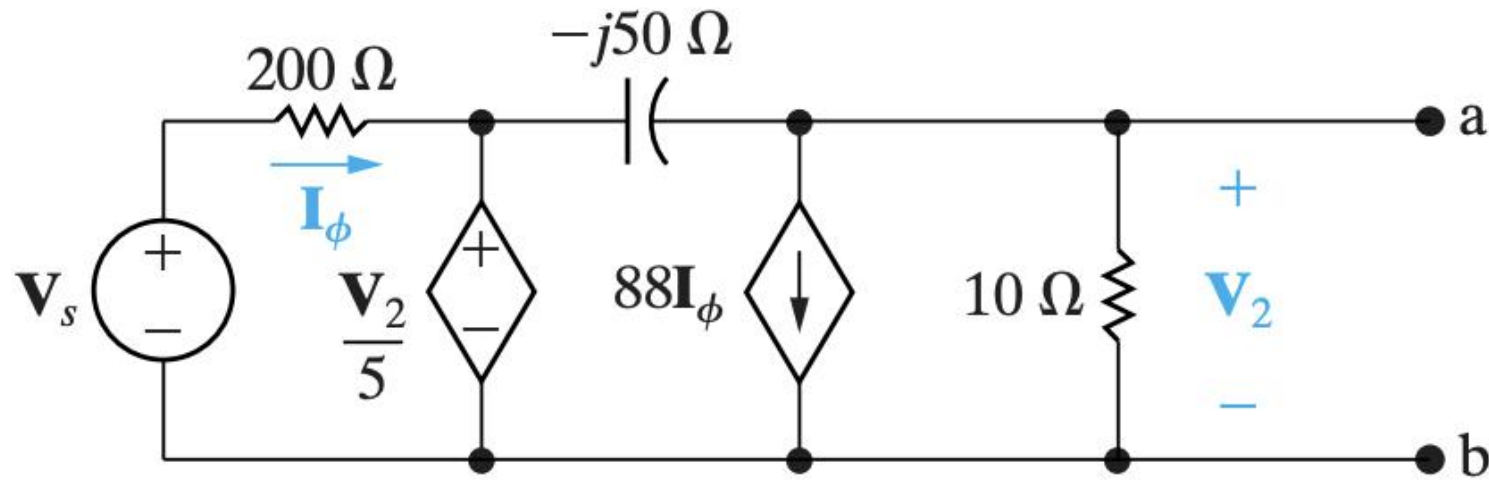

P 9.50 Open circuit voltage:

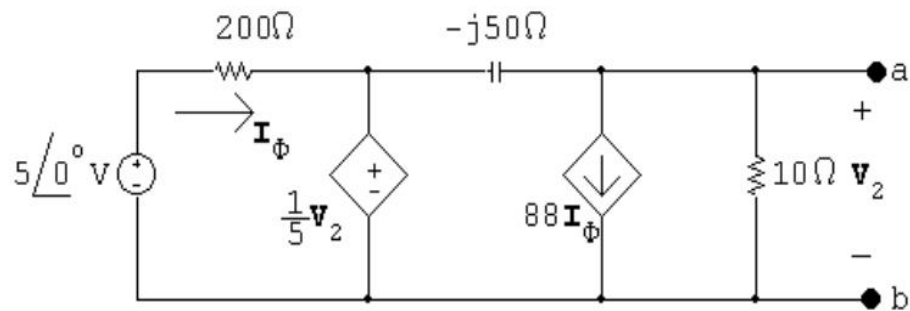


$$\frac{V_2}{10} + 88I_\phi + \frac{V_2 - \frac{1}{5}V_2}{-j50} = 0$$

$$I_\phi = \frac{5 - (V_2/5)}{200}$$

Solving,

$$V_2 = -66 + j88 = 110/\underline{126.87^\circ} \text{ V} = V_{\text{Th}}$$

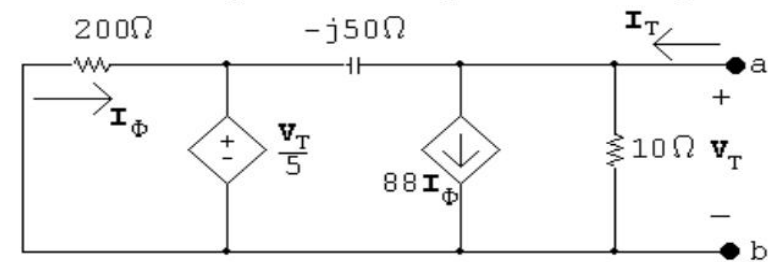Find the Thévenin equivalent impedance using a test source:



$$I_T = \frac{V_T}{10} + 88I_\phi + \frac{0.8V_T}{-j50}$$


$$I_\phi = \frac{-V_T/5}{200}$$

$$I_T = V_T \left(\frac{1}{10} - 88 \frac{V_T/5}{200} + \frac{0.8}{-j50} \right)$$

$$\therefore \frac{V_T}{I_T} = 30 - j40 = Z_{\text{Th}}$$

$$I_N = \frac{V_{\text{Th}}}{Z_{\text{Th}}} = \frac{-66 + j88}{30 - j40} = -2.2 + j0 \text{ A}$$

The Norton equivalent circuit:

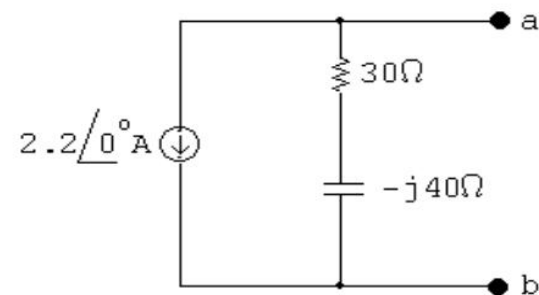


Exercise 4

10.48 Find i_o in the circuit of Fig. 10.93 using superposition.




ML

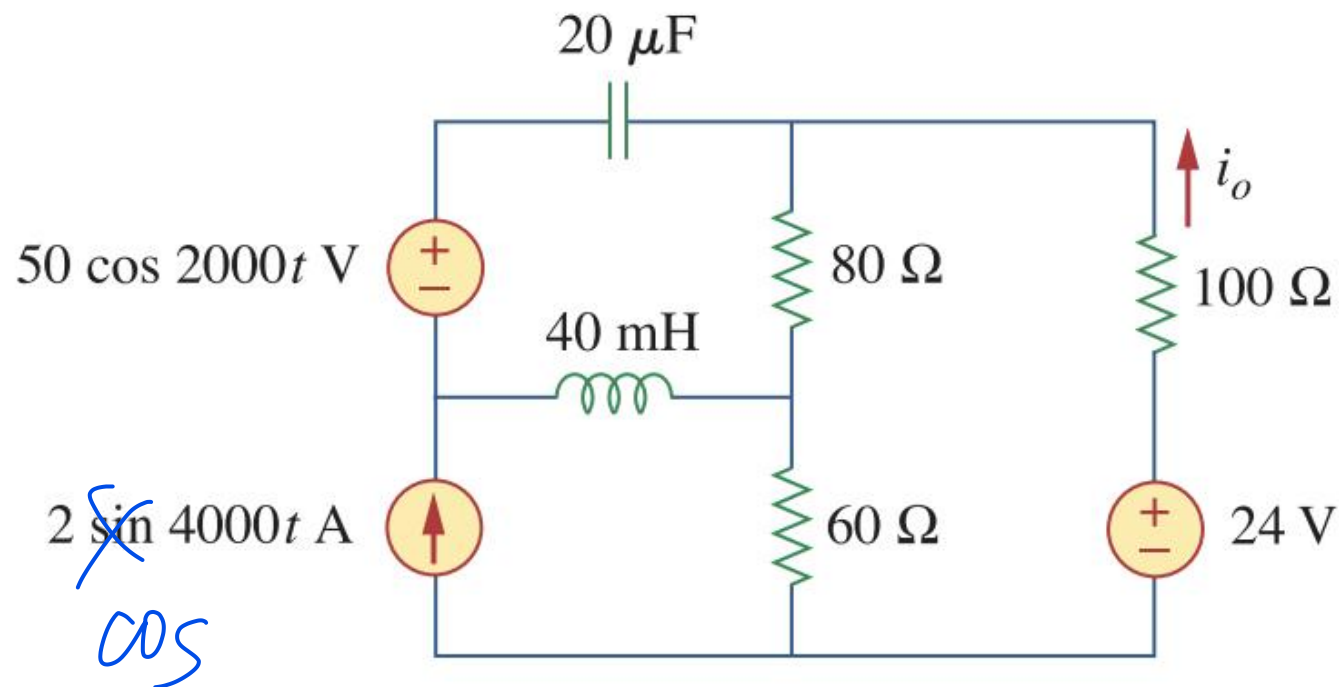

Chapter 10, Solution 48.

Let $i_o = i_{o1} + i_{o2} + i_{o3}$, where i_{o1} is due to the ac voltage source, i_{o2} is due to the dc voltage source, and i_{o3} is due to the ac current source. For i_{o1} , consider the circuit in Fig. (a).
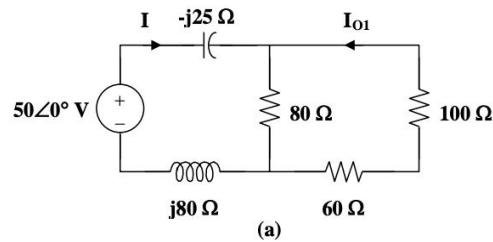
$$\begin{aligned}\omega &= 2000 \\ 50 \cos(2000t) &\longrightarrow 50 \angle 0^\circ \\ 40 \text{ mH} &\longrightarrow j\omega L = j(2000)(40 \times 10^{-3}) = j80 \\ 20 \text{ } \mu\text{F} &\longrightarrow \frac{1}{j\omega C} = \frac{1}{j(2000)(20 \times 10^{-6})} = -j25\end{aligned}$$




$$\begin{aligned}80 \parallel (60 + 100) &= 160/3 \\ \mathbf{I} &= \frac{50}{160/3 + j80 - j25} = \frac{30}{32 + j33}\end{aligned}$$

Using current division,

$$\begin{aligned}\mathbf{I}_{o1} &= \frac{-80\mathbf{I}}{80 + 160} = \frac{-1}{3}\mathbf{I} = \frac{10 \angle 180^\circ}{46 \angle 45.9^\circ} \\ \mathbf{I}_{o1} &= 0.217 \angle 134.1^\circ\end{aligned}$$

Hence, $i_{o1} = 0.217 \cos(2000t + 134.1^\circ) \text{ A}$

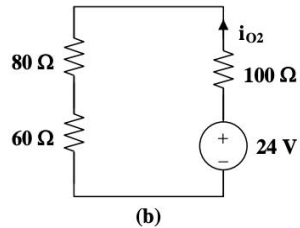
For i_{o2} , consider the circuit in Fig. (b).



$$i_{o2} = \frac{24}{80 + 60 + 100} = 0.1 \text{ A}$$

For i_{o3} , consider the circuit in Fig. (c).
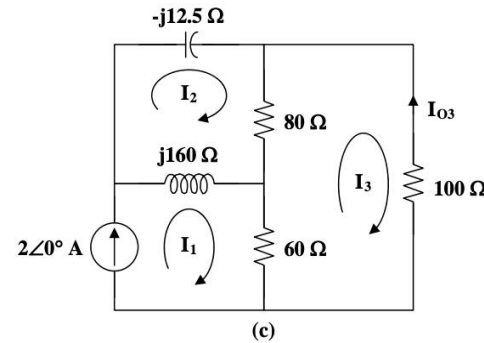
$$\begin{aligned}\omega &= 4000 \\ 2 \cos(4000t) &\longrightarrow 2 \angle 0^\circ \\ 40 \text{ mH} &\longrightarrow j\omega L = j(4000)(40 \times 10^{-3}) = j160 \\ 20 \text{ } \mu\text{F} &\longrightarrow \frac{1}{j\omega C} = \frac{1}{j(4000)(20 \times 10^{-6})} = -j12.5\end{aligned}$$



For mesh 1,

$$\mathbf{I}_1 = 2 \quad (1)$$

For mesh 2,

$$(80 + j160 - j12.5)\mathbf{I}_2 - j160\mathbf{I}_1 - 80\mathbf{I}_3 = 0$$

Simplifying and substituting (1) into this equation yields

$$(8 + j14.75)\mathbf{I}_2 - 8\mathbf{I}_3 = j32 \quad (2)$$

For mesh 3,

$$240\mathbf{I}_3 - 60\mathbf{I}_1 - 80\mathbf{I}_2 = 0$$

Simplifying and substituting (1) into this equation yields

$$\mathbf{I}_2 = 3\mathbf{I}_3 - 1.5 \quad (3)$$

Substituting (3) into (2) yields

$$\begin{aligned}(16 + j44.25)\mathbf{I}_3 &= 12 + j54.125 \\ \mathbf{I}_3 &= \frac{12 + j54.125}{16 + j44.25} = 1.1782 \angle 7.38^\circ\end{aligned}$$

Hence,

$$\begin{aligned}\mathbf{I}_{o3} &= -\mathbf{I}_3 = -1.1782 \angle 7.38^\circ \\ i_{o3} &= -1.1782 \sin(4000t + 7.38^\circ) \text{ A}\end{aligned}$$

Therefore,

$$i_o = \{0.1 + 0.217 \cos(2000t + 134.1^\circ) - 1.1782 \sin(4000t + 7.38^\circ)\} \text{ A}$$

Tips for this part:

1. Get familiar with basic concepts
2. Get familiar with your calculator

THANK YOU