

Due Date: 23:59, Oct.28th, 2024


In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated. This assignment covers content from chapter 1 to 3.

Exercise 1.1 (20%)

The current entering the positive terminal of a device is $i(t) = 2e^{-2t} \text{ mA}$ and the voltage across the device is $v(t) = 15 \frac{di}{dt} \text{ V}$.

- (a) Find the total charge in the device at $t = 3 \text{ s}$, $q(0)=0$.
- (b) Calculate the power absorbed $P(t)$.
- (c) Determine the total energy absorbed in 5s.


Exercise 1.2 (20%) Please find the voltage v_1 and v_2 in the circuit below by using delta-to-wye transformation.

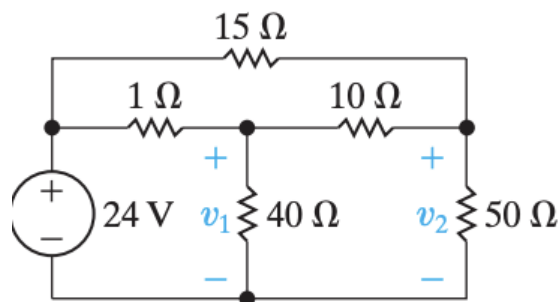

Exercise 1.3 (20%)


In the network graph below

- Determine the number of branches, nodes and meshes.
- Assuming all the resistor have the resistance of 5 ohm, calculate out v_{Δ} and i_{Δ}

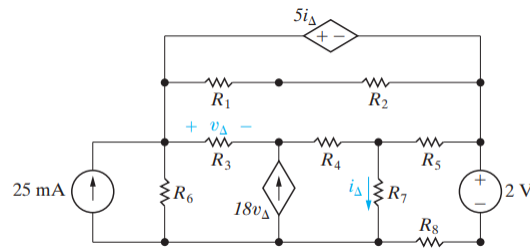


Exercise 1.4 (10+10%)

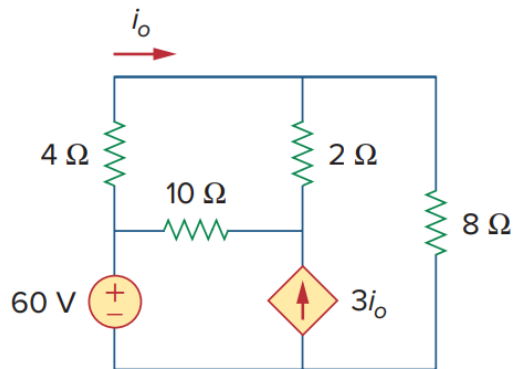(a) (10%) Using nodal analysis, find current i_o in the circuit below.




(b) (10%) Obtain the node voltages v_1 , v_2 , and v_3 in the circuit below.

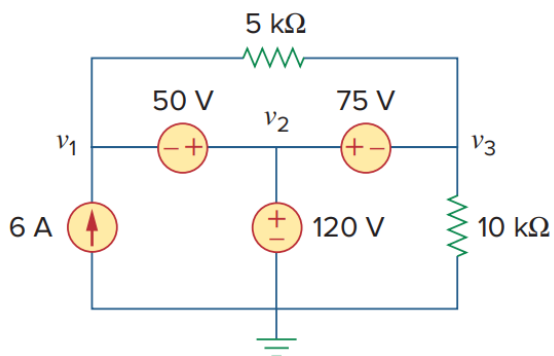

Exercise 1.5 (10+10%)

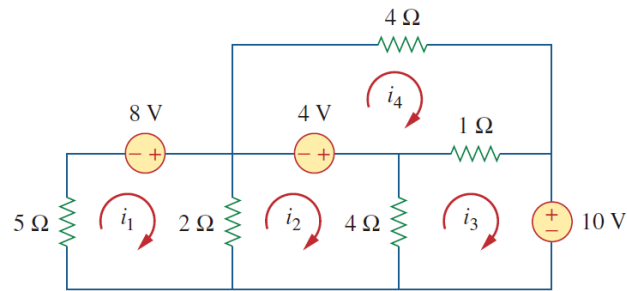(a) (10%) Use mesh analysis **by inspection** to find current i_1 , i_2 , i_3 and i_4 in the circuit below.



(b) (10%) Find current I_1 , I_2 and I_3 in the circuit below.

