

UM-SJTU JI 2024FA VE215 Lab #2

We will evaluate the Thevenin equivalent in this lab.

- Please hand in your post-lab assignment before the due date. Please do your post-lab assignment following the requirements in each problem. Both hand-written and printed are accepted.

- You are encouraged to print this lab manual and then finish the post-lab questions on it. For pictures or diagrams, you may print it in a paper, cut it down and paste on this worksheet.

Instruments

DC power supply

Multimeter


Breadboard and Wires

Resistors of 50Ω and 100Ω

Rheostat of 200Ω (or 500Ω)


Instruments Introduction

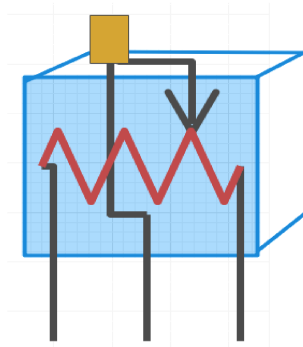For the **rheostats**, please connect the middle port and one of the sided ports inside the circuit (refer to the diagram). Please rotate the button at the top of rheostat using a mini-screwdriver to change its resistance.



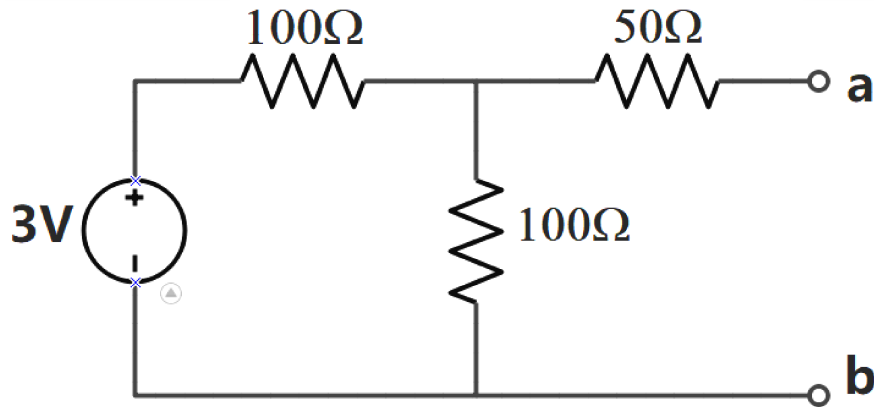Problem #1 Thevenin Equivalent

Please connect the circuit on your breadboard based on the schematic.



After the connection, please turn on the voltage source and measure the open-circuit voltage V_{ab} between port **a** and port **b** by multi-meter. Then, please turn off the voltage source and measure the equivalent resistance R_{ab} between port **a** and port **b** by multi-meter. Please record your data in the table:


Term	Open-circuit voltage V_{ab}	Equivalent resistance R_{ab}
Value		

Post-Lab Questions for (P1)

(1) Please calculate the theoretical values of the Thevenin's equivalent voltage and the equivalent resistance between port **a** and port **b**. Then, please compare the experimental values with the theoretical ones and explain how this experiment verifies the Thevenin theorem.

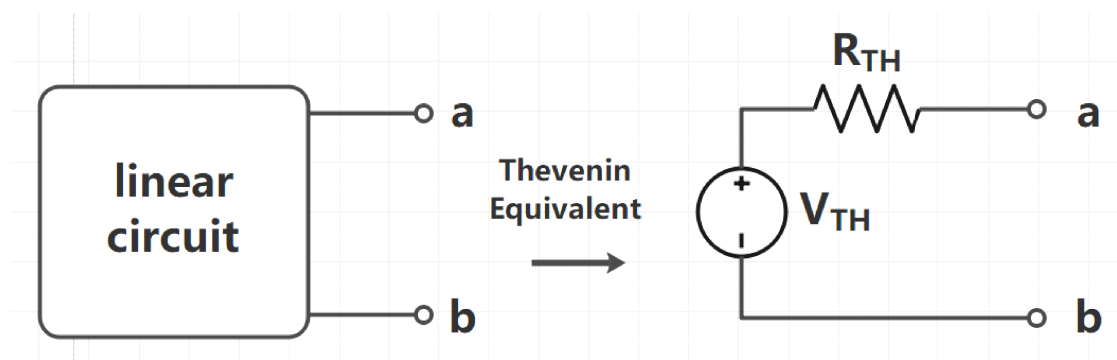Problem #2 Application of Thevenin Equivalent


Based on Thevenin theorem, most of linear circuits could be replaced by equivalent models composed of an equivalent voltage source V_{TH} connected in series with equivalent resistance R_{TH} , which is represented by the following diagram:




By adopting Thevenin transformation, the amount of calculation could be reduced significantly when analyzing complex circuits. For a linear

circuit, suppose the Thevenin equivalent voltage is V_{TH} and the equivalent resistance is R_{TH} . If we connect a load resistance R_L between the two reference ports (please refer to the following schematics), the load voltage V_L will be:
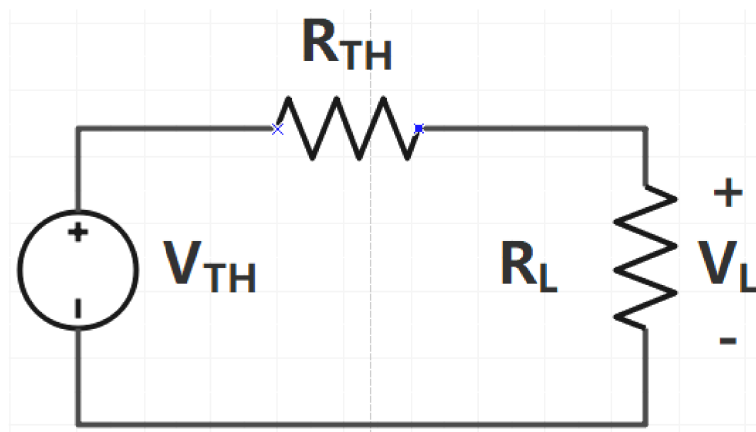
$$V_L = V_{TH} \frac{R_L}{R_L + R_{TH}}$$



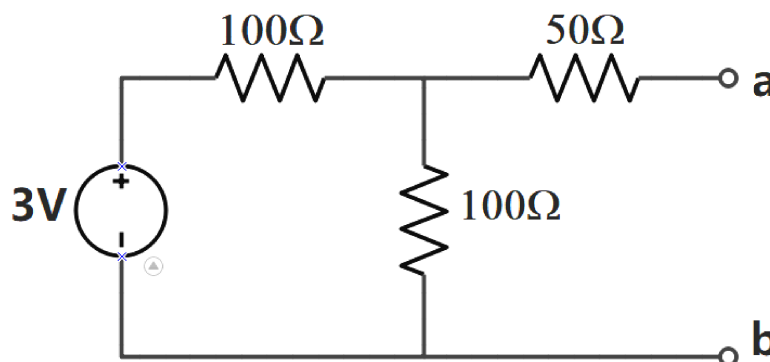Please connect a **50Ω** resistor and an **100Ω** resistor respectively between port **a** and port **b** as the load in the following circuit (same as the circuit in problem 1). Then, please turn on the source, measure the load voltage V_{ab} (the voltage between port **a** and port **b**) by multi-meter and fill in the table next page:



Load Resistance	50Ω	100Ω
V_{ab}		

Post-Lab Questions for (P2)



(1) Please calculate the theoretical values of the load voltage **V_{ab}** for the **50Ω** and **100Ω** loads. Then, please compare the experimental results with the theoretical ones.

Problem #3 Maximum Power Transfer

According to the maximum power transformation theorem, for a linear circuit with Thevenin voltage **V_{TH}** and equivalent resistance **R_{TH}**, the power transformed to the load will reaches its maximum if the load resistance **R_L = R_{TH}** and the maximum power absorbed by the load is:

$$P_{\max} = \frac{V_{\text{TH}}^2}{4R_{\text{TH}}}$$

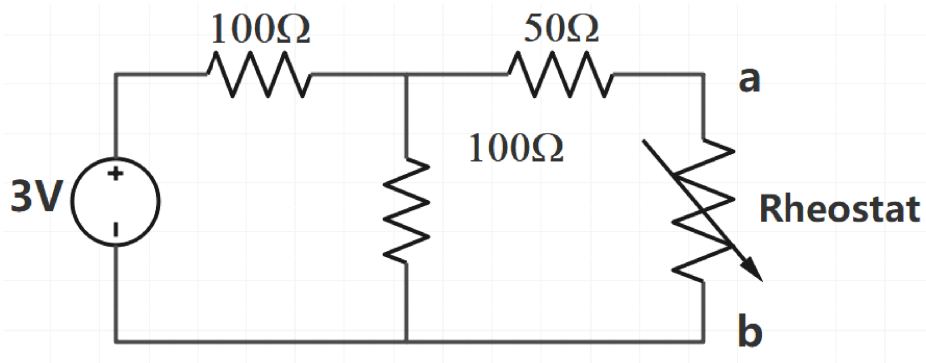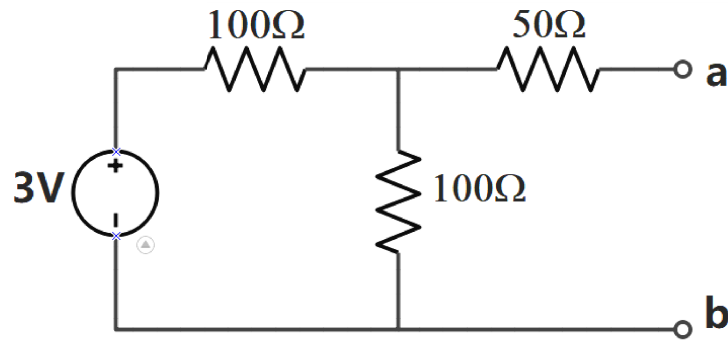In order to evaluate the maximum power transformation theorem, please connect a **200Ω** (or **500Ω**) rheostat between port **a** and port **b** in the schematic.



Please set your rheostat at its minimum resistance (about 0Ω) at first, use multi-meter to measure the load resistance (resistance of rheostat) R_L and the load voltage V_L . Then, please increase the resistance by 10Ω or 20Ω each time, measure R_L and V_L following the same procedure. Please record the data of R_L , V_L in the table and calculate the power transformed to the load P_L for each R_L .

Rheostat Resistance R_L	Load Voltage V_L	Power absorbed by load P_L
0Ω		

(2) Please plot the curve of P_L and R_L . What is the maximum power transferred to the load and the corresponding load resistance based on the curve you obtained? Is it consistent with the expected?