


### 3.1

(a) (4%)

$$i_o(0) = -i_1(0) - i_2(0) = 6 - 1 = 5 \text{ A}$$

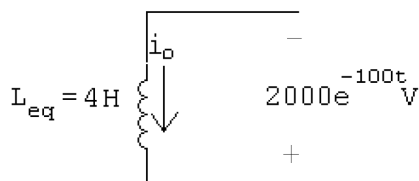(b) (4%) For the equivalent circuit with  $L_{eq} = 4 \text{ H}$ :

$$i_o = -\frac{1}{4} \int_0^t 2000e^{-100x} dx + 5 = 5(e^{-100t} - 1) + 5 = 5e^{-100t} \text{ A}, \quad t \geq 0$$



(c) (4%)


Using the values of  $v_a$  and  $v_c$ :

$$v_a = 3.2 \cdot (-500e^{-100t}) = -1600e^{-100t} \text{ V}$$

$$v_c = v_a + v_b = -1600e^{-100t} + 2000e^{-100t} = 400e^{-100t} \text{ V}$$

$$i_1 = \frac{1}{1} \int_0^t 400e^{-100x} dx - 6 = -4e^{-100t} + 4 - 6$$
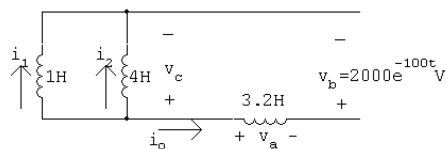
$$i_1 = -4e^{-100t} - 2 \text{ A}, \quad t \geq 0$$



(d) (4%)

$$i_2 = \frac{1}{4} \int_0^t 400e^{-100x} dx + 1 = -e^{-100t} + 2 \text{ A}, \quad t \geq 0$$

(e) (4%)

$$w(0) = \frac{1}{2}(1)(6)^2 + \frac{1}{2}(4)(1)^2 + \frac{1}{2}(3.2)(5)^2 = 60 \text{ J}$$

### 3.2

- (a) (6%) When the switch is in position A, the 5-ohm and 6-ohm resistors are short-circuited so that

$$i_1(0) = i_2(0) = v_o(0) = 0$$

but the current through the 4-H inductor is  $i_L(0) = \frac{30}{10} = 3 \text{ A}$ .

- (b) (8%) When the switch is in position B,

$$R_{Th} = \frac{3}{1+6} = 2 \Omega, \quad \tau = \frac{L}{R_{Th}} = \frac{4}{2} = 2 \text{ s}$$

$$i_L(t) = i_L(\infty) + [i_L(0) - i_L(\infty)] e^{-t/\tau} = 0 + 3e^{-t/2} = 3e^{-t/2} \text{ A}$$

- (c) (6%)


$$i_1(\infty) = \frac{30}{10+5} = 2 \text{ A}$$

$$i_2(\infty) = -\frac{3}{9}i_L(\infty) = 0 \text{ A}$$

$$v_o(\infty) = L \frac{di_L}{dt} \Rightarrow v_o(\infty) = 0 \text{ V}$$
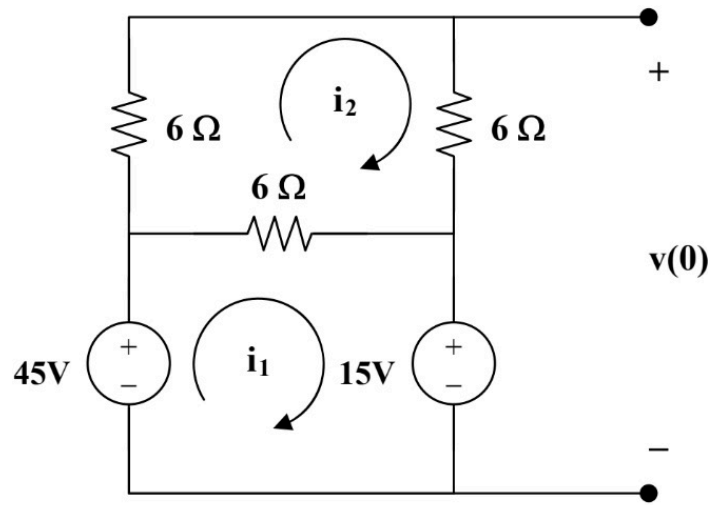
### 3.3

For  $t = 0^-$ , the equivalent circuit is shown below.



$$18i_2 - 6i_1 = 0 \text{ or } i_1 = 3i_2 \quad (1)$$

$$-45 + 6(i_1 - i_2) + 15 = 0 \text{ or } i_1 - i_2 = 30/6 = 5 \quad (2)$$

From (1) and (2),  $(2/3)i_1 = 5$  or  $i_1 = 7.5$  and  $i_2 = i_1 - 5 = 2.5$

$$i(0) = i_1 = 7.5\text{A}$$

$$-15 - 6i_2 + v(0) = 0$$

$$v(0) = 15 + 6 \times 2.5 = 30$$

For  $t > 0$ , we have a series RLC circuit.

$$R = 6 \parallel 12 = 4$$

$$\omega_o = 1/\sqrt{LC} = 1/\sqrt{(1/2)(1/8)} = 4$$

$$\alpha = R/(2L) = (4)/(2 \times (1/2)) = 4$$


$\alpha = \omega_o$ , therefore the circuit is critically damped

$$v(t) = V_s + [(A + Bt)e^{-4t}], \text{ and } V_s = 15$$

$$v(0) = 30 = 15 + A, \text{ or } A = 15$$

$$i_C = Cdv/dt = C[-4(15 + Bt)e^{-4t}] + C[(B)e^{-4t}]$$

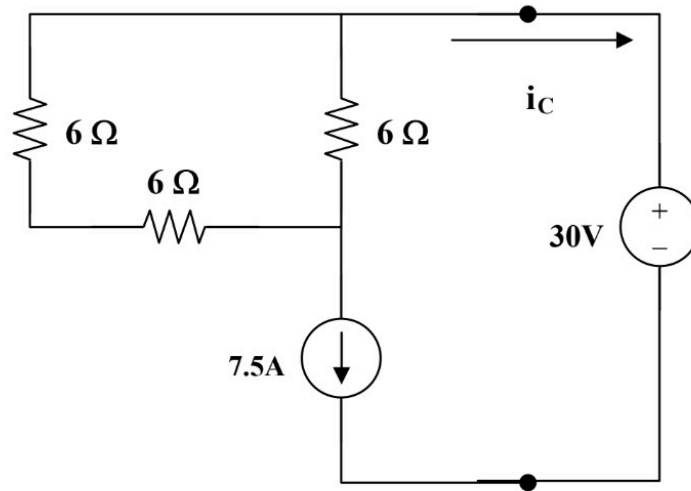To find  $i_C(0)$  we need to look at the circuit right after the switch is opened. At this time, the current through the inductor forces that part of the circuit to act like a current source and the capacitor acts like a voltage source. This produces the circuit shown below. Clearly,  $i_C(0+)$  must equal  $-i_L(0) = -7.5\text{A}$ .



$$i_C(0) = -7.5 = C(-60 + B) \text{ which leads to } -60 = -60 + B \text{ or } B = 0$$

$$i_C = Cdv/dt = (1/8)[-4(15 + 0t)e^{-4t}] + (1/8)[(0)e^{-4t}]$$

$$i_C(t) = [-(1/2)(15)e^{-4t}]$$

$$i(t) = -i_C(t) = \mathbf{7.5e^{-4t} \text{ A}}$$

### 3.4 Solution

At node 1,

$$\frac{v_{in} - v_1}{R_1} = C_1 \frac{d(v_1 - v_o)}{dt} + C_2 \frac{d(v_1 - 0)}{dt} \quad (1)$$


At node 2,

$$C_2 \frac{d(v_1 - 0)}{dt} = \frac{0 - v_o}{R_2}, \text{ or } \frac{dv_1}{dt} = \frac{-v_o}{C_2 R_2} \quad (2)$$

From (1) and (2),

$$v_{in} - v_1 = -\frac{R_1 C_1}{C_2 R_2} \frac{dv_o}{dt} - R_1 C_1 \frac{dv_o}{dt} - R_1 \frac{v_o}{R_2}$$
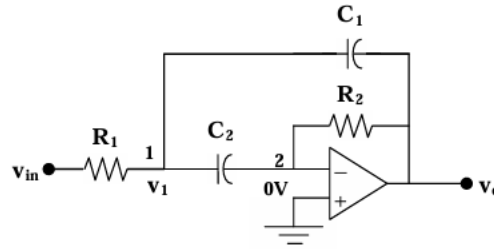
$$v_1 = v_{in} + \frac{R_1 C_1}{C_2 R_2} \frac{dv_o}{dt} + R_1 C_1 \frac{dv_o}{dt} + R_1 \frac{v_o}{R_2} \quad (3)$$



From (2) and (3),

$$-\frac{v_o}{C_2 R_2} = \frac{dv_1}{dt} = \frac{dv_{in}}{dt} + \frac{R_1 C_1}{C_2 R_2} \frac{dv_o}{dt} + R_1 C_1 \frac{d^2 v_o}{dt^2} + \frac{R_1}{R_2} \frac{dv_o}{dt}$$

$$\frac{d^2 v_o}{dt^2} + \frac{1}{R_2} \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \frac{dv_o}{dt} + \frac{v_o}{C_1 C_2 R_2 R_1} = -\frac{1}{R_1 C_1} \frac{dv_{in}}{dt}$$

$$\text{But } C_1 C_2 R_1 R_2 = 10^{-4} \times 10^{-4} \times 10^4 \times 10^4 = 1$$

$$\frac{1}{R_2} \left( \frac{1}{C_1} + \frac{1}{C_2} \right) = \frac{2}{R_2 C_1} = \frac{2}{10^4 \times 10^{-4}} = 2$$

$$\frac{d^2 v_o}{dt^2} + 2 \frac{dv_o}{dt} + v_o = -\frac{dv_{in}}{dt}$$

Which leads to  $s^2 + 2s + 1 = 0$  or  $(s + 1)^2 = 0$  and  $s = -1, -1$

$$\text{Therefore, } v_o(t) = [(A + Bt)e^{-t}] + V_f$$

As  $t$  approaches infinity, the capacitor acts like an open circuit so that

$$V_f = v_o(\infty) = 0$$

$v_{in} = 10u(t)$  mV and the fact that the initial voltages across each capacitor is 0

means that  $v_o(0) = 0$  which leads to  $A = 0$ .

$$v_o(t) = [Bte^{-t}]$$

$$\frac{dv_o}{dt} = [(B - Bt)e^{-t}] \quad (4)$$

From (2),

$$\frac{dv_o(0+)}{dt} = -\frac{v_o(0+)}{C_2 R_2} = 0$$


From (1) at  $t = 0+$ ,

$$\frac{1-0}{R_1} = -C_1 \frac{dv_o(0+)}{dt} \text{ which leads to } \frac{dv_o(0+)}{dt} = -\frac{1}{C_1 R_1} = -1$$

Substituting this into (4) gives  $B = -1$

$$\text{Thus, } v(t) = -te^{-t}u(t) \text{ V}$$

[a]

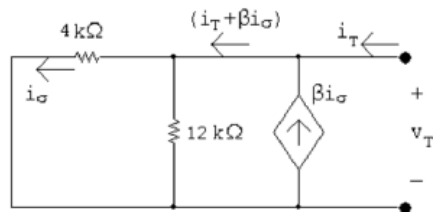

Using Ohm's law,

$$v_T = 4000i_\sigma$$

Using current division,

$$i_\sigma = \frac{12000}{12000 + 4000}(i_T + \beta i_\sigma) = 0.75i_T + 0.75\beta i_\sigma$$

Solve for  $i_\sigma$ :

$$i_\sigma(1 - 0.75\beta) = 0.75i_T$$


$$i_\sigma = \frac{0.75i_T}{1 - 0.75\beta}; \quad v_T = 4000i_\sigma = \frac{3000i_T}{1 - 0.75\beta}$$

Find  $\beta$  such that  $R_{Th} = -4k\Omega$ :

$$R_{Th} = \frac{v_T}{i_T} = \frac{3000}{1 - 0.75\beta} = -4000$$

$$1 - 0.75\beta = -0.75 \quad \beta = 2.33$$

[b] Find  $V_{Th}$ :

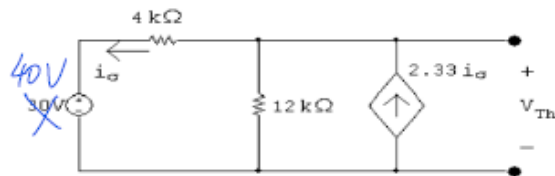

Write a KCL equation at the top node:

$$\frac{V_{Th} - 40}{4000} + \frac{V_{Th}}{12000} - 2.33i_\sigma = 0$$

The constraint equation is:

$$i_\sigma = \frac{V_{Th} - 40}{4000}$$

Solving,

$$V_{Th} = \frac{160}{3} \text{ V}$$

Write a KVL equation around the loop:

$$\frac{160}{3} = -4000i + 0.08 \frac{di}{dt}$$

Rearranging:

$$\frac{di}{dt} = \frac{2000}{3} + 50000i = 50000\left(i + \frac{1}{75}\right)$$

Separate the variables and integrate to find  $i$ :

$$\int \frac{di}{i + \frac{1}{75}} = \int 50000 dt$$

Thus,

$$i = -\frac{40}{3} + \frac{40}{3} e^{50000t} \text{ mA}$$

$$\frac{di}{dt} = \left(\frac{40}{3} \times 10^{-3}\right)(50000)e^{50000t} = \frac{2000}{3}e^{50000t}$$

Solve for the arc time:

$$v = 0.08 \frac{di}{dt} = \frac{160}{3} e^{50000t} = 30000; \quad e^{50000t} = 562.5$$

Thus,

$$t = \frac{\ln 562.5}{50000} = 126.6 \mu s$$