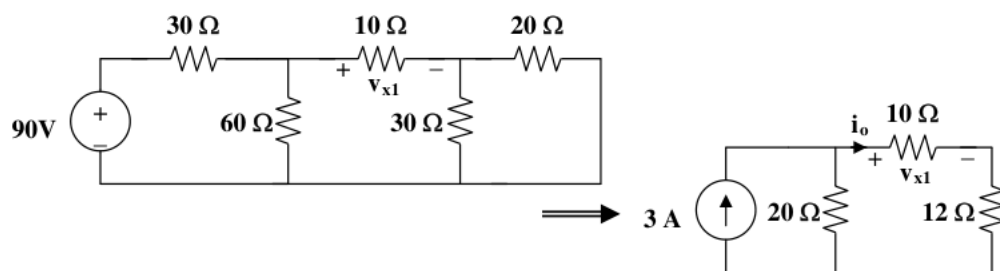


Problem 1:

Let $v_x = v_{x1} + v_{x2} + v_{x3}$, where v_{x1} , v_{x2} , and v_{x3} are due to the 90-V, 6-A, and 40-V sources. For v_{x1} , consider the circuit below.




$$20 \parallel 30 = 12 \text{ ohms}, 60 \parallel 30 = 20 \text{ ohms}$$

By using current division,


$$i_o = [20/(22 + 20)]3 = 60/42, v_{x1} = 10i_o = 600/42 = 14.286 \text{ V}$$

For v_{x2} , consider the circuit below.

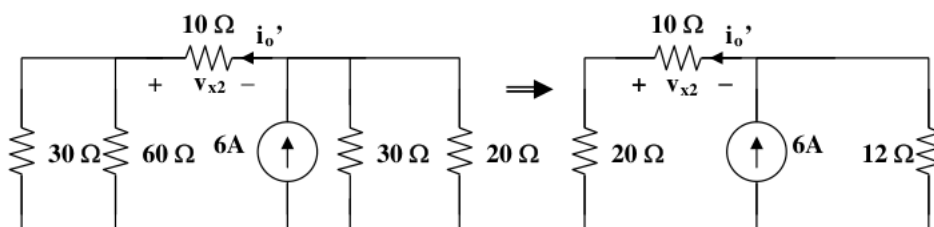

$$i_o' = [12/(12 + 30)]6 = 72/42, v_{x2} = -10i_o' = -17.143 \text{ V}$$


For v_{x3} , consider the circuit below.

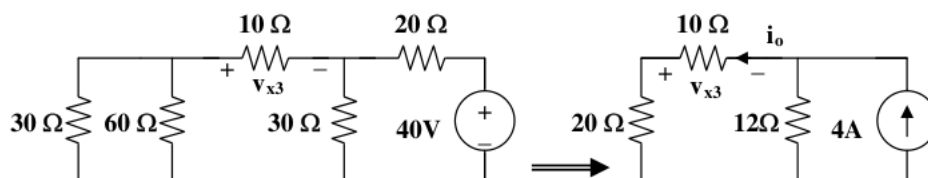


$$\begin{aligned} i_o'' &= [12/(12 + 30)]2 = 24/42, v_{x3} = -10i_o'' = -5.714 \\ v_{x3} &= -10i_o'' = -5.714 \\ &= [12/(12 + 30)]2 = 24/42, v_{x3} = -10i_o'' = -5.714 \\ v_x &= 14.286 - 17.143 - 5.714 = \mathbf{-8.571 \text{ V}} \end{aligned}$$

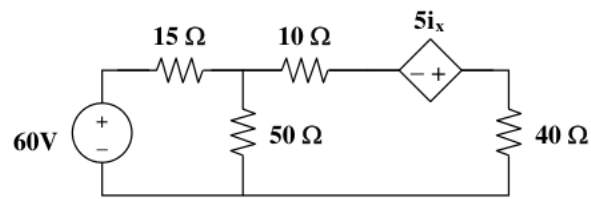Problem 2:


As shown in Fig. (a), we transform the dependent current source to a voltage source,



(a)

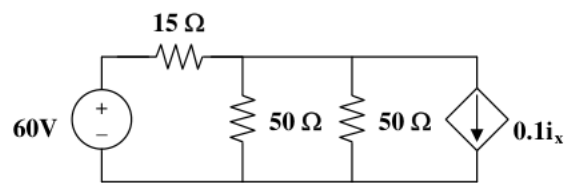

(b)

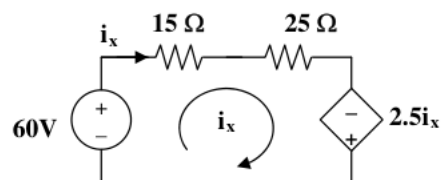


(c)

In Fig. (b), $50\parallel 50 = 25$ ohms. Applying KVL in Fig. (c),

$$-60 + 40i_x - 2.5i_x = 0, \text{ or } i_x = \mathbf{1.6 \text{ A}}$$

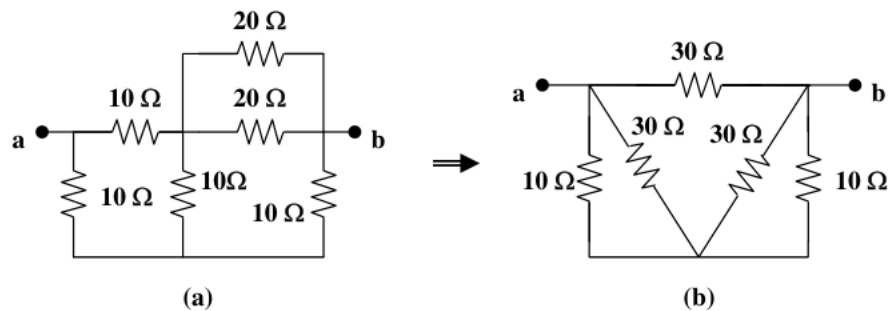
Problem3:

To find R_{Th} , consider the circuit in Fig. (a).



$20 \parallel 20 = 10$ ohms. Transform the wye sub-network to a delta as shown in Fig. (b).
 $10 \parallel 30 = 7.5$ ohms. $R_{Th} = R_{ab} = 30 \parallel (7.5 + 7.5) = 10$ ohms.

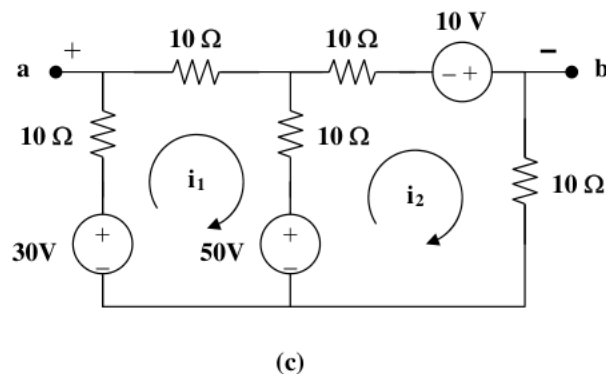To find V_{Th} , we transform the 20-V (to a current source in parallel with the 20Ω resistor and then back into a voltage source in series with the parallel combination of the two 20Ω resistors) and the 5-A sources. We obtain the circuit shown in Fig. (c).



For loop 1, $-30 + 50 + 30i_1 - 10i_2 = 0$, or $-2 = 3i_1 - i_2$ (1)

For loop 2, $-50 - 10 + 30i_2 - 10i_1 = 0$, or $6 = -i_1 + 3i_2$ (2)


Solving (1) and (2), $i_1 = 0$, $i_2 = 2$ A

Applying KVL to the output loop, $-v_{ab} - 10i_1 + 30 - 10i_2 = 0$, $v_{ab} = 10$ V

$V_{Th} = v_{ab} = 10$ volts

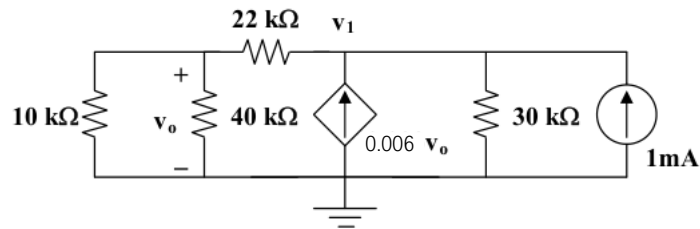Problem4:

We need the Thevenin equivalent across the resistor R. To find R_{Th} , consider the circuit below.



Assume that all resistances are in k ohms and all currents are in mA.

$$10 \parallel 40 = 8, \text{ and } 8 + 22 = 30$$

$$1 + 6 v_o = (v_1/30) + (v_1/30) = (v_1/15)$$

$$15 + 90 v_o = v_1$$

But $v_o = (8/30)v_1$, hence,


$$15 + 90 \times (8v_1/30) = v_1, \text{ which leads to } v_1 = -0.65217$$

$$R_{Th} = v_1/1 = -652.17 \text{ ohms}$$

R_{Th} being negative indicates an active circuit and if you now make R equal to $1.3636 \text{ k}\Omega$, then the active circuit will actually try to supply infinite power to the resistor. The correct answer is therefore:

$$p_R = \left(\frac{V_{Th}}{-652.17 + 652.17} \right)^2 = \left(\frac{V_{Th}}{0} \right)^2 = \infty$$

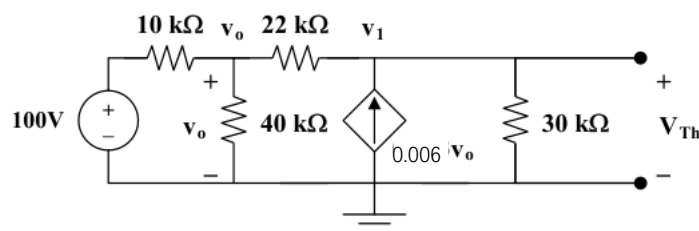It may still be instructive to find V_{Th} . Consider the circuit below.




$$(100 - v_o)/10 = (v_o/40) + (v_o - v_1)/22 \quad (1)$$

$$[(v_o - v_1)/22] + 6 v_o = (v_1/30) \quad (2)$$

Solving (1) and (2),

$$v_1 = V_{Th} = -231.30 \text{ volts}$$

Problem5:

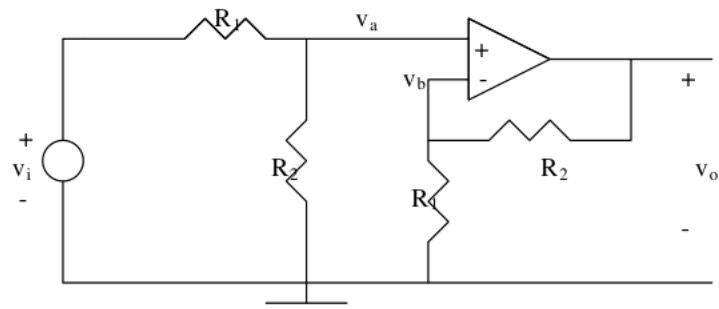


$$v_a = \frac{R_2}{R_1 + R_2} v_i, \quad v_b = \frac{R_1}{R_1 + R_2} v_o$$

But $v_a = v_b \longrightarrow \frac{R_2}{R_1 + R_2} v_i = \frac{R_1}{R_1 + R_2} v_o$

Or

$$\frac{v_o}{v_i} = \frac{R_2}{R_1}$$

Problem6:

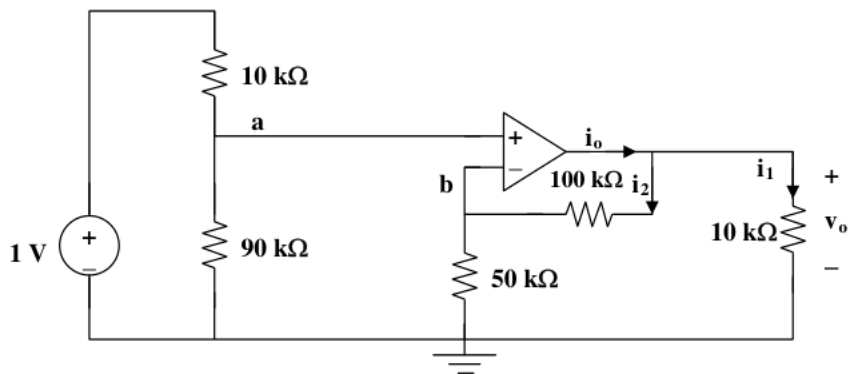

By voltage division,

$$v_a = \frac{90}{100} (1) = 0.9V$$

$$v_b = \frac{50}{150} v_o = \frac{v_o}{3}$$

But $v_a = v_b \longrightarrow \frac{v_o}{3} = 0.9 \longrightarrow v_o = 2.7V$

$$i_o = i_1 + i_2 = \frac{v_o}{10k} + \frac{v_o}{150k} = 0.27mA + 0.018mA = 288 \mu A$$