


2. Please analyze an **ideal transformer** circuit below. Assume all values in the question below are **RMS** values. [Total 16 points]

(1) Transform the circuit below to the phasor domain, e.g.  $L \rightarrow j\omega L$ . [2 points]

(2) Please assign currents at the transformer terminals (any direction as you prefer).

Determine polarities of turn ratio  $n$  of both voltage and current. [2 points]

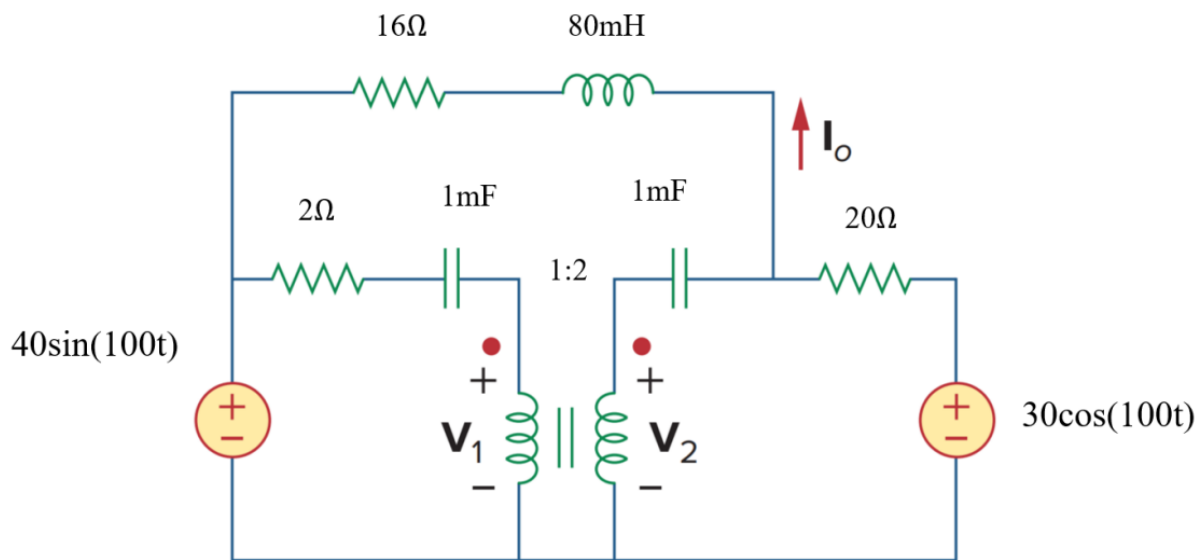(3) Please get values for  $V_1$ ,  $V_2$  and  $I_o$  respectively in the circuit. [12 points]




2. Please analyze an **ideal transformer** circuit below. Assume all values in the question below are **RMS** values. [Total 16 points]

(1) Transform the circuit below to the phasor domain, e.g.  $L \rightarrow j\omega L$ . [2 points]

(2) Please assign currents at the transformer terminals (any direction as you prefer).

Determine polarities of turn ratio  $n$  of both voltage and current. [2 points]

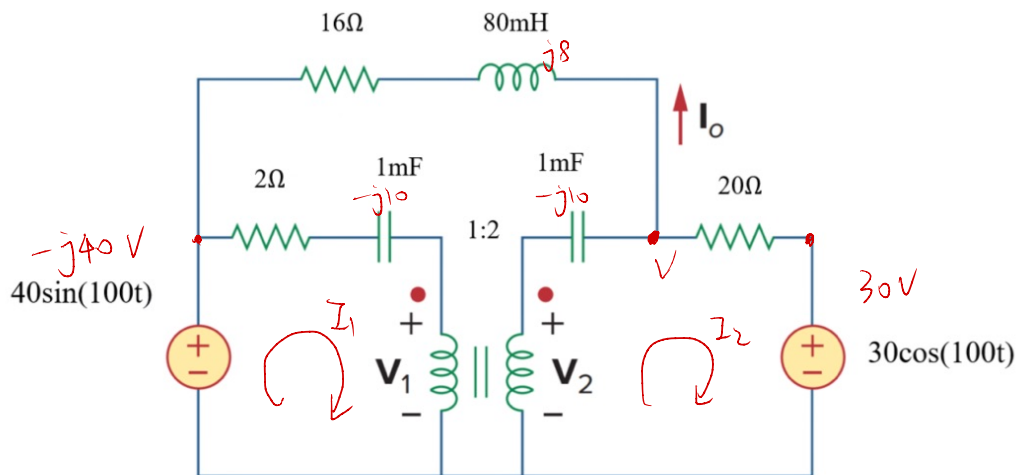(3) Please get values for  $V_1$ ,  $V_2$  and  $I_o$  respectively in the circuit. [12 points]



(1)  $\omega = 100$

$80\text{mH} \rightarrow j8 \Omega$  (1')

$1\text{mF} \rightarrow -j10 \Omega$  (1')

(2)  $\frac{V_1}{V_2} = \frac{1}{2}$  (1')

$\frac{I_1}{I_2} = \frac{2}{1}$  (depending on the assigned direction) (1')

(3)  $I_1 = \frac{-j40 - V_1}{2 - j10}$  (2')

$I_2 = \frac{V_2 - V}{-j10}$  (2')

$\frac{I_1}{I_2} = 2, \frac{V_1}{V_2} = \frac{1}{2}$

$\frac{V - V_2}{-j10} + \frac{V + j40}{16 + j8} + \frac{V - 30}{20} = 0$  (2')

$I_o = \frac{V + j40}{16 + j8}$  (2')

Any other partial procedure (1')


$\Rightarrow \begin{cases} V_1 = 7.56 - 15.80j \text{ V} & (1') \\ = 17.52 \angle -64.43^\circ \text{ V} & \checkmark \\ V_2 = 15.12 - 31.60j \text{ V} & (1') \\ = 35.03 \angle -64.43^\circ \text{ V} & \checkmark \\ I_o = 1.54 + 0.44j \text{ A} & (1') \\ = 1.60 \angle 15.95^\circ \text{ A} & \checkmark \end{cases}$

3. Below shows an **AC circuit** with an independent voltage and current source. [18 points]

(1) Please find the  $V_{TH}$  (Thevenin voltage) and  $Z_{TH}$  (Thevenin impedance) and draw Thevenin equivalent circuits between terminal a and b under  $\omega = 100 \text{ rad/s}$  and  $\omega = 200 \text{ rad/s}$ . [12 points]

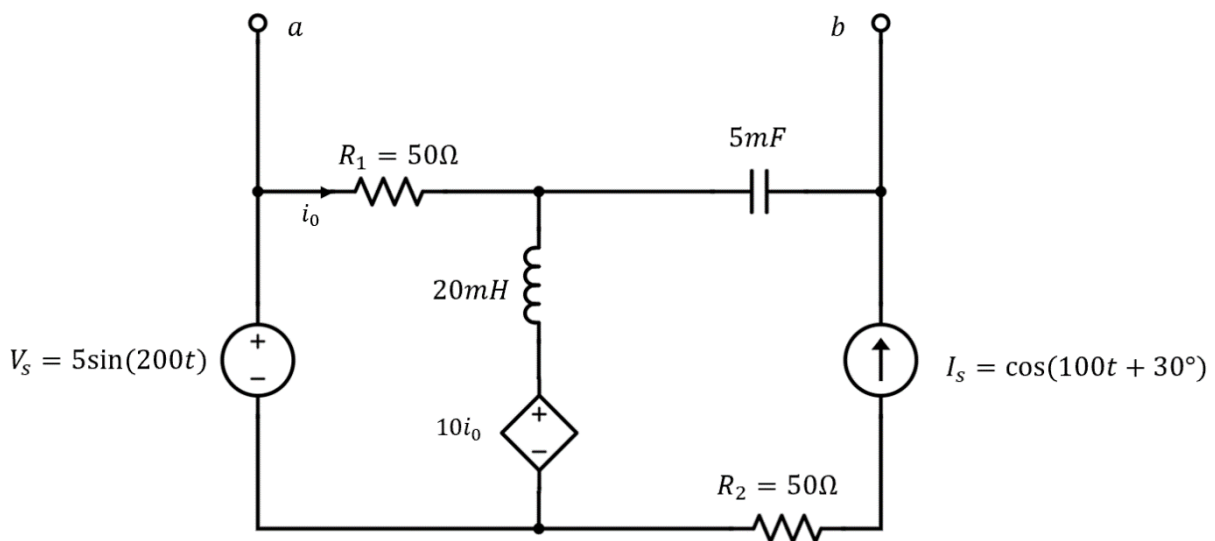
(2) Please draw a phasor diagram of the Thevenin equivalent impedance under (a)  $\omega = 100 \text{ rad/s}$  and (b)  $\omega = 200 \text{ rad/s}$ . [6 points]

Hint: There should be 2 separate phasor diagrams in total. Please label all the angles, coordinates and magnitudes of the phasors on your phasor diagrams.



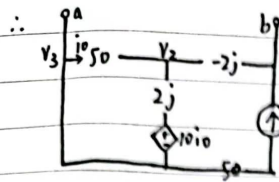(1)  $\omega = 100 \text{ rad/s}$

$\therefore Z_L = j\omega L = 2j, Z_C = \frac{1}{j\omega C} = -2j$



$V_{Th}$

$\therefore i_o = \frac{V_o - V_1}{5\Omega}$

$\therefore V_1 = (2j+10)i_o, V_2 = (2j+10)i_o + 2jI_5$

$\frac{V_2 - V_1}{5\Omega} + \frac{V_2 - 10i_o}{2j} = I_5 = \angle 30^\circ$

$V_3 = (2j+10)i_o + 2jI_5$


$V_1 - V_2 = -2jI_5 = -2j \cdot \angle 30^\circ$

$\therefore V_{ab} = V_3 - V_1 = 50i_o + 2jI_5$

$\therefore 50i_o + 2j(i_o + I_5) + 10i_o = 0, i_o = -\frac{1}{30+j} I_5$

$\therefore V_{Th} = V_{ab} = (2j - \frac{50j}{30+j}) I_5 = -0.216 + 0.263j = 0.340 \angle 129.4^\circ$

(3')

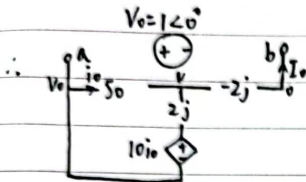

$R_{Th}$

$V_o - V = 50i_o$


(Equation max 2')

$\frac{V - V_o}{5\Omega} + \frac{V - (V_o + 10i_o)}{2j} + \frac{V}{-2j} = 0$

$\therefore V = \frac{151-25j}{26} V_o$

$\therefore I_o = \frac{V}{-2j} = \frac{151-25j}{-52j} V_o$

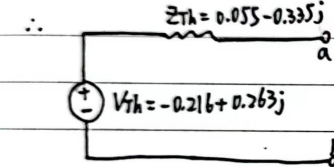
$\therefore Z_{Th} = \frac{V_o}{I_o} = \frac{-52j}{151-25j} = 0.055 - 0.335j = 0.340 \angle -80.6^\circ$  (2')



(No Figure/Wrong -1)

2'  $\omega = 200 \text{ rad/s}$

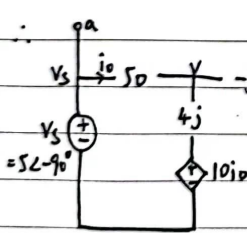$\therefore Z_L = j\omega L = 4j, Z_C = \frac{1}{j\omega C} = -j, V_s = 5 \angle -90^\circ$



$V_{Th}$


$V_s - V = 50i_o$

$\therefore V_s = (60+4j)i_o, V = (10+4j)i_o$

$\frac{V - V_s}{5\Omega} + \frac{V - (V_s + 10i_o)}{4j} = i_o$

$\therefore V_{Th} = V_s - V = 50i_o = \frac{50}{60+4j} V_s = -0.277 - 4.148j$

$= 4.157 \angle -93.81^\circ$  (3')

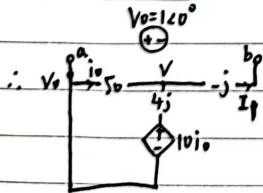


$Z_{Th}$

$V_o - V = 50i_o$

$\frac{V - V_o}{5\Omega} + \frac{V - (V_o + 10i_o)}{4j} + \frac{V}{-j} = 0$



$\therefore V = -\frac{262+25j}{613} V_o, \therefore I_0 = \frac{V}{-j} = \frac{262+25j}{613j} V_o$

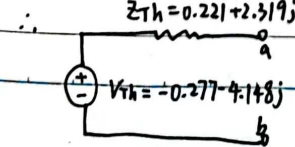$\therefore Z_{Th} = \frac{V_o}{I_0} = \frac{613j}{262+25j} = 0.221 + 2.319j = 2.329 \angle 84.55^\circ$  (2')



(1')

Date \_\_\_\_\_
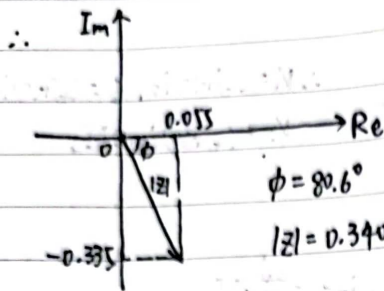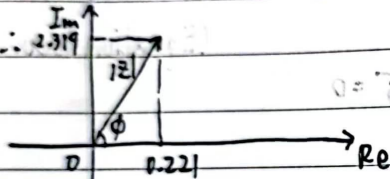
$$\therefore Z_{Th} = 0.34 \angle 14.04^\circ$$

$$\therefore Z_{Th} = 2.329 \angle 84.55^\circ$$


Notice:

1. magnitude  $|z|$  ; coordinates (Re, Im) ; angle  $\phi$  ;  $z = |z| e^{j\phi}$

(1- growth origin)


4. Please answer the following questions with the circuit shown below. [18 points]

(1) Find the mutual inductance (assume  $\omega = 1000$ ) between  $j10\ \Omega$ ,  $j4\ \Omega$  and  $j10\ \Omega$ ,  $j20\ \Omega$



$\Omega$ , are they tightly coupled or loosely coupled? [2 points]

(2) Please draw the equivalent circuit using the dependent voltage sources (example below). [8 points]

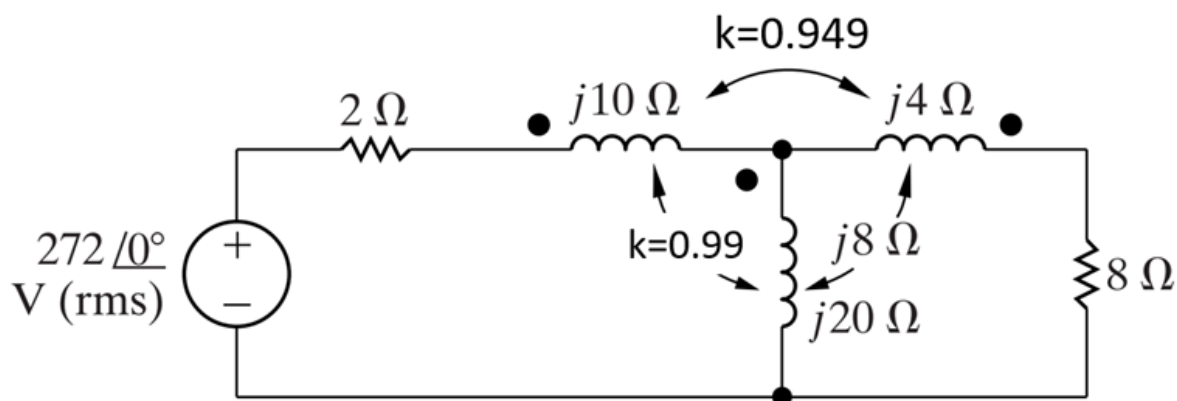(3) Verify the conservation of average power in this circuit. [8 points]



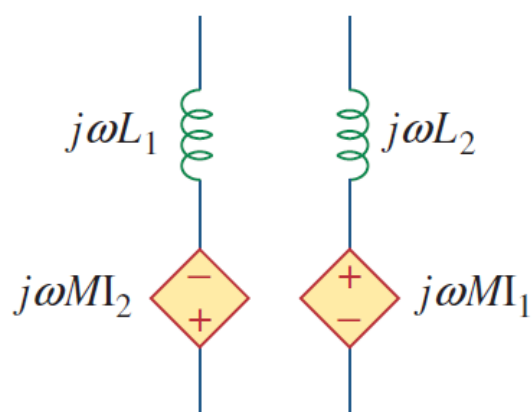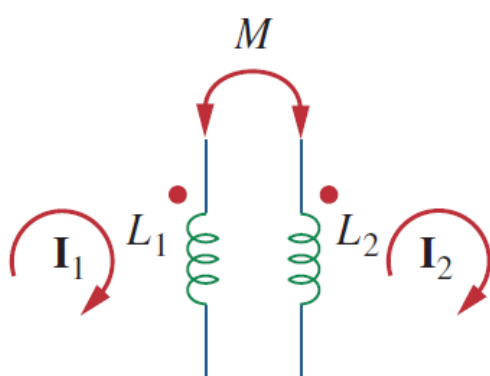*Example:* Magnetically coupled circuit and its equivalent circuit with dependent voltage sources.






## 4 (I)

4

$$(1) \quad j10, j4. \quad M = \frac{\sqrt{10 \times 4} \times 0.949}{1000} = 6 \text{ mH} \quad (0.5')$$

$$j10, j20. \quad M = \frac{\sqrt{10 \times 20} \times 0.99}{1000} = 14 \text{ mH} \quad (0.5')$$

They are both tightly coupled. (1')

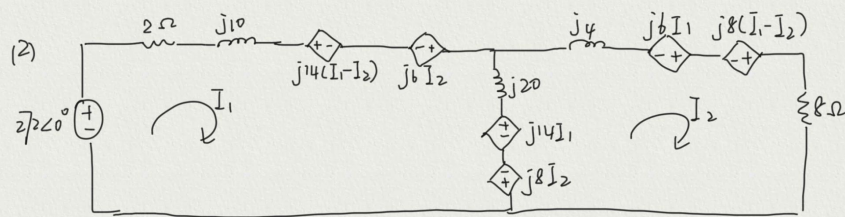

All correct 8'

one dependent source wrong: (start from b')

$$(3) \quad \begin{cases} -2\sqrt{2} + 2I_1 + j10I_1 + j14(I_1 - I_2) + j14(I_1 - I_2) - j6I_2 + j14I_1 - j8I_2 = 0 & (1') \\ j8I_2 - j14I_1 + j20(I_1 - I_1) + j4I_2 - j6I_1 - j8(I_1 - I_2) + 8I_2 = 0 & (1') \end{cases}$$

$$\begin{cases} I_1 = 20 - j4 & (1') \\ I_2 = 24 & (1') \end{cases}$$

$$P_s = \Re(V_{rms} I_1^*) = 2\sqrt{2} \times 20 = 5440 \text{ W} \quad (1')$$

$$P_{2\Omega} = |I_1|^2 \cdot R = 832 \text{ W} \quad (1')$$

$$P_{8\Omega} = |I_2|^2 \cdot R = 4608 \text{ W} \quad (1')$$

No average power in inductance.  $5440 = 832 + 4608$

$\Rightarrow$  Conservation of average power. (1')