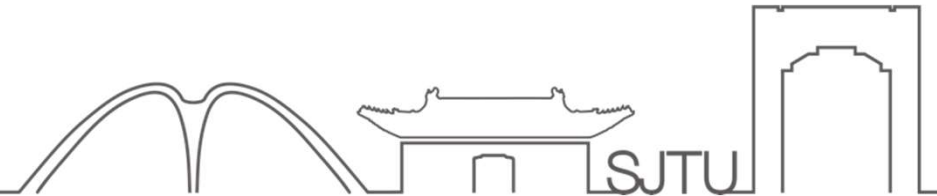




JOINT INSTITUTE
交大密西根学院

VE215 Final RC Part 2

Yu Jiayi
2024/12/13



JOINT INSTITUTE
交大密西根学院

Overview

AC Power Analysis

Instantaneous and Average Power

Maximum Average Power Transfer

Effective or RMS Value

Complex Power

Power Factor Correction

Instantaneous Power

Definition:

$$p(t) = v(t) \cdot i(t)$$

Both $v(t)$ and $i(t)$ here are instantaneous values, **not rms values**.

Instantaneous Power for **sinusoids**: $v(t) = V_m \cos(\omega t + \theta_v)$ $i(t) = I_m \cos(\omega t + \theta_i)$

$$\begin{aligned} p(t) &= V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i) \\ &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) \end{aligned}$$

$$\cos \alpha \cos \beta = \frac{1}{2} [\cos(\alpha + \beta) + \cos(\alpha - \beta)]$$



Average Power

Definition:

$$\underline{P = \frac{1}{T} \int_0^T p(t) dt}$$

For sinusoids:

$$\underline{P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)}$$

Expressed in Phasor:

$$\underline{P = \frac{1}{2} \operatorname{Re}(\tilde{V} \tilde{I}^*)}$$

$$e^{j\theta} = \cos\theta + j\sin\theta$$



Average Power

When $\theta_v = \theta_i$, we have a purely resistive load R :

$$P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R = \frac{1}{2} \frac{V_m^2}{R}$$

only valid in this case

When $\theta_v - \theta_i = \pm 90^\circ$, we have a purely reactive load X :

$$P = \frac{1}{2} V_m I_m \cos(\pm 90^\circ) = 0$$

We can conclude that only R absorbs average power. X absorbs no average power.

General Case:

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} \operatorname{Re}(\tilde{V} \tilde{I}^*) = \frac{1}{2} \operatorname{Re}((\tilde{I} Z) \tilde{I}^*)$$

$\tilde{V} = \tilde{I} Z$

$$= \frac{1}{2} \operatorname{Re}(\tilde{I} (R + jX) \tilde{I}^*) = \frac{1}{2} I_m^2 R$$

Maximum Average Power Transfer

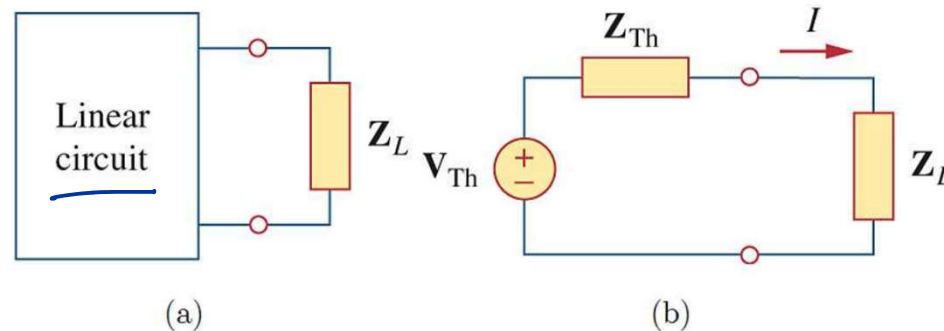


Figure 11.7 Finding the maximum average power transfer
(a) circuit with a load, (b) the Thevenin equivalent.

If there is no restriction on Z_L ,

$$Z_L = Z_{Th}^*$$

$$R_L = R_{Th} \quad X_L = -X_{Th} \quad P_{max} = \frac{|V_{Th}^2|}{8R_{Th}}$$

If Z_L is purely resistive,

$$X_L = 0$$

$$R_L = \sqrt{R_{Th}^2 + X_{Th}^2} \quad P_{max} = \frac{|V_{Th}^2|}{4(R_{Th} + \sqrt{R_{Th}^2 + X_{Th}^2})}$$

Effective or RMS Value

Definition: The effective value of an ac current i is the dc current I_{eff} that delivers the same average power to a resistor as the ac current.

$$\underline{I_{eff}^2 R = \frac{R}{T} \int_0^T i^2 dt}$$

Effective value = Root mean square (RMS) value:

$$\underline{I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{eff}}$$

$$\underline{V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2 dt} = V_{eff}}$$

Effective or RMS Value

Avg power absorbed by a circuit element (General Case):

$$P = I_{rms}^2 R = V_{rms}^2 \frac{R}{R^2 + X^2}$$
$$P = \frac{1}{2} \operatorname{Re}(\tilde{V} \tilde{I}^*) = \operatorname{Re}(\tilde{V}_{rms} \tilde{I}_{rms}^*) = \frac{1}{2} I_m^2 R = I_{rms}^2 R = \frac{1}{2} V_m^2 \operatorname{Re}\left(\frac{1}{Z^*}\right) = V_{rms}^2 \frac{R}{R^2 + X^2}$$

For **sinusoids**:

$$I_{rms} = \frac{I_m}{\sqrt{2}} \quad V_{rms} = \frac{V_m}{\sqrt{2}}$$

Avg power absorbed by an element in a **sinusoidal** circuit:

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$



Effective or RMS Value

Caution: from now on, unless specified, all values will be assumed to be RMS values.

Complex Power

$$P = \underbrace{V_{rms} I_{rms}}_{|S|} \underbrace{\cos(\theta_v - \theta_i)}_{pf}$$

$$\begin{aligned} \text{Complex Power} = \tilde{S} &= \tilde{V}_{rms} \tilde{I}_{rms}^* = |I_{rms}| |V_{rms}| \angle(\theta_v - \theta_i) \\ &= |S| \angle(\theta_v - \theta_i) \text{ (polar form)} \\ &= P + jQ \text{ (rectangular form)} \end{aligned}$$

Value	Name	Meaning	Unit
$ S $	Apparent power	Magnitude of \tilde{S}	VA
$\cos(\theta_v - \theta_i)$	Power factor	Cosine of angle of \tilde{S}	/
P	Real power	Real part of \tilde{S}	W
Q	Reactive power	Imaginary part of \tilde{S}	VAR

Complex Power

Complex power:

$$\begin{aligned}\tilde{S} &= \tilde{V}_{rms} \tilde{I}_{rms}^* = |I_{rms}| |V_{rms}| \angle(\theta_v - \theta_i) = |S| \angle(\theta_v - \theta_i) = P + jQ \\ &= |I_{rms}|^2 Z = \frac{|V_{rms}|^2}{Z^*}\end{aligned}$$

Apparent power:

$$|S| = |V_{rms}| |I_{rms}| = |I_{rms}|^2 |Z| = \sqrt{P^2 + Q^2}$$

Real power:

$$P = \operatorname{Re}(\tilde{S}) = |S| \cos(\theta_v - \theta_i) = |I_{rms}|^2 R$$

Reactive power:

$$Q = \operatorname{Im}(\tilde{S}) = |S| \sin(\theta_v - \theta_i) = |I_{rms}|^2 X$$

Power factor (pf or $\cos\theta$):

$$pf = \frac{P}{|S|} = \cos(\theta_v - \theta_i)$$

Complex Power

Power factor:

$$pf = \cos(\theta_v - \theta_i)$$

$\theta_v - \theta_i < 0$: leading pf

$\theta_v - \theta_i > 0$: lagging pf

Since $\cos(\theta_v - \theta_i) = \cos(\theta_i - \theta_v)$, the pf value only tells part of the story. Every time you are asked for a power factor, **you must declare whether it is leading or lagging.**

Complex Power

We can use the sign of pf angle or Q to identify the property of the circuit and the loads:

	(1)	(2)	(3)
pf Angle	$\theta_v - \theta_i = 0$	$\theta_v - \theta_i < 0$	$\theta_v - \theta_i > 0$
Sign of Q	$Q = 0$	$Q < 0$	$Q > 0$
Properties	<u>Unity pf</u> I, V in phase $X = 0$ Resistive loads	<u>Leading pf</u> I leads V $X < 0$ Capacitive loads	<u>Lagging pf</u> I lags V $X > 0$ Inductive loads






Complex Power

$$S = P + jQ$$

$$Z = R + jX$$

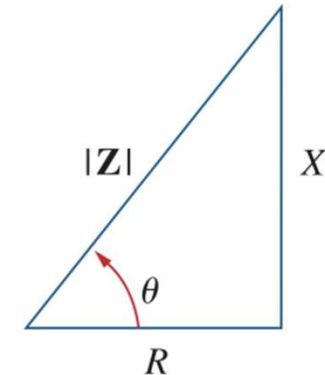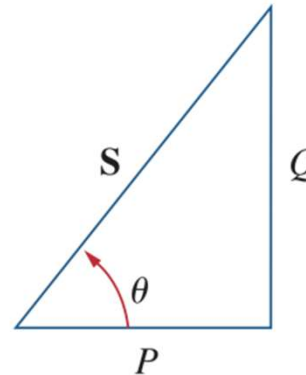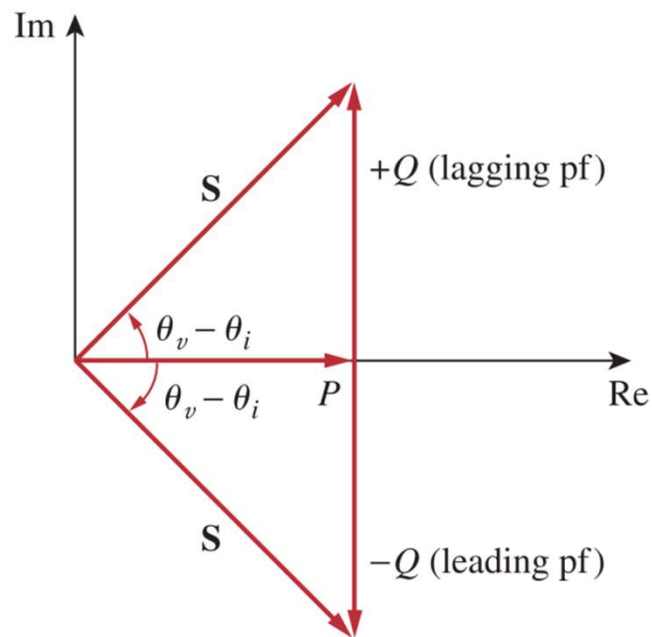
And observe that the power factor angle is equal to the angle of the impedance of that part of the circuit.



Power Factor Correction


Goal: increase the pf of a load \rightarrow make it less inductive \rightarrow reduce energy loss

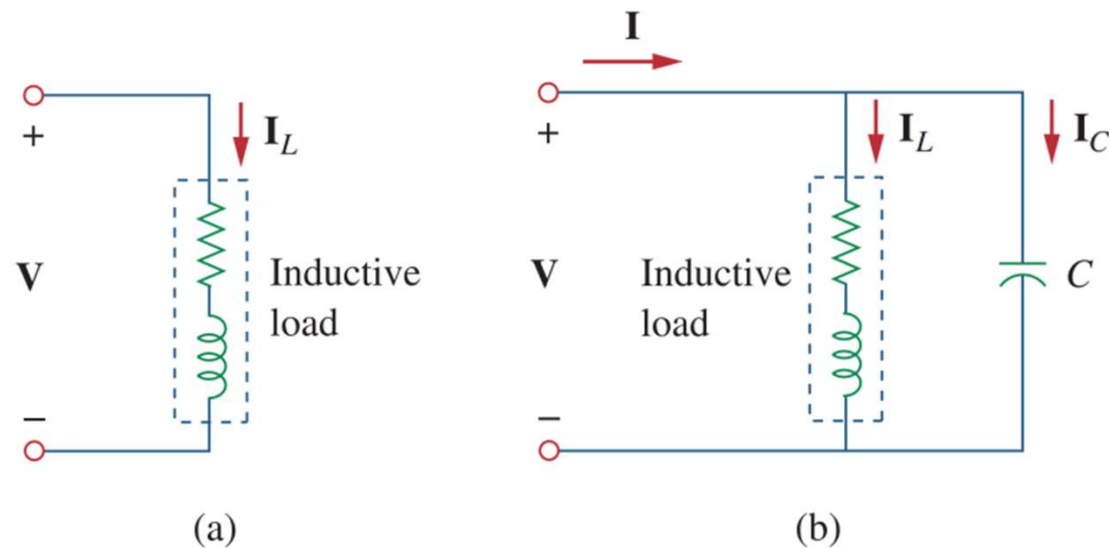Solution: add a capacitor in parallel to the load



Power Factor Correction

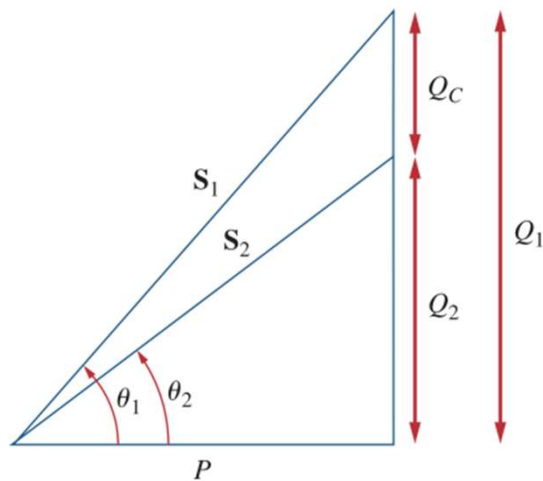Goal: increase the pf from $\cos\theta_1$ to $\cos\theta_2$.



Initial:

$$\begin{aligned} P &= |S_1| \cos\theta_1 \\ Q &= |Q_1| \sin\theta_1 = P \tan\theta_1 \end{aligned}$$

Expected outcome:

$$\begin{aligned} P &= |S_2| \cos\theta_2 \\ Q &= |Q_2| \sin\theta_2 = P \tan\theta_2 \end{aligned}$$


Since $Q_c (= Q_1 - Q_2) = \frac{V_{rms}^2}{X_c}$, then the value of the required capacitance C is:

$$C = \frac{Q_c}{\omega V_{rms}^2} = \frac{Q_1 - Q_2}{\omega V_{rms}^2} = \frac{P(\tan\theta_1 - \tan\theta_2)}{\omega V_{rms}^2}$$

Conservation of AC Power

The Principle of Conservation of AC Power:

The complex, real, and reactive powers of the source equal the respective sums of the complex, real, and reactive powers of the individual loads.
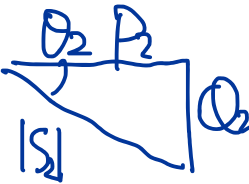
$$\begin{array}{l} \cos \theta_2 = 0.8 \\ P_2 = 4 \text{ kW} \\ Q_2 = -3 \text{ kVAR} \end{array}$$


Exercise 1

Three loads are connected in parallel across a 300 V(rms) line, as shown in the figure. Load 1 absorbs 3 kW at unity power factor $Q_1 = 0$; Load 2 absorbs 5 kVA at 0.8 leading; Load 3 absorbs 5 kW and delivers 6 kvars. a) Find the impedance that is equivalent to the three parallel loads. b) Find the power factor of the equivalent load as seen from the line's input terminals.

$$a) S_1 = 3 \text{ kW} + j0 \text{ kVAR}$$

$$S_2 = 4 \text{ kW} - j3 \text{ kVAR}$$

$$S_3 = 5 \text{ kW} - j6 \text{ kVAR}$$

$$S = S_1 + S_2 + S_3$$


$$= 12 \text{ kW} + j9 \text{ kVAR}$$

$$= V_{\text{rms}} I_{\text{rms}}^*$$

$$\Rightarrow I_{\text{rms}}^* = 40 - j30 \text{ A}$$

$$I_{\text{rms}} = 40 + j30 \text{ A}$$
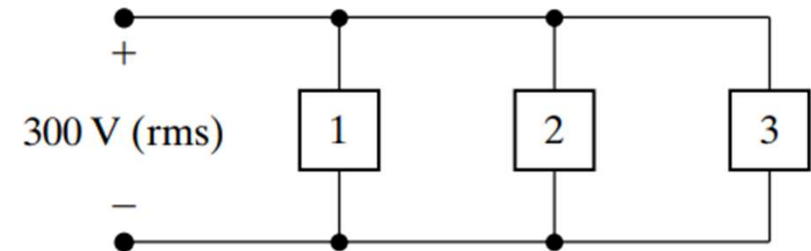
$$b) \text{ pf} = \cos(-36.87^\circ) = 0.8 \text{ leading}$$



$$Z = \frac{V_{\text{rms}}}{I_{\text{rms}}} = 4.8 - j3.6 \Omega = 6 \angle -36.87^\circ \Omega$$



Exercise 1

$$[\text{a}] \quad S_1 = 3 + j0 \text{ kVA}; \quad S_2 = 4 - j3 \text{ kVA}; \quad S_3 = 5 - j6 \text{ kVA}$$

$$S_T = S_1 + S_2 + S_3 = 12 - j9 \text{ kVA}$$

$$300\mathbf{I}^* = (12 - j9) \times 10^3; \quad \therefore \quad \mathbf{I} = 40 + j30 \text{ A}$$

$$Z = \frac{300}{40 + j30} = 4.8 - j3.6 \Omega = 6 \angle -36.87^\circ \Omega$$

$$[\text{b}] \quad \text{pf} = \cos(-36.87^\circ) = 0.8 \text{ leading}$$

Exercise 2

- a) Determine the load impedance for the circuit shown in the figure that will result in maximum average power being transferred to the load if $\omega = 8 \text{ krad/s}$.
- b) Determine the maximum average power delivered to the load from part (a) if

$$v_g = 10 \cos 8000t \text{ V.}$$

$$\begin{aligned} \text{a) } Z_{Th} &= -j4k // 4k + j4k \\ &= 2k + j2k \Omega \end{aligned}$$


$$Z_L = Z_{Th}^* = 2k - j2k \Omega$$

$$\text{b) } V_{Th} = 4k \Omega \cdot \frac{V_g}{-j4k + 4k}$$

$$V_g = 10 \angle 0^\circ \text{ V}$$

$$V_{Th} = 5 + j5 \text{ V}$$

$$P_{max} = \frac{|V_{Th}|^2}{8R_{Th}} = 3.125 \text{ mW}$$

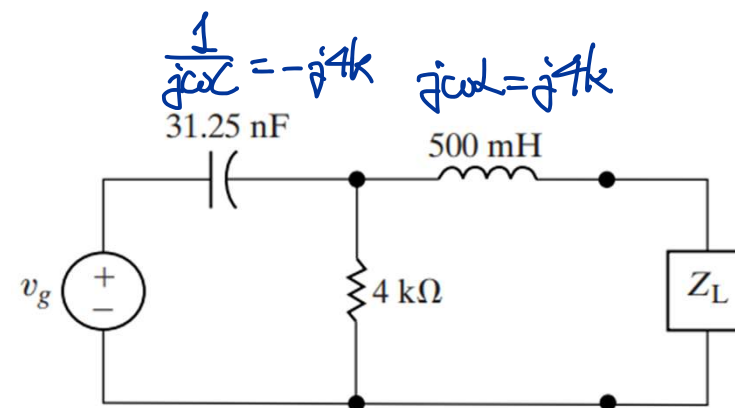


Exercise 2

$$[a] Z_{Th} = j4000 + \frac{(4000)(-j4000)}{4000 - j4000} = 2000 + j2000 \Omega$$

$$\therefore Z_L = Z_{Th}^* = 2000 - j2000 \Omega$$
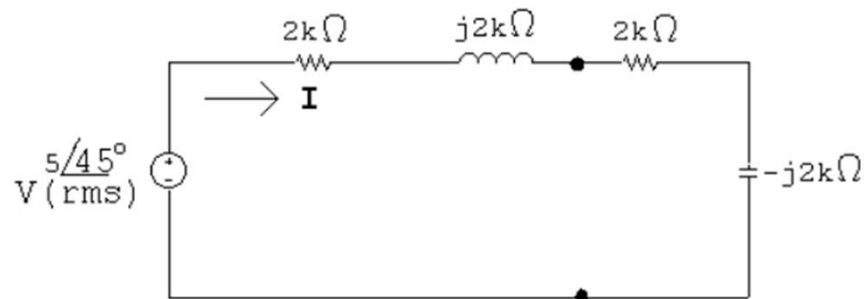
$$[b] V_{Th} = \frac{10\angle 0^\circ(4000)}{4000 - j4000} = 5 + j5 = 5\sqrt{2}\angle 45^\circ \text{ V}$$



$$\mathbf{I} = \frac{5\sqrt{2}\angle 45^\circ}{4000} = 1.25\sqrt{2}\angle 45^\circ \text{ mA}$$

$$|\mathbf{I}_{\text{rms}}| = 1.25 \text{ mA}$$

$$P_{\text{load}} = (0.00125)^2(2000) = 3.125 \text{ mW}$$

Exercise 3

When connected to a 120-V (rms), 60-Hz power line, a load absorbs 4 kW at a lagging power factor of 0.8. Find the value of capacitance necessary to raise the pf to 0.95.

$$C = \frac{P(\tan\theta_1 - \tan\theta_2)}{\omega V_{\text{rms}}^2}$$

$$= 310.44 \mu\text{F}$$

Exercise 3

Solution:

If the $\text{pf} = 0.8$, then

$$\cos\theta_1 = 0.8 \quad \Rightarrow \quad \theta_1 = 36.87^\circ$$

where θ_1 is the phase difference between voltage and current.
obtain the apparent power from the real power and the pf as

$$S_1 = \frac{P}{\cos\theta_1} = \frac{4000}{0.8} = 5000 \text{ VA}$$

The reactive power is

$$Q_1 = S_1 \sin\theta = 5000 \sin 36.87 = 3000 \text{ VAR}$$

When the pf is raised to 0.95,

$$\cos\theta_2 = 0.95 \quad \Rightarrow \quad \theta_2 = 18.19^\circ$$

The real power P has not changed. But the apparent power has changed; its new value is

$$S_2 = \frac{P}{\cos\theta_2} = \frac{4000}{0.95} = 4210.5 \text{ VA}$$

The new reactive power is

$$Q_2 = S_2 \sin\theta_2 = 1314.4 \text{ VAR}$$

The difference between the new and old reactive powers is due to the parallel addition of the capacitor to the load. The reactive power due to the capacitor is

$$Q_C = Q_1 - Q_2 = 3000 - 1314.4 = 1685.6 \text{ VAR}$$

and

$$C = \frac{Q_C}{\omega V_{\text{rms}}^2} = \frac{1685.6}{2\pi \times 60 \times 120^2} = 310.5 \mu\text{F}$$



References

1. 2023 Fall VE215 slides, Sung-Liang Chen
2. 2023 Fall RC5, Shunyao Huang
3. Fundamentals of Electric Circuits, 5th e, Sadiku, Matthew



JOINT INSTITUTE
交大密西根学院

Good luck for your exam!

