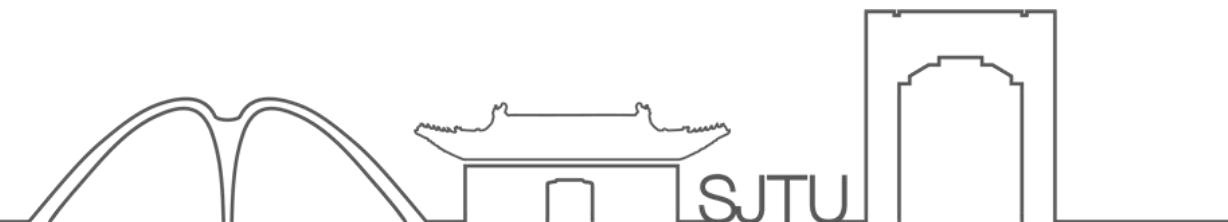




JOINT INSTITUTE
交大密西根学院

VE215 Final RC Part 1

Jiang Naicheng 姜乃成
2024/12/9



Contents

Sinusoids and Phasors

Sinusoidal steady-state analysis

Three Phase Circuits



JOINT INSTITUTE
交大密西根学院

Alternating Current(AC) Circuits:

Circuits driven by sinusoidal current or voltage sources

Leads & Lags:


$$v(t) = V_m \sin(\omega t + \phi)$$

where

V_m : amplitude

ω : angular frequency

ϕ : initial phase

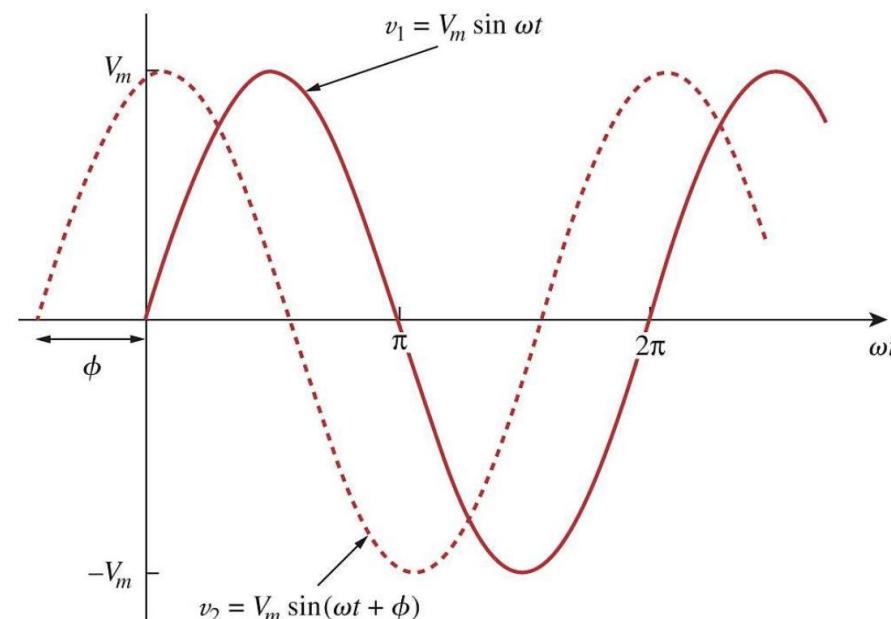

Phasors:

$$v(t) = V_m \cos(\omega t + \phi) = \operatorname{Re}(\tilde{V} e^{j\omega t})$$

where

$$\tilde{V} = V_m e^{j\phi} = V_m \angle \phi$$

is the **phasor** representation, polar form



while $V = a + bj$, is teh so called rectangular form

memorize, or copy

Phasor Diagram:

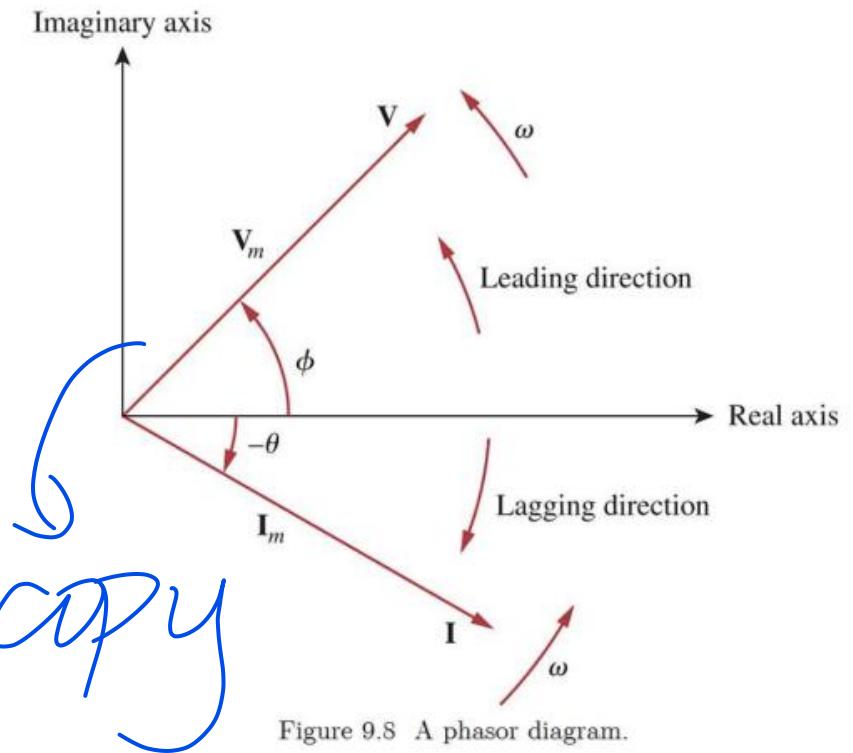


Figure 9.8 A phasor diagram.

$$v(t) = V_m \cos(\omega t + \phi) \Leftrightarrow \tilde{V} = V_m \angle \phi$$

A little more about lag, lead, and in phase: sinusoidal

Let us examine the two sinusoids

$$v_1(t) = V_m \sin \omega t$$

$$v_2(t) = V_m \sin(\omega t + \phi)$$

shown in Fig. 9.2.

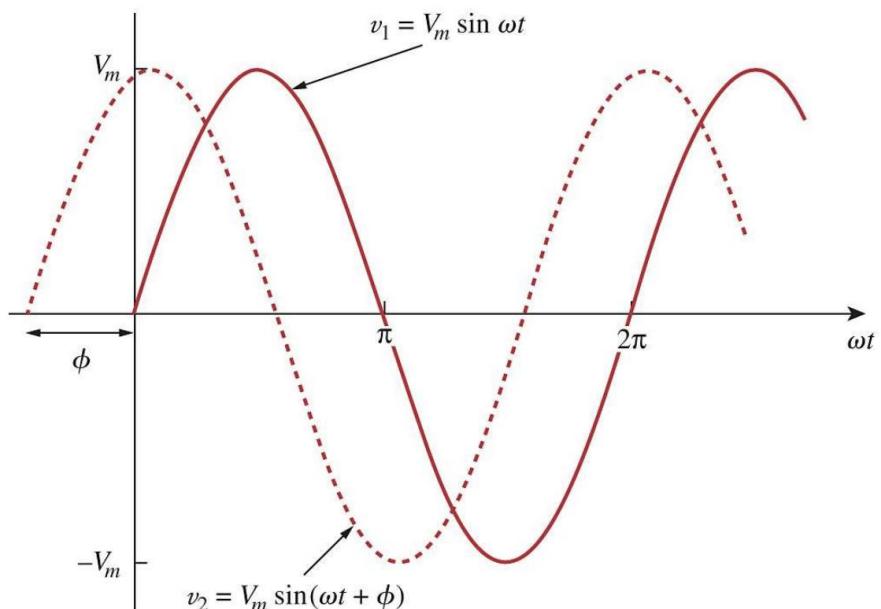


Figure 9.2 Two sinusoids with different phases.

The starting point of v_2 in Fig. 9.2 occurs first in time. Therefore, we say that v_2 leads v_1 by ϕ or that v_1 lags v_2 by ϕ . If $\phi \neq 0$, we say that v_1 and v_2 are out of phase. If $\phi = 0$, then v_1 and v_2 are said to be in phase.

memorize, or copy

Recall:

$$\sin(x) = \cos(x - \pi/2)$$

No need to differentiate sine/cosine forms here!

TABLE 9.2**Summary of voltage - current relationships**

Element	Time domain	Frequency domain
R	$v = Ri$	$\tilde{V} = R\tilde{I}$
L	$v = L \frac{di}{dt}$	$\tilde{V} = j\omega L\tilde{I}$
C	$i = C \frac{dv}{dt}$	$\tilde{V} = \frac{1}{j\omega C} \tilde{I}$

copy

About admittance and impedance:

$$Y = \frac{\tilde{I}}{\tilde{V}} = \frac{1}{Z}$$

copy

The admittance can be written as

$$Y = G + jB$$

where

G : conductance

B : susceptance

The admittance, conductance, and susceptance are all measured in siemens.

$$Z = R + jX = |Z| \angle \theta$$

where

R : resistance

X : reactance

If $X > 0$, we say that the impedance is inductive or lagging since current lags voltage; If $X < 0$, we say that the impedance is capacitive or leading because current leads voltage.

The impedance, resistance, and reactance are all measured in ohms.

Equivalence Circuits

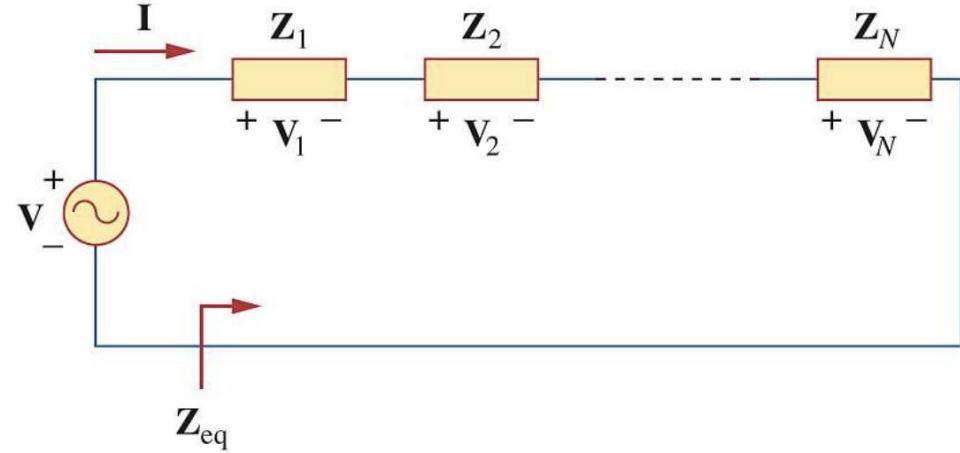


Figure 9.18 N impedances in series.

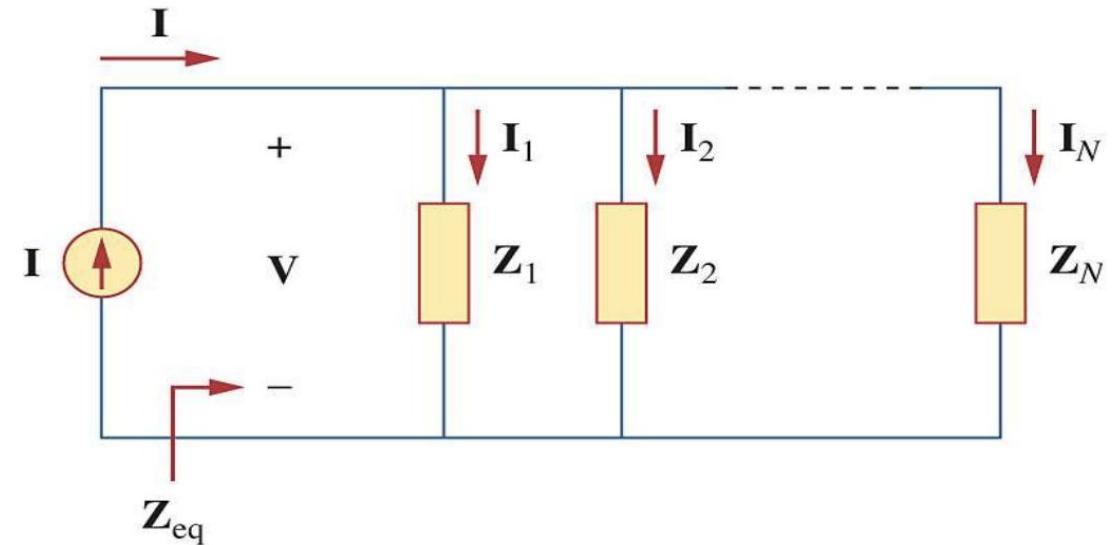


Figure 9.20 N impedances in parallel.

$$Z_{eq} = \frac{\tilde{V}}{\tilde{I}} = \frac{\sum_{i=1}^N \tilde{V}_i}{\tilde{I}} = \sum_{i=1}^N \frac{\tilde{V}_i}{\tilde{I}} = \sum_{i=1}^N Z_i$$

KVL

COPY

$$Y_{eq} = \frac{\tilde{I}}{\tilde{V}} = \frac{\sum_{i=1}^N \tilde{I}_i}{\tilde{V}} = \sum_{i=1}^N \frac{\tilde{I}_i}{\tilde{V}} = \sum_{i=1}^N Y_i$$

Exercise 1

Suppose we have following elements: 600Ω resistors, $0.1\mu\text{F}$ capacitances, 10mH inductances. Please use the above elements to create an impedance of $300 - 400j \Omega$ at a frequency of 10,000 rad/s. The number of each elements is adequate.



JOINT INSTITUTE
交大密西根学院


$$R = 300 \Omega = \frac{600^2}{600+600} \Omega$$

$$\omega L - \frac{1}{\omega C} = 10000L - \frac{1}{10^4 C} = -400$$

$$L = 10 \text{ mH}$$

$$\Rightarrow \frac{1}{10^4 C} = 100 + 400$$

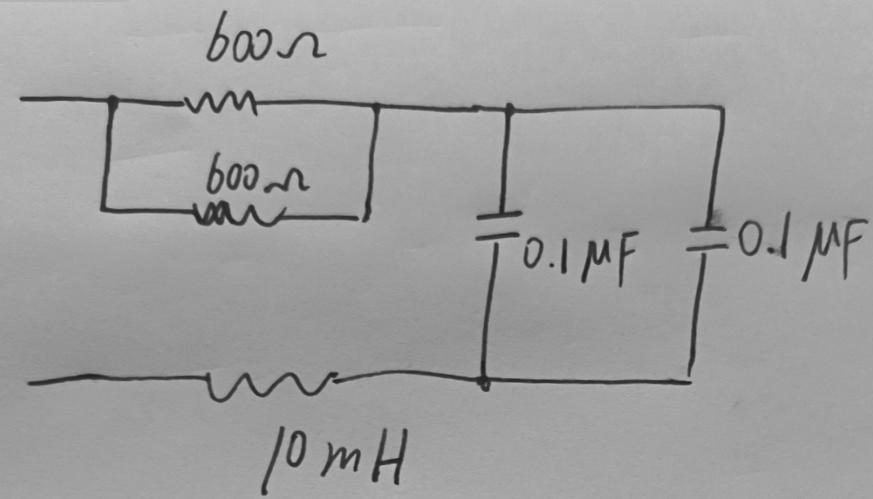$\Rightarrow C = 0.2 \mu\text{F}$, two $0.1 \mu\text{F}$ in parallel.



Source Transformation and Equivalence Circuit:


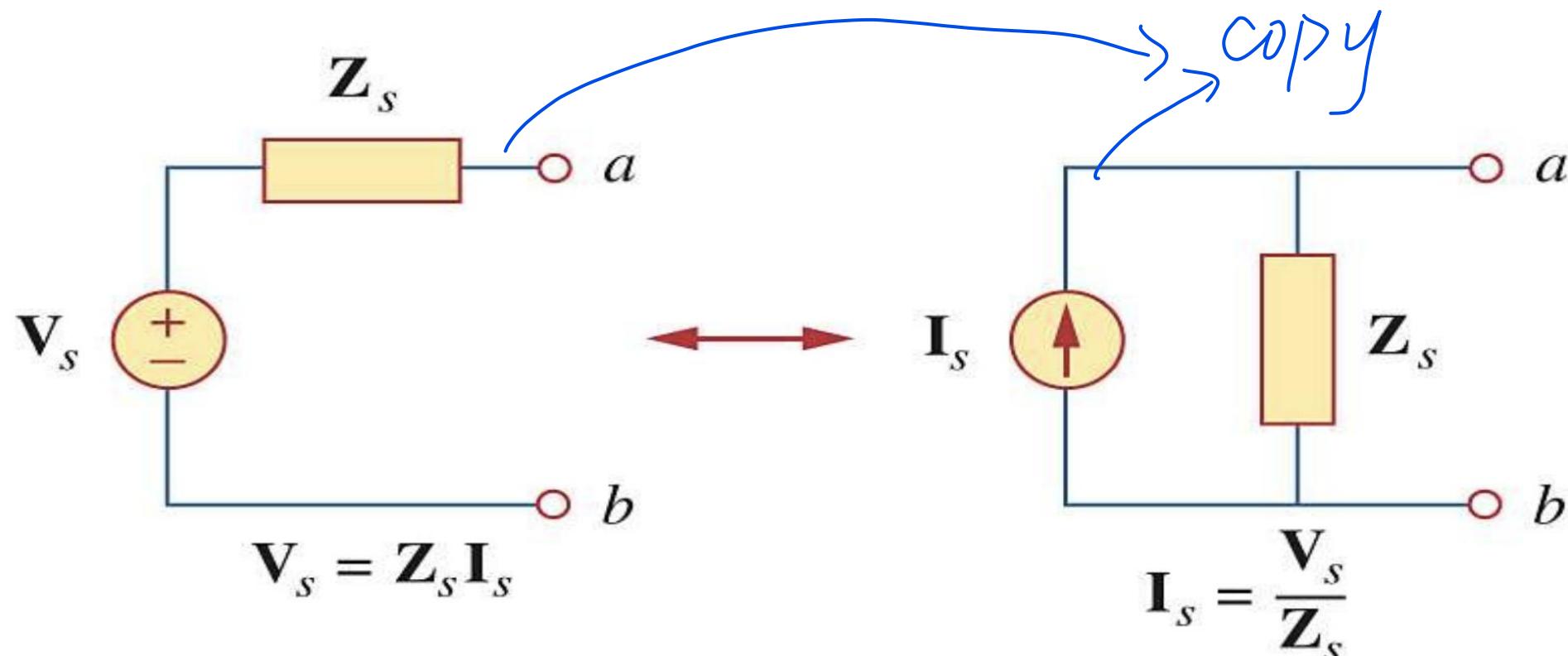


Figure 10.16 Source transformation.


Exercise 2

Find the Norton equivalent circuit with respect to the terminals a,b for the circuit shown in Fig. P9.50 when $\mathbf{V}_s = 5 \angle 0^\circ \text{ V}$.

Figure P9.50

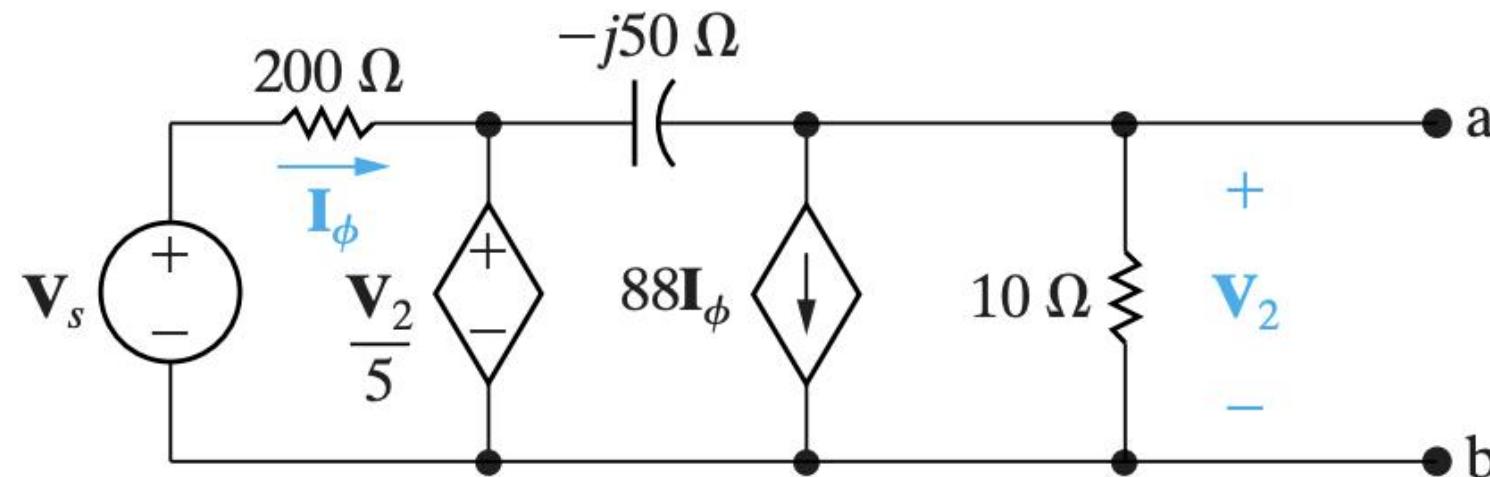

P 9.50 Open circuit voltage:

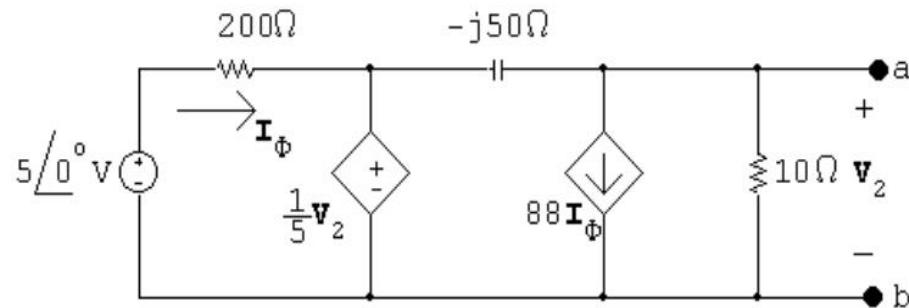


$$\frac{\mathbf{V}_2}{10} + 88\mathbf{I}_\phi + \frac{\mathbf{V}_2 - \frac{1}{5}\mathbf{V}_2}{-j50} = 0$$

$$\mathbf{I}_\phi = \frac{5 - (\mathbf{V}_2/5)}{200}$$

Solving,

$$\mathbf{V}_2 = -66 + j88 = 110\angle 126.87^\circ \text{ V} = \mathbf{V}_{\text{Th}}$$

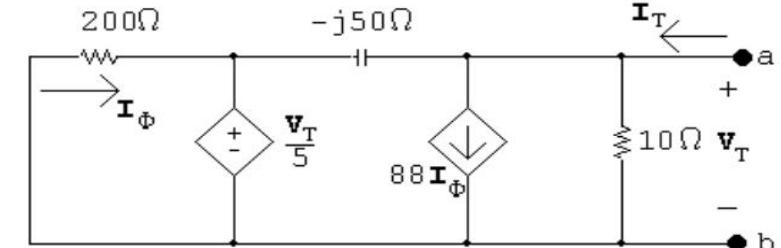Find the Thévenin equivalent impedance using a test source:



$$\mathbf{I}_T = \frac{\mathbf{V}_T}{10} + 88\mathbf{I}_\phi + \frac{0.8\mathbf{V}_t}{-j50}$$


$$\mathbf{I}_\phi = \frac{-\mathbf{V}_T/5}{200}$$

$$\mathbf{I}_T = \mathbf{V}_T \left(\frac{1}{10} - 88 \frac{\mathbf{V}_T/5}{200} + \frac{0.8}{-j50} \right)$$

$$\therefore \frac{\mathbf{V}_T}{\mathbf{I}_T} = 30 - j40 = Z_{\text{Th}}$$

$$\mathbf{I}_N = \frac{\mathbf{V}_{\text{Th}}}{Z_{\text{Th}}} = \frac{-66 + j88}{30 - j40} = -2.2 + j0 \text{ A}$$

The Norton equivalent circuit:

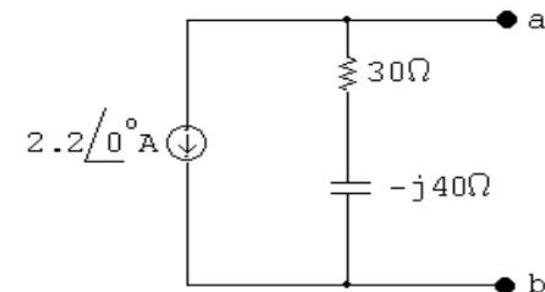


Superposition in AC Circuits:

* Follow these three steps

1. For DC voltage/current sources: take capacitance as an open and inductance as a short circuit.
2. For AC voltage/current sources: transform capacitance and inductance into impedance in frequency domain.
3. In AC circuit, when analyzing one specific source:
 - (1)Handle the capacitance and inductance following 1.&2. above, based on what type of the source is being analyzed.
 - (2)Then, take other voltage sources as a short circuit while other current sources as an open circuit.

Exercise 3

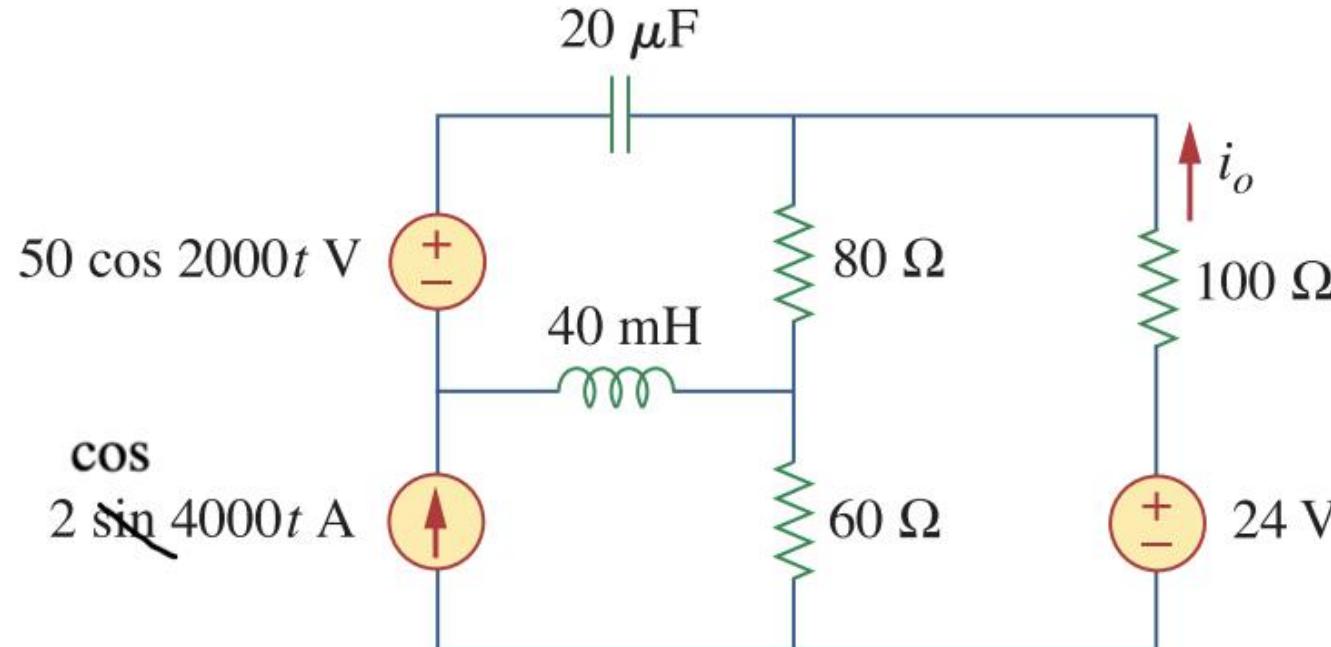
10.48 Find i_o in the circuit of Fig. 10.93 using superposition.



Chapter 10, Solution 48.

Let $i_o = i_{o1} + i_{o2} + i_{o3}$, where i_{o1} is due to the ac voltage source, i_{o2} is due to the dc voltage source, and i_{o3} is due to the ac current source. For i_{o1} , consider the circuit in Fig. (a).
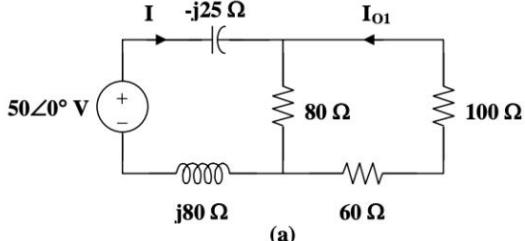
$$\begin{aligned}\omega &= 2000 \\ 50\cos(2000t) &\longrightarrow 50\angle 0^\circ \\ 40 \text{ mH} &\longrightarrow j\omega L = j(2000)(40 \times 10^{-3}) = j80 \\ 20 \mu\text{F} &\longrightarrow \frac{1}{j\omega C} = \frac{1}{j(2000)(20 \times 10^{-6})} = -j25\end{aligned}$$



$$80 \parallel (60 + 100) = 160/3$$

$$I = \frac{50}{160/3 + j80 - j25} = \frac{30}{32 + j33}$$

Using current division,


$$I_{o1} = \frac{-80I}{80+160} = \frac{-1}{3}I = \frac{10\angle 180^\circ}{46\angle 45.9^\circ}$$

$$I_{o1} = 0.217\angle 134.1^\circ$$

Hence,

$$i_{o1} = 0.217\cos(2000t + 134.1^\circ) \text{ A}$$

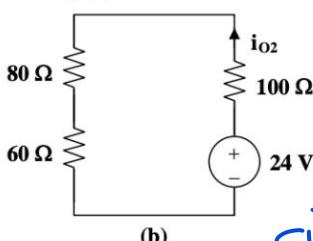For i_{o2} , consider the circuit in Fig. (b).




when there are multiple W_s , conserve the "W" part by using sin/cos (wt + ...) in time domain.

$$i_{o2} = \frac{24}{80 + 60 + 100} = 0.1 \text{ A}$$

For i_{o3} , consider the circuit in Fig. (c).
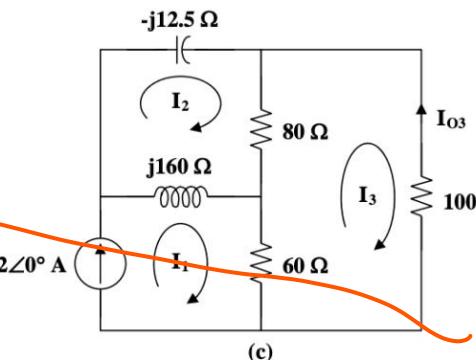
$$\begin{aligned}\omega &= 4000 \\ 2\cos(4000t) &\longrightarrow 2\angle 0^\circ \\ 40 \text{ mH} &\longrightarrow j\omega L = j(4000)(40 \times 10^{-3}) = j160 \\ 20 \mu\text{F} &\longrightarrow \frac{1}{j\omega C} = \frac{1}{j(4000)(20 \times 10^{-6})} = -j12.5\end{aligned}$$



For mesh 1,

$$I_1 = 2 \quad (1)$$

For mesh 2,

$$(80 + j160 - j12.5)I_2 - j160I_1 - 80I_3 = 0$$

Simplifying and substituting (1) into this equation yields

$$(8 + j14.75)I_2 - 8I_3 = j32 \quad (2)$$

For mesh 3,

$$240I_3 - 60I_1 - 80I_2 = 0$$

Simplifying and substituting (1) into this equation yields

$$I_2 = 3I_3 - 1.5 \quad (3)$$

$$\begin{aligned}W_1 : I_1 &= a_1 + b_1 j \\ &= C_1 \angle \theta_1\end{aligned}$$

$$\begin{aligned}W_2 : I_2 &= a_2 + b_2 j \\ &= C_2 \angle \theta_2\end{aligned}$$

If $W_1 \neq W_2$
Don't directly sum I_1, I_2 up
in phasor or
or rect form !

$$\begin{aligned}\text{Substituting (3) into (2) yields} \\ (16 + j44.25)I_3 &= 12 + j54.125\end{aligned}$$

$$I_3 = \frac{12 + j54.125}{16 + j44.25} = 1.1782 \angle 7.38^\circ$$

$$\begin{aligned}I_{o3} &= -I_3 = -1.1782 \angle 7.38^\circ \\ i_{o3} &= -1.1782 \sin(4000t + 7.38^\circ) \text{ A}\end{aligned}$$

Hence,

Therefore,


$$i_o = \{0.1 + 0.217 \cos(2000t + 134.1^\circ) - 1.1782 \sin(4000t + 7.38^\circ)\} \text{ A}$$

Three-phase Circuits

A three-phase system is produced by a generator consisting of three sources having **the same amplitude and frequency** but **out of phase with each other by 120 degrees**. **Voltage sources meeting this condition is called balanced sources.**

i.e., $\tilde{V}_{an} + \tilde{V}_{bn} + \tilde{V}_{cn} = 0$


Physical illustration of three-phase

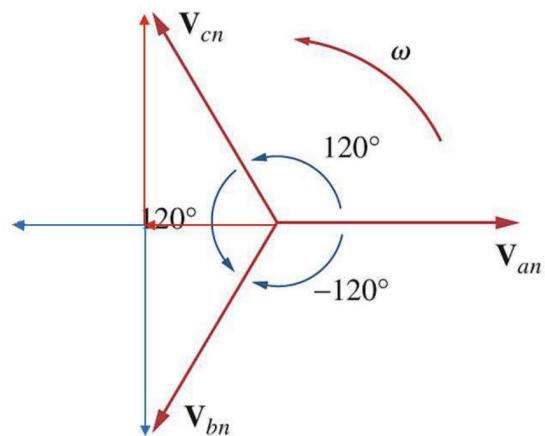


▼ Balanced Three-Phase Voltage Sources

▼ Diffrent Types

- Y-Type

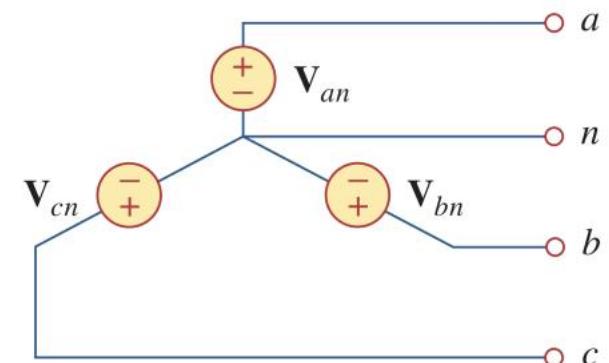

- Δ -Type

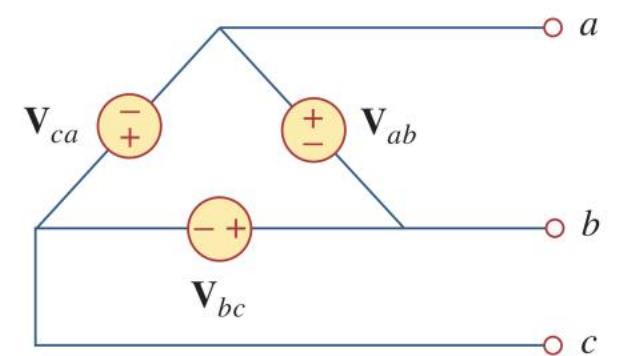

A load is said to be balanced if the phase impedances **are equal in magnitude and phase**

COPY

For a balanced wye-connected load,

$$Z_1 = Z_2 = Z_3 = Z_Y$$


For a balanced delta-connected load,

$$Z_A = Z_B = Z_C = Z_\Delta$$

If loads are balanced, the relationship below holds:

$$Z_\Delta = 3Z_Y \text{ or } Z_Y = \frac{1}{3}Z_\Delta$$

Copy

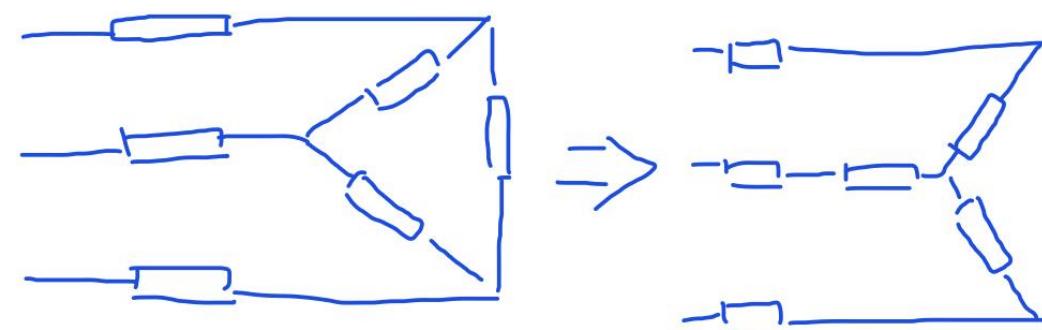

Some concepts to be emphasized:

Line:

Conductors connecting loads and sources

Line voltage:

voltage measured between two different lines

Line currents:

The current passing along each line

Phase:

Connected between any pair of line terminals (an element)

Phase voltage:

The voltage measured across any phase. In delta-delta system, $VP=VL$.

Phase currents:

The current passing through the phase. In Y-Y system, $IP=IL$.

ignore
this if
you find
difficult
to
understand

Just refer
to Page 20-21
is enough.

Also, abc/acb, positive/negative sequence, check them in your slides!

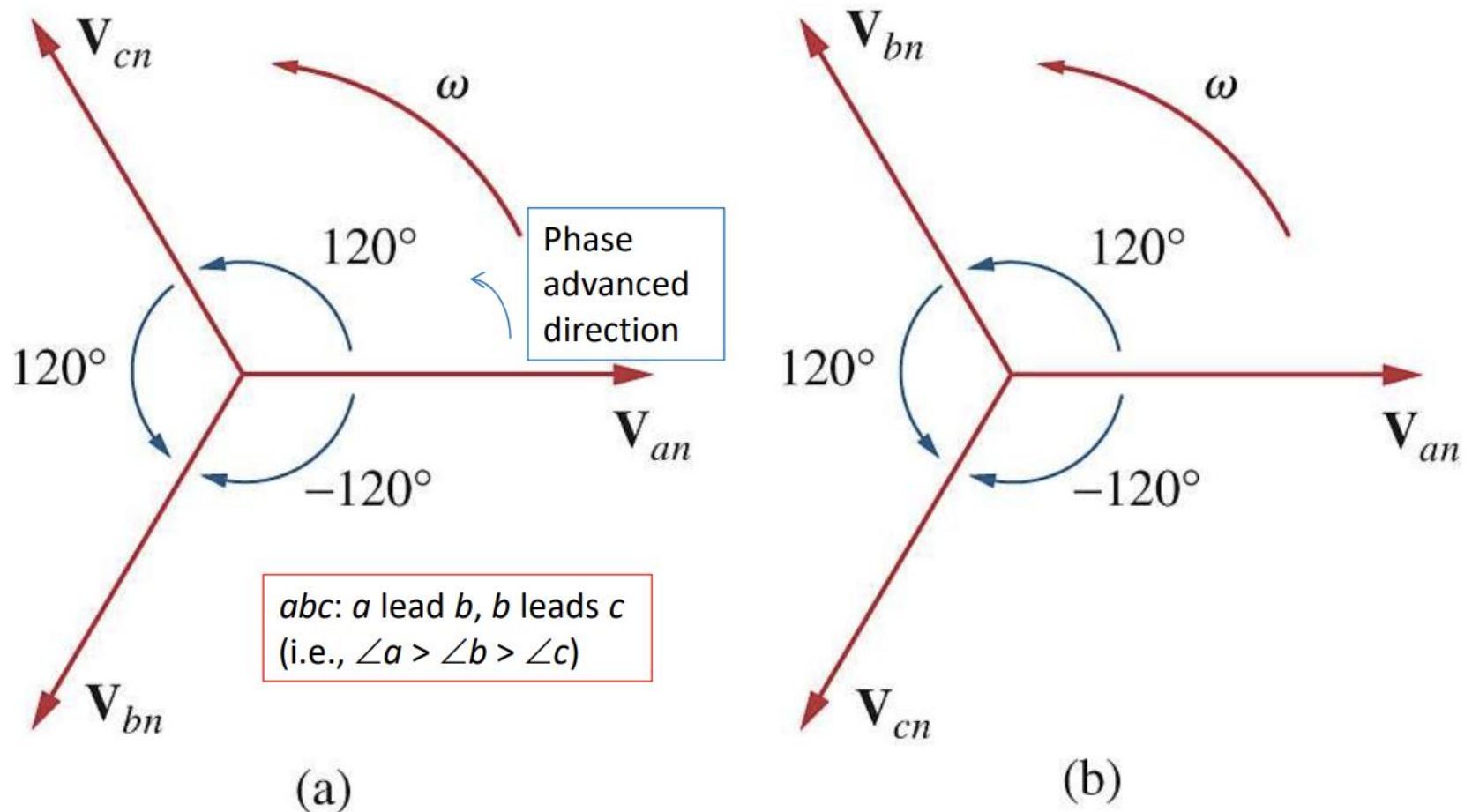


Figure 12.7 Phase sequences: (a) *abc* or positive sequence, (b) *acb* or negative sequence.

Take-aways: V_p is the effective or rms value of phase voltage

Y-Y

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle +120^\circ$$

Same as line currents

$$V_{ab} = \sqrt{3} V_p \angle 30^\circ$$

$$V_{bc} = V_{ab} \angle -120^\circ$$

$$V_{ca} = V_{ab} \angle +120^\circ$$

$$I_a = V_{an}/Z_Y$$

$$I_b = I_a \angle -120^\circ$$

$$I_c = I_a \angle +120^\circ$$

COP

Y-Δ

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle +120^\circ$$

$$I_{AB} = V_{AB}/Z_\Delta$$

$$I_{BC} = V_{BC}/Z_\Delta$$

$$I_{CA} = V_{CA}/Z_\Delta$$

$$V_{ab} = \overline{V_{AB}} = \sqrt{3} V_p \angle 30^\circ$$

$$V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$$


$$V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$$

$$I_a = I_{AB} \sqrt{3} \angle -30^\circ$$


$$I_b = I_a \angle -120^\circ$$

$$I_c = I_a \angle +120^\circ$$

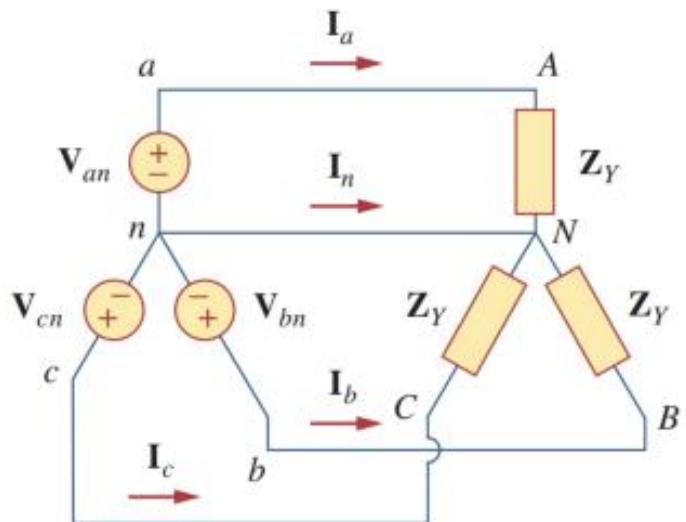magnitude: $V_L = \sqrt{3} V_p$
 $I_L = I_p$



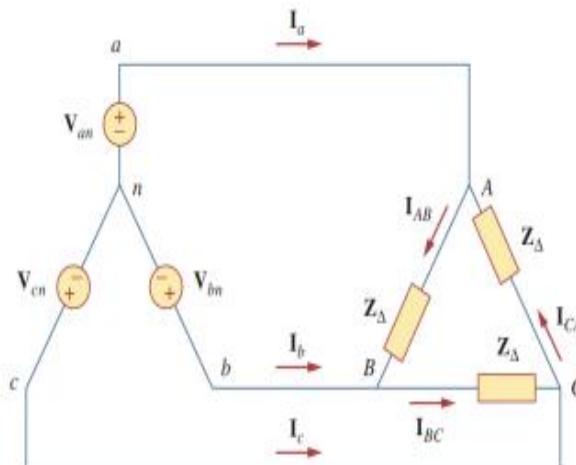magnitude
 $V_L = \sqrt{3} V_p$
 $I_L = \sqrt{3} I_p$



for Page 20-21: assume all are balanced.

Take-aways: V_p is the effective or rms value of phase voltage

Δ -Y

$$\begin{aligned} \mathbf{V}_{ab} &= V_p \angle 0^\circ \\ \mathbf{V}_{bc} &= V_p \angle -120^\circ \\ \mathbf{V}_{ca} &= V_p \angle +120^\circ \end{aligned}$$

Same as line currents


Same as phase voltages

$$\begin{aligned} \mathbf{I}_a &= \frac{V_p \angle -30^\circ}{\sqrt{3} Z_Y} \\ \mathbf{I}_b &= \mathbf{I}_a \angle -120^\circ \\ \mathbf{I}_c &= \mathbf{I}_a \angle +120^\circ \end{aligned}$$

magnitude

$$I_L = I_P$$

$$V_L = V_P$$

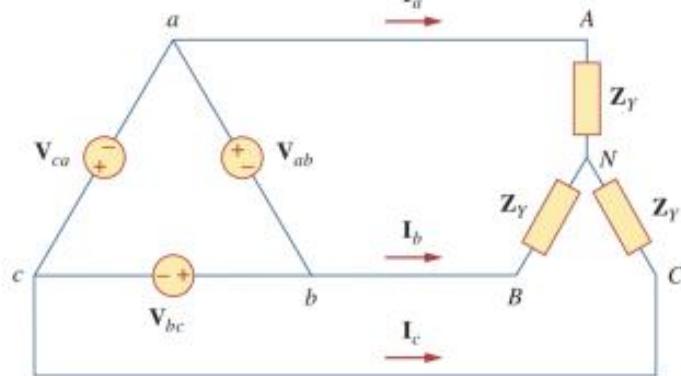

COPY

Δ - Δ

$$\begin{aligned} \mathbf{V}_{ab} &= V_p \angle 0^\circ \\ \mathbf{V}_{bc} &= V_p \angle -120^\circ \\ \mathbf{V}_{ca} &= V_p \angle +120^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{I}_{AB} &= \mathbf{V}_{ab}/Z_\Delta \\ \mathbf{I}_{BC} &= \mathbf{V}_{bc}/Z_\Delta \\ \mathbf{I}_{CA} &= \mathbf{V}_{ca}/Z_\Delta \end{aligned}$$


Same as phase voltages

$$\begin{aligned} \mathbf{I}_a &= \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ \\ \mathbf{I}_b &= \mathbf{I}_a \angle -120^\circ \\ \mathbf{I}_c &= \mathbf{I}_a \angle +120^\circ \end{aligned}$$

magnitude:

$$V_L = V_P$$

$$I_L = \sqrt{3} I_P$$

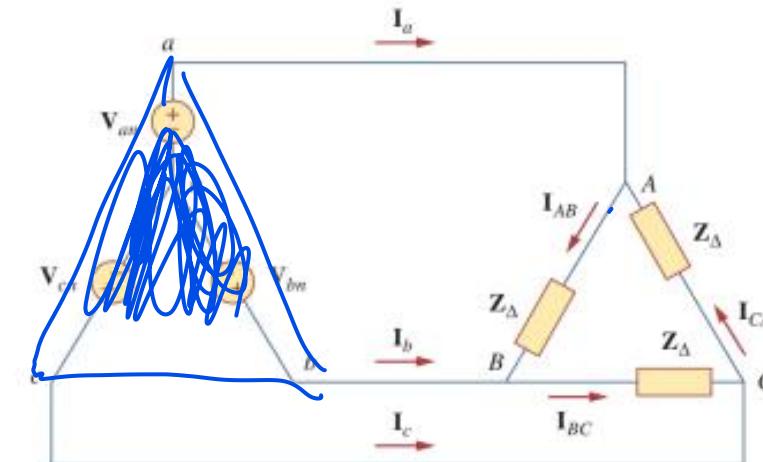

Take-aways:

Power analysis in Three-phase circuits

COPY

- Total instantaneous/average power

$$\bullet P = 3V_{Prms}I_{Prms} \cos(\angle Z)$$

You can always use this

- Total reactive power

$$\bullet Q = 3V_{Prms}I_{Prms} \sin(\angle Z)$$

- Total complex power

$$\bullet S = \widetilde{3V_{Prms}} \widetilde{I_{Prms}}^*$$

If you want to use this
make sure it's Y-Y / Δ-Δ.

- In particular, for Y-Y and Δ-Δ structures:

$$\bullet P = 3V_{Prms}I_{Prms} \cos(\angle Z) = \sqrt{3}V_{Lrms}I_{Lrms} \cos(\angle Z)$$

Exercise 4


(Prof.Chen's slides, chapter 12, example 12.8)

Two balanced loads are connected to a 240-kV rms 60-Hz line, as shown in Fig. 12.22(a).

Load 1 draws 30 kW at a power factor of 0.6 lagging, while load 2 draws 45 kVAR at a power factor of 0.8 lagging.

Assuming the **abc** sequence, determine:

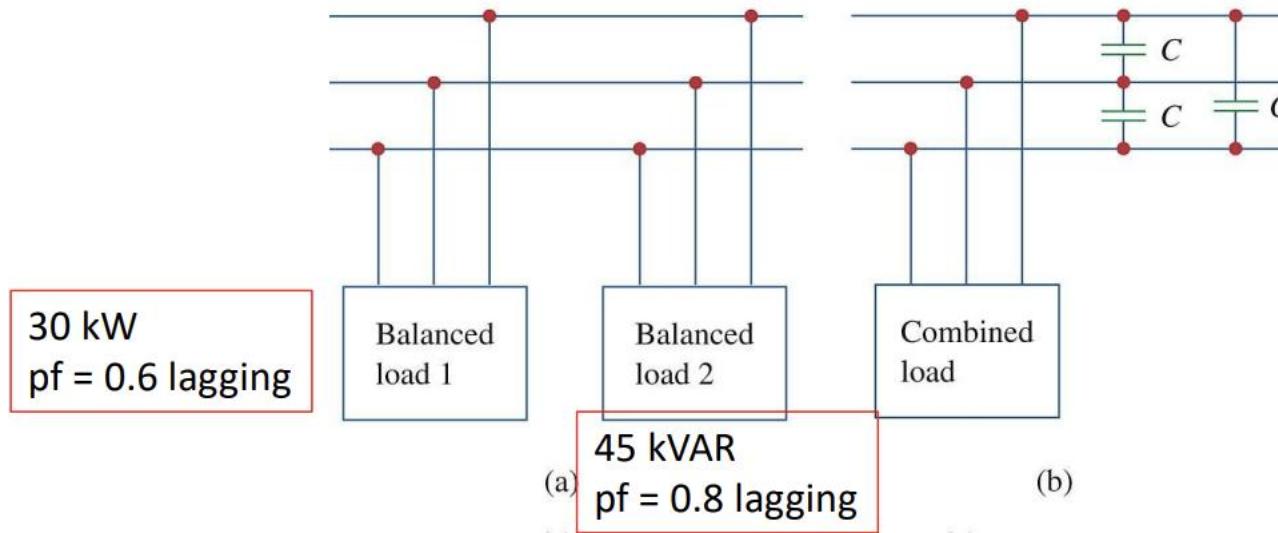- the complex, real, and reactive powers absorbed by the combined load,
- the line current
- the kVAR rating of the three capacitors -connected in parallel with the load that will raise the power factor to 0.9 lagging and the capacitance of each capacitor.



$$(a) V_L = 240 \text{ kV}$$

$$\boxed{\text{recall } Pf = \frac{P}{|S|}}$$

$$\cos \theta_1 = 0.6 \Rightarrow \tan \theta_1 = \frac{4}{3}$$

$$S_1 = P_1 + j Q_1$$

$$= P_1 + j P_1 \tan \theta_1$$

$$= 30 + j 40 \text{ (kVA)}$$

$$\text{Similarly, } S_2 = P_2 + j Q_2 = 60 + j 45 \text{ (kVA)}$$

$$S = S_1 + S_2 = 90 + j 85 \text{ (kVA)}$$

$$S = 90 + j 85 \text{ (kVA)}$$

$$P = 90 \text{ (kW)}$$

$$Q = 85 \text{ (kVAR)}$$

pay attention to the units!

$$(b) \text{ phase as whole: } \theta_1 = \tan^{-1} \left(\frac{85}{90} \right) = 43.36^\circ \quad * \text{ clarify degrees & radians}$$

$$I_L = \frac{P}{\sqrt{3} V_L \cos \theta_1} = \frac{90 \times 10^3}{\sqrt{3} \times 240 \times 10^3 \times \cos 43.36^\circ} = 0.298 \text{ (A)}$$

$$(c) \text{ new phase: } \theta_2 = \cos^{-1} 0.9 = 25.84^\circ$$

ΔQ contributed by capacitors:

$$\Delta Q = P(\tan \theta_1 - \tan \theta_2) = 90 \times (\tan 43.36^\circ - \tan 25.84^\circ) = 41.40 \text{ (kVAR)}$$

for a single Capacitor: $\Delta Q' = \Delta Q / 3 = 13.80 \text{ (kVAR)}$

Recall $|Q_C| = |I^2 X| = |V^2 / X^*| = wCV^2$, if purely capacitive.

$$\Rightarrow C = \frac{|\Delta Q'|}{wV^2 L} = \frac{13.8 \times 10^3}{2\pi \times 60 \times (240 \times 10^3)^2} = 635.51 \text{ PF}$$

pay attention to the difference between f and w

Assume Y-Y
or D-D
connected.

Tips for exams:

1. Get familiar with basic concepts
2. Get familiar with your calculator

Reference

- [1] 2024 Fall VE215 slides, Songliang Chen
- [2] 2024 Fall RC6, Yuting Cao
- [3] 2023 Fall Final RC
- [4] Fundamentals of Electric Circuits, 5th e, Sadiku, Matthew

THANK YOU