

# ECE2150J RC3

Jierui Xu

UM-SJTU JI

October 30, 2024

# Overview

Operational Amplifiers

Capacitors and Inductors

First-Order Circuit

# Overview

Operational Amplifiers

Capacitors and Inductors

First-Order Circuit

# Ideal Op-amp

Assumption:

- ▶ Infinite open-loop gain ( $A = \infty$ )
- ▶ Infinite input resistance ( $R_i = \infty$ )
- ▶ Zero output resistance ( $R_o = 0$ )
- ▶ (Does not mean that  $v_o = \infty$ )

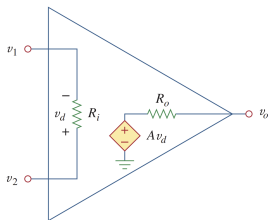


Figure: Op-amp's equivalent circuit

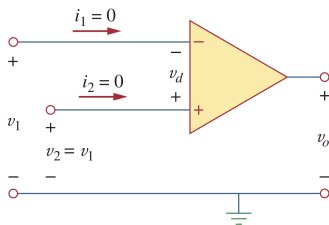


Figure: Symbol of ideal op-amp

# Ideal Op-amp

Characteristics of ideal op-amp:

- ▶ Open circuit at two input terminals ( $i_1 = i_2 = 0$ )
- ▶ Same voltage at two input terminals ( $v_1 = v_2$ )
- ▶ **(Does not mean that  $i_o = 0$ !)**

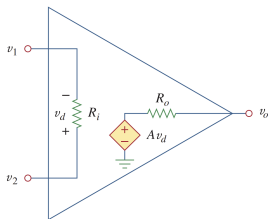


Figure: Op-amp's equivalent circuit


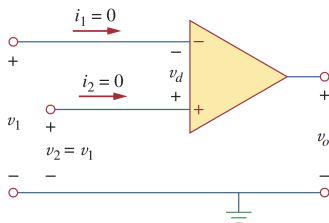


Figure: Symbol of ideal op-amp

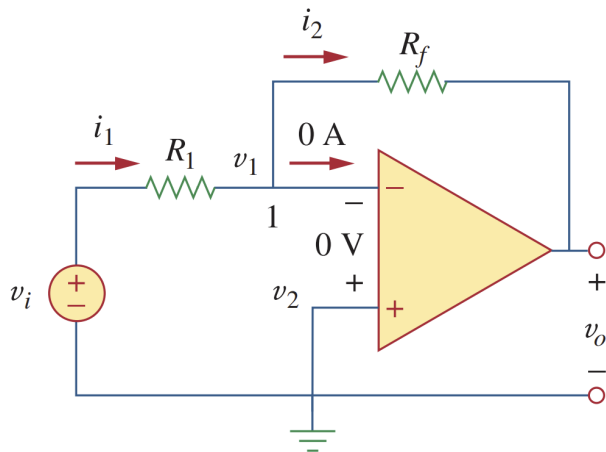
# Inverting Amplifier

$$A_v = \frac{v_o}{v_i} = -\frac{R_f}{R_1}$$



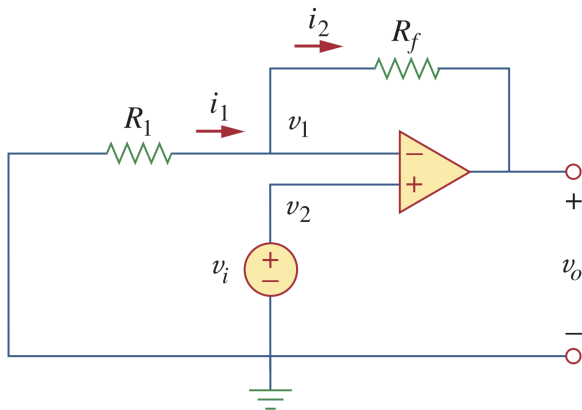
# Non-inverting Amplifier

$$A_v = \frac{v_o}{v_i} = 1 + \frac{R_f}{R_1}$$


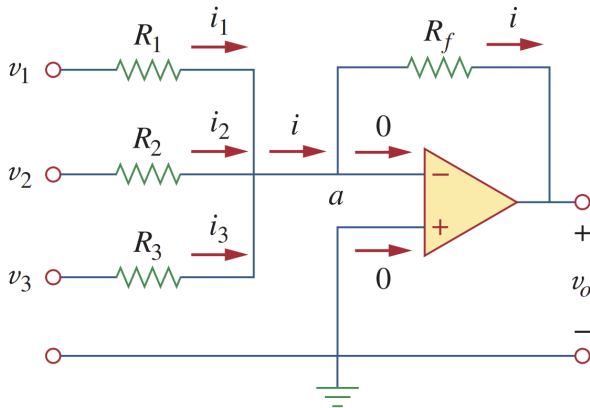
# Summing Amplifier

$$v_o = - \left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$





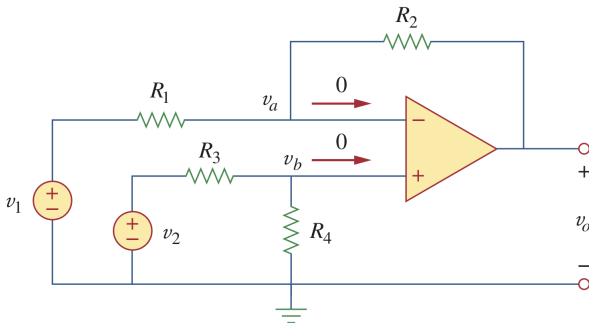
# Difference Amplifier


Check if  $R_1 = R_2$ ,  $R_3 = R_4$

$$v_o = \left( \frac{R_2}{R_1} + 1 \right) \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} v_1$$



# Cascaded Op Amps

## Gain of Cascaded Op Amp

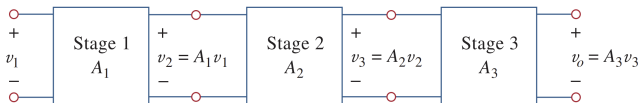

Original input signal is increased by the gain of the individual stage, and the final gain is the **product of all gains at each stage**.

$$A = \frac{v_o}{v_1} = \frac{v_2}{v_1} \cdot \frac{v_3}{v_2} \cdot \frac{v_o}{v_3} = A_1 A_2 A_3$$

## Basic Op-amp Circuits: Summary

For basic op-amp circuits:


Op-amp circuits	Input-output relationship
Inverting amplifier	$A = \frac{v_o}{v_i} = -\frac{R_f}{R_1}$
Non-inverting amplifier	$A = \frac{v_o}{v_i} = 1 + \frac{R_f}{R_1}$
Summing amplifier	$v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3\right)$
Difference amplifier	$v_o = \left[\left(\frac{R_2}{R_1} + 1\right)\left(\frac{R_4/R_3}{1+R_4/R_3}\right)\right]v_2 - \left[\frac{R_2}{R_1}\right]v_1$

For complicated op-amp circuits:

- ▶ Identify basic op-amp circuits within it
- ▶ Use the formula for cascaded op-amp circuit
- ▶ Be proficient in listing nodal analysis equations to obtain  $v_o/v_i$


# Exercise 1

Find  $v_o$ .

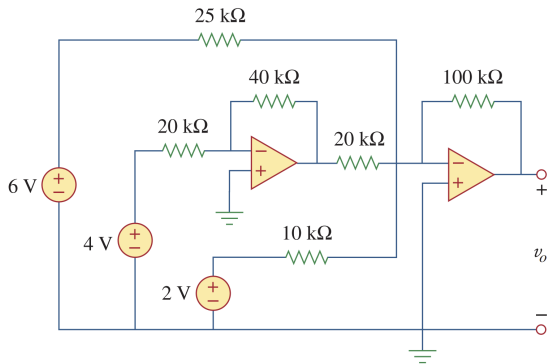
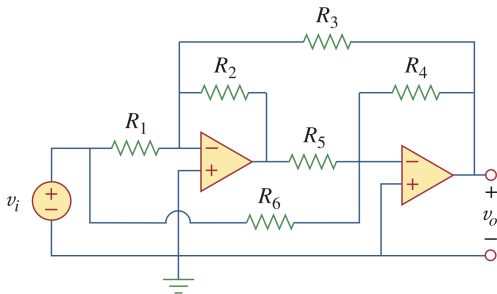
## Exercise 2

Determine the gain  $v_o/v_i$  of the circuit.



# Overview



Operational Amplifiers

Capacitors and Inductors

First-Order Circuit

# Capacitors

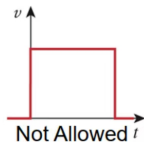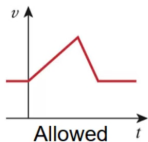1. **Open Circuit Property** When the voltage across a capacitor is not changing with time (**DC steady state**), the capacitor could be treated as an open circuit.
2. **Continuity property** The voltage on a capacitor must be continuous.




## 3. Capacitors IV relationship

$$i = C \frac{dv}{dt}$$

property 2 can be intuitively shown by property 3. If the voltage across the capacitor is not continuous, say  $\frac{dv}{dt} = \infty$ , which will cause  $i$  to be infinity.

# Capacitors

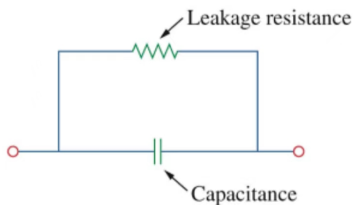
1. **An ideal capacitor will not dissipate energy.** It takes power from the circuit when storing energy in its electric field and returns previously stored energy when delivering power to the circuit.
2. **A real capacitor has a large leakage resistance**






# Capacitors in parallel & in series

## ► capacitors in parallel

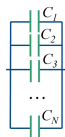

$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

## ► capacitors in series

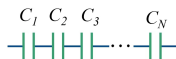

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4} + \dots + \frac{1}{C_N}$$

## Energy stored in Capacitors

**The instantaneous power** delivered to the capacitor is

$$p = vi = v\left(C \frac{dv}{dt}\right)$$

Therefore, **the total energy** stored in the capacitor is

$$w = \frac{1}{2}CV^2$$


# Inductors

1. **Short Circuit Property** When the current through an inductor is not changing with time (**DC steady state**), **the inductor could be treated as a short circuit in the circuit.**
2. **Continuity property** The current through a capacitor must be continuous.
3. **Inductor IV relationship**

$$v = L \frac{di}{dt}$$


# Inductors

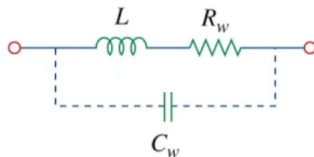1. **An ideal inductor will not dissipate energy.** It takes power from the circuit when storing energy in its magnetic field and returns previously stored energy when delivering power to the circuit.
2. **A real inductor has a significant winding resistance and a small winding capacitance**




# Inductors in parallel & in series

## ► inductors in parallel

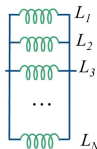

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4} + \dots + \frac{1}{L_N}$$

## ► inductors in series

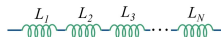

$$L_{eq} = L_1 + L_2 + L_3 + L_4 + \dots + L_N$$

## Energy stored in Inductors

**The instantaneous power** delivered to the inductor is

$$p = vi = (L \frac{di}{dt})i$$

Therefore, **the total energy** stored in the inductor is


$$w = \frac{1}{2}Li^2$$

# Summary of Capacitors and Inductors

	Capacitor	Inductor
Electric/magnetic	$q$	$\psi$
	$q=Cv$	$\psi=Li$
i-v (or v-i) relation	$i=C \times dv/dt$	$v=L \times di/dt$
energy	$1/2Cv^2$	$1/2Li^2$
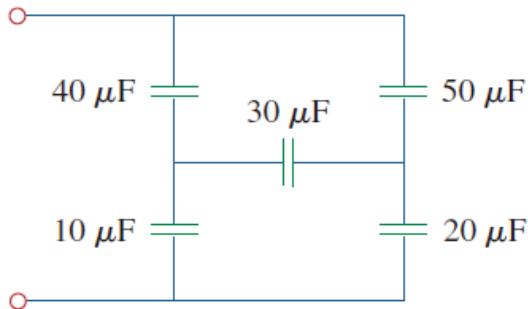
## Exercise 3



Obtain the equivalent capacitance of the network below.




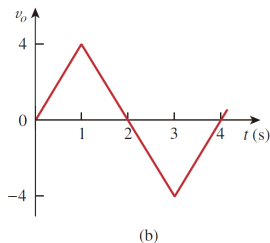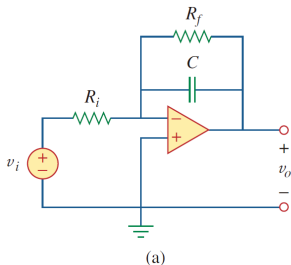
## Exercise 4

The output  $v_o$  of the op amp circuit in Fig.(a) is shown in Fig.(b). Let  $R_i = R_f = 1\text{ M}\Omega$  and  $C = 1\text{ }\mu\text{F}$ . Determine the input voltage waveform and sketch it.



## Exercise 4

# Overview


Operational Amplifiers

Capacitors and Inductors

First-Order Circuit

# Source-Free Circuits (I) Response

## Source-free RC

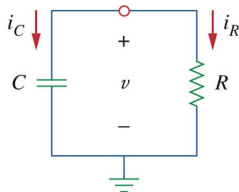

Voltage:  $v = v_0 e^{-t/RC}$


Time constant:  $\tau = RC$

Current:  $i_R = \frac{v}{R} = \frac{v_0}{R} e^{-t/\tau}$

Power:  $p = v i_R = \frac{v_0^2}{R} e^{-2t/\tau}$

Energy:  $w_R = \int_0^t p dt = \frac{1}{2} C v_0^2$

## Source-free RL

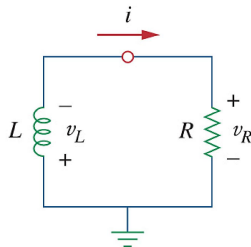

Current:  $i = i_0 e^{-t/(L/R)}$


Time constant:  $\tau = L/R$

Voltage:  $v_R = iR = \frac{i_0 R}{R} e^{-t/\tau}$

Power:  $p = v_R i = i_0^2 R e^{-2t/\tau}$

Energy:  $w_R = \int_0^t p dt = \frac{1}{2} L i_0^2$
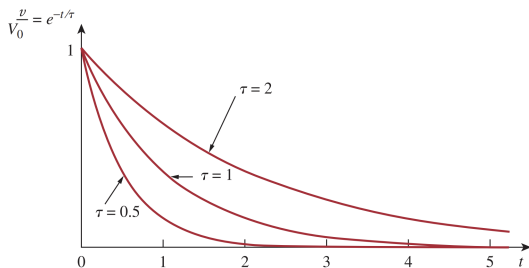
# Source-Free Circuits (II) Time Constant






	Source-free RC	Source-free RL
Time constant	$\tau = RC$	$\tau = L/R$
Relation to initial decay rate	$\frac{d}{dt}\left(\frac{v}{v_0}\right) = -1/\tau$	$\frac{d}{dt}\left(\frac{i}{i_0}\right) = -1/\tau$

- ▶ Time required for the response to decay to a factor of  $1/e$  or 36.8% of its initial value
- ▶ Indicates the initial decaying rate
- ▶ Assume complete decay after  $5\tau$

## Source-Free Circuits (III) General Steps

- ▶ Find the initial value  $v_0$ ,  $i_0$ .
- ▶ Find the time constant, i.e., find  $R_{eq}$ . ( $R_{eq}$  is the Thevenin or Norton equivalent resistance at the capacitor and inductor terminals.)
- ▶ Use the equation in the previous slide to get results.
- ▶ You can always use Mesh/Nodal analysis to calculate if you are not familiar with the steps above.
- ▶ (Of course, you need to remember that  $i = C \frac{dv}{dt}$  for capacitors and  $v = L \frac{di}{dt}$  for inductors!)

# Singularity Functions

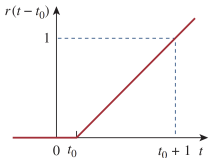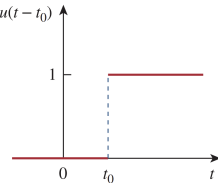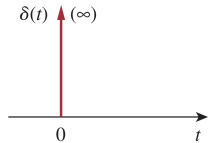Unit ramp	Unit step	Unit impulse
$r(t) = \begin{cases} 0, & t \leq 0 \\ t, & t > 0 \end{cases}$	$u(t) = \begin{cases} 0, & t \leq 0 \\ 1, & t > 0 \end{cases}$	$\delta(t) = \begin{cases} 0, & t \neq 0 \\ \text{Undef.}, & t = 0 \end{cases}$
		

Give a nice way to represent “Switch on/off” of the sources/part of circuits.

$$\delta(t) \xrightarrow{f} u(t) \xrightarrow{f} r(t)$$

## Exercise 5

Please plot the function diagram of the following singular function

$$f(t) = r(t + 1) + u(t - 2) - r(t - 3)$$


and calculate

$$\int_{-\infty}^{+\infty} f'(t) \delta(t - 5) dt$$



# Circuits with Step Input (I) Response

## Step-input RC

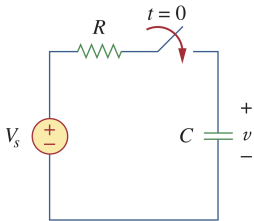


Initial condition:  
 $v(0^+) = v(0^-) = V_0$

Equation:  
(KVL)  $(C \frac{dv}{dt} R + v = V_s)$

Response:  
 $v(t) = V_s + (V_0 - V_s)e^{-t/\tau}$

## Step-input RL

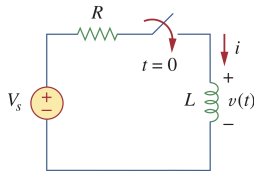

Initial condition:  
 $i(0^+) = i(0^-) = I_0$

Equation:  
(KCL)  $iR + L \frac{di}{dt} = V_s$

Response:  
 $i(t) = \frac{V_s}{R} + (I_0 - \frac{V_s}{R})e^{-t/\tau}$

## Circuits with Step Input (II) General Steps

- ▶ General form:  $x(t) = x(\infty) + (x(0) - x(\infty))e^{-t/\tau}$ .
- ▶ Step response = natural response + forced response, where natural response is  $x(0)e^{-t/\tau}$ , forced response is  $x(\infty)(1 - e^{-t/\tau})$ .
- ▶ Step response = transient state response + steady state response, where transient response is  $(x(0) - x(\infty))e^{-t/\tau}$ , steady state response is  $x(\infty)$ .
- ▶ Steps to find step response:
  - ▶ Find  $x(0)$ .
  - ▶ Find  $x(\infty)$ .
  - ▶ Find  $\tau$ .
- ▶ Still, you can find step response using mesh/nodal analysis. By solving the differential equation, you will find that natural response is the homogeneous solution of the equation, while the forced response is the particular solution.

# General Formula for First-Order Circuits

General formula for RC:


$$v(t) = v(\infty) + [v(0^+) - v(\infty)] e^{-t/\tau}$$

General formula for RL:

$$i(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-t/\tau}$$
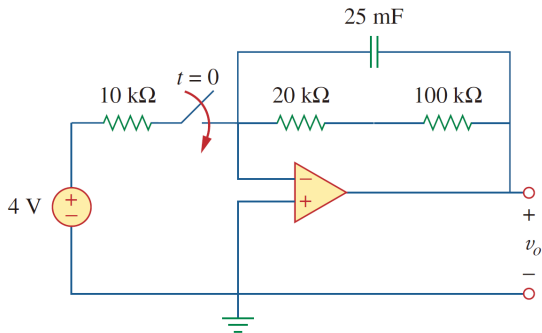
## Exercise 6

For the op amp circuit below, find  $v_o(t)$  for  $t > 0$ .



## Exercise 6

# References

1. 2024 Fall VE215 slides, Sung-Liang Chen
2. Fundamentals of Electric Circuits, 5th e, Sadiku, Matthew
3. 2023 Summer RC3, Erdao Liang, Chongye Yang
4. 2024 Summer RC3, Runting Zhang

Thank you!