

Q1

1.1 D. 4'

1.2. $\gamma \rightarrow \Delta$ change.

$$Z_1 = \frac{1}{j\omega L_0}$$

$$Z_2 = 3Z_1 \Rightarrow Z_2 = \frac{1}{j\omega \frac{L_0}{3}} \quad 2'$$

$$\Rightarrow C = \frac{L_0}{3} = \frac{100}{3} \mu F. \quad 2'$$

1.3 $\frac{I_1}{I_2} = \frac{V_2}{V_1} = \frac{220}{1100} \quad 1'$

$$I_1 = 10 A$$

$$\Rightarrow I_2 = 50 A \quad 3'$$


1.4 C 2'

reasoning: 4'

(reasonable ones would be ok).

eg. use circuit transformation:

$$n = \frac{n_2}{n_1}$$

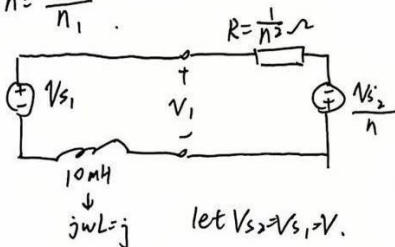

$$I = \frac{V_{s1} + \frac{V_{s2}}{n}}{\frac{1}{n^2} + j} = \frac{(n^2 + n)V(1 - n^2j)}{1 + n^4}$$

$$P = I^2 R = \left[\frac{(n^2 + n)V}{1 + n^4} \right]^2 (1 + n^4) \cdot \frac{1}{n^2} = \frac{(n+1)^2}{1 + n^4} V^2$$

$$\frac{dP}{dn} = \frac{2(n+1)(1+n^4) - 4n^3(n+1)^2}{(1+n^4)^2} \quad \frac{dP}{dn} = 0$$

$$\Rightarrow n = 0.7167 \quad \frac{n_2}{n_1} < 1 \Rightarrow n_2 < n_1$$

1.5 6'

(reasonable provement would be ok)

eg. Let $V_i = V_m \cos \omega t = V_m \angle 0^\circ$

$$Z_C = \frac{1}{j\omega C}$$

$$I = \frac{V_i}{R + Z_C} = \frac{V_m}{R + \frac{1}{j\omega C}} = \frac{V_m \cdot j\omega C}{j\omega RC + 1}$$

$$V_o = I Z_C = \frac{V_m}{j\omega RC + 1}$$

$$= \frac{V_m (-j\omega RC + 1)}{(j\omega RC + 1)(-j\omega RC + 1)}$$

$$= \frac{V_m}{1 + \omega^2 R^2 C^2} (1 - j\omega RC)$$

$$\text{Arg}(1 - j\omega RC) = -90^\circ \Rightarrow \omega = \infty \text{ rad.s}^{-1}$$

It is not achievable.

$$|V_o| = \frac{|V_m|}{|j\omega RC + 1|} = 0$$

Q2

Q2

(1) $V_R = 1.5\Omega \cdot 2.204 = 3V$
 $V_{\#2} = \frac{S}{I} = \frac{1}{2+j} V$
 $V_S = V_R + V_{\#2} = 3.5 + j1 = \frac{\sqrt{53}}{2} \angle 15.95^\circ V$

(2) If Maximum power transfer
 $S_{other} = S_{Load}^* = 14 + j4$
 $S_{left} = 7 + j2 = S_{other} - S_{Box\#2} = -I^2 R$
 $S = I^2 Z = \left(\frac{V_S}{Z}\right)^2 \cdot 8 = 7 + j2$
 $\Rightarrow Z = 1.75 + j0.5 \Rightarrow \omega = 25 \text{ rad}$
 $f = 3.98 \text{ Hz}$

If you use any ~~use~~ practical way and making effort toward the final answer, 2 points / 1 point will be added.
 If you get the final result without calculation error 1 point will be added.


(3) $S_{total} = 28V$
 $\text{pf} = 0.9 \Rightarrow \theta = 25.84^\circ$
 $Q' = S \cdot \tan \theta = 13.56 \text{ VAR}$
 $Q = \frac{V^2}{\omega L} \Rightarrow L = \frac{V^2}{\omega Q} = 0.0894$
 $C = \frac{Q}{\omega V^2} = 0.041 F$
 Any one is right
 +2 additional points.

Above is the intended solution of the Question 2 and its design. It is solvable by the process above, but at the same time we encountered that the question has the design issue: If we use Thevenin equivalent model, the question is not solvable, meaning that there is the design issue.

We marked your answer (a) as above. However, for (b) and (c), we first provided **full credits**. And, we took into your detailed answers and gave **additional points on your approach/conceptual thought**.

Q3

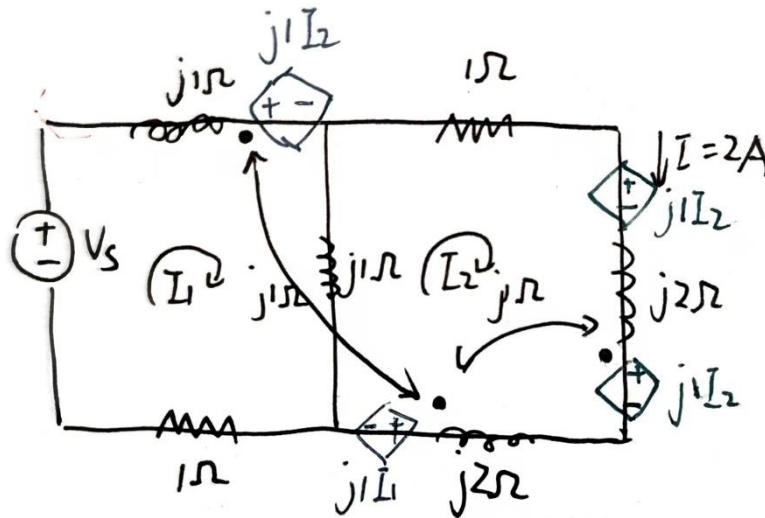(a) The diagram for part (a) is shown below:



(b) For part (b), the simplified equations are as follows:

$$\begin{cases} V_s = (2j + 1)I_1, \\ (7j + 1)I_2 = 0. \end{cases}$$

From the second equation, we get $I_2 = 0$. However, this contradicts the conditions stated in the problem.

Rubrics:

Case 1. No modification and derived right KVL. **Full marks.**

Case 2. Modification and derived right KVL. We checked your **consistency** of the answer in (a) and (b). e.g. If you modified (a) part due to the contradiction, and KVL is derived in a right way. **Full marks.**

Case of deductions:


Case 1. No modification with wrong answer in (a). 2 points were deducted for each incorrect voltage source (including direction and magnitude). If the answer includes ω , each will only get 1 point.

Case 2. For (b), if KVL is not used, 0 points will be awarded.

Case 3. For (b), if KVL equations do not match the diagram in (a), 3 points will be deducted for each incorrect equation.

Full marks for (c).

Q4

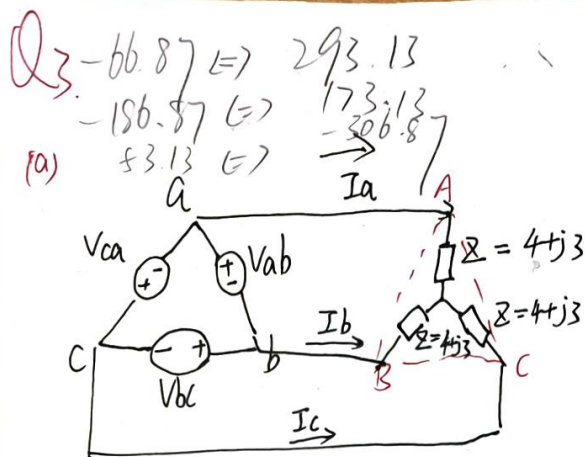

$$\Rightarrow \left\{ \begin{array}{l} V_{AB} = V_{ab} = 8.66 \angle 0^\circ \text{ V} \\ V_{CA} = V_{ca} = 8.66 \angle 120^\circ \text{ V} \\ V_{BC} = V_{bc} = 8.66 \angle -120^\circ \text{ V} \end{array} \right\} 3'$$

$$\Rightarrow \left\{ \begin{array}{l} I_a = 1.00 \angle -66.87^\circ \text{ A} \\ I_b = 1.00 \angle -186.87^\circ \text{ A} \\ I_c = 1.00 \angle 53.13^\circ \text{ A} \end{array} \right\} 1'$$

(a) full mark is assigned if results are correct.

Otherwise, $Z_\Delta = 3Z_Y = 12 + 9j$ 1', or the calculation for $\hat{I}_a, \hat{I}_b, \hat{I}_c$ each earns 1' 1' maximum

(b) $S_{\text{per-phase}} = V_{\text{rms}} I_{\text{rms}}^* = V_{p\text{-load}} I_{p\text{-load}}^* = 15 \angle 36.87^\circ \text{ [VA]}$

$S_{\text{total}} = 3 S_{\text{per-phase}} = 15 \angle 36.87^\circ \text{ [VA]} + 2$

(c) $\theta = 36.87^\circ$ (or $12 + 9j$)

$Pf = \cos \theta = \frac{0.8}{+1} \quad \text{lagging} \quad \frac{+2}{+2}$

If this is wrong 3' is deducted.

(c): no process point.

$\Delta-Y: V_L = V_P \Rightarrow \tilde{V}_{AB} = \tilde{V}_{ab}$

$\tilde{V}_{ab} = 8.66 \angle 0^\circ$

$\tilde{V}_{bc} = 8.66 \angle -120^\circ$

$\tilde{V}_{ca} = 8.66 \angle +120^\circ$

Replace the Y-connected load with its equivalent Δ -connected load and recall that for a Δ -connected load,

$\hat{I}_a = \hat{I}_{AB} \sqrt{3} \angle -30^\circ = \frac{\tilde{V}_{AB}}{Z_\Delta} \sqrt{3} \angle -30^\circ$

$Z_\Delta = 3Z_Y = 12 + 9j$ (2)

$\hat{I}_b = \hat{I}_a \angle -120^\circ = \frac{\tilde{V}_{AB}}{Z_\Delta} \sqrt{3} \angle -150^\circ$

$\hat{I}_c = \hat{I}_a \angle +120^\circ = \frac{\tilde{V}_{AB}}{Z_\Delta} \sqrt{3} \angle 90^\circ$

process points: 1'
 (b): $V_{\text{rms}} I_{\text{rms}}^*$ 1'

$S_{\text{total}} = 3 S_{\text{per}}$
 or $S_{\text{total}} = 3 V_P I_P \cos \theta$ 1' maximum

Rubrics

(a) $V_L = V_P$ of the source, and followed this to calculate three line sources -----3point

Then , calculate I_a, I_b, I_c ----3points

The full marks were given as long as the result (= **value+unit**) is correct. If one or more unit is missing or wrong, 1 point is deducted (did not deduct repeatedly).

If the result is wrong, a maximum 1 point for process can be assigned, as long as an equation for calculating I, V, Z is shown correctly.

(b)

$$S_{phase} = V_{pload} * (I_{pload})^* = 4 + 3j[VA] \text{-----2point}$$

$$S_{total} = 3 * S_{phase} = 12 + 9j[VA] \text{-----1point}$$

The full marks was given as long as the result (= **value+unit**) is correct. If one or more unit is missing or wrong, 1 point is deducted (did not deduct repeatedly).


If the result is wrong, a maximum1 point for process can be assigned, as long as an equation such as $S_{total} = 3S_{per_phase}$ is shown correctly.

(c)

No process point is assigned for this sub-question, $pf = \cos(36.87) = 0.8$ ---- 1point
lagging-----2 point

Q5

Q5.

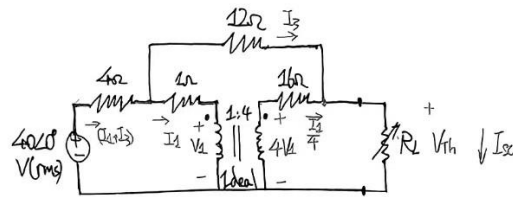

(a) Open circuit voltage:

$$\begin{cases} 40\angle 0^\circ = 4(I_1 + I_3) + 12I_3 + V_{th} & 1' \\ \frac{I_1}{4} = -I_3 & 1' \end{cases}$$

$$\Rightarrow V_{th} = 40\angle 0^\circ \quad 2'$$

Short circuit current:

$$\begin{cases} 40\angle 0^\circ = 4(I_1 + I_3) + I_1 + V_1 & 1' \\ 4V_1 = 16 \cdot \frac{I_1}{4} & 1' \\ 40\angle 0^\circ = 4(I_1 + I_3) + 12I_3 & 1' \end{cases}$$

$$\Rightarrow I_1 = 6A \quad 1' \quad I_3 = 1A \quad 1'$$

$$I_{sc} = \frac{I_1}{4} + I_3 = 2.5A \quad 1'$$

$$(b) R_{th} = \frac{V_{th}}{I_{sc}} = 16\Omega \quad 2'$$

(c) When $R_L = R_{th} = 16\Omega \quad 2'$

$$P_{max} = \frac{1}{2} I^2 R_L = \left(\frac{40\angle 0^\circ}{32} \right)^2 \times 16 = 125W \quad 2'$$

* If you calculated as $P_{max} = I^2 R \quad -1'$

maximum avg power refers to the load

(d)

$$\begin{cases} 40\angle 0^\circ = 4(I_1 + I_3) + 12I_3 + 20\angle 0^\circ & 1' \\ 4V_1 = 16\Omega \cdot \left(\frac{I_1}{4} \right) + 16\left(\frac{I_1}{4} + I_3 \right) & 1' \end{cases}$$

$$\Rightarrow I_1 = 6A \quad 1' \quad I_3 = -0.25A \quad 1' \quad I = I_1 + I_3 = 5.75A$$

$$P = VI = 40\angle 0^\circ \cdot (6 - 0.25) = 230W \quad 2'$$