

Homework 2

Coverage: Chapter 4 and 5

Due date: 5th November 2024

Problem 1

Find v_x in the below circuit:


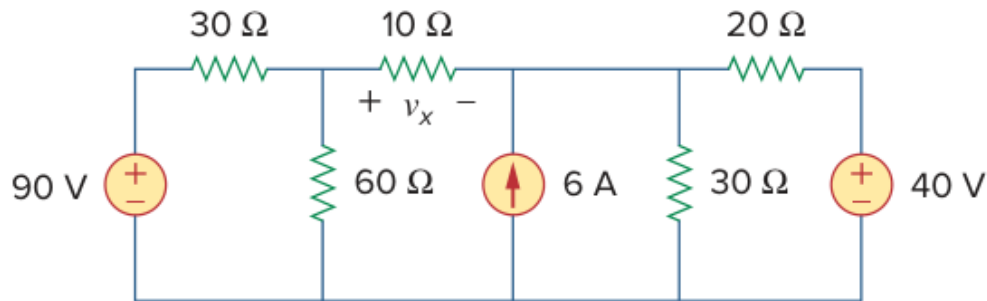


Figure 1: Circuit for Problem 1

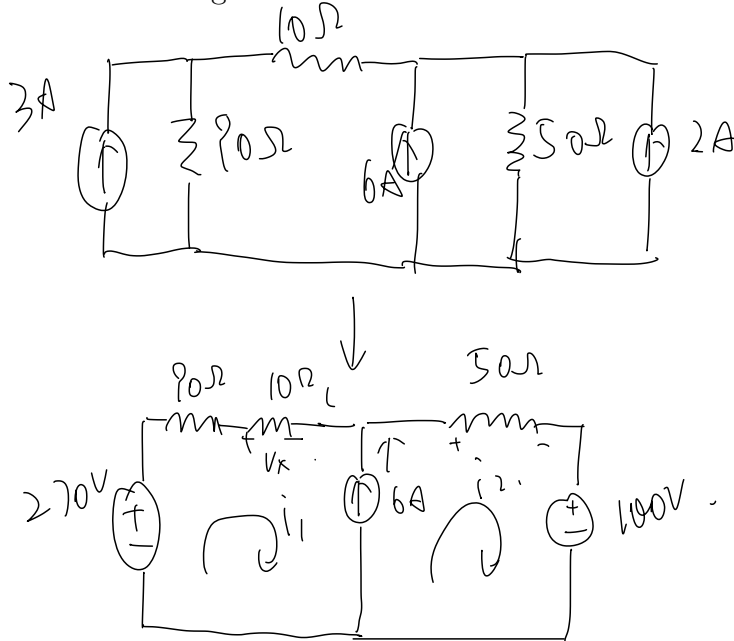

$$\begin{cases} i_1 + 6 = i_2 \\ -270 + 90i_1 + 10i_1 + 50i_2 + 100 = 0 \end{cases}$$

$$\begin{cases} i_1 = -\frac{13}{15} \text{ A} \\ i_2 = \frac{21}{15} \text{ A} \end{cases} \quad V_x = i_1 \cdot 10\Omega = -8.67 \text{ V}$$

Problem 2

Use source transformation to find i_x in the circuit


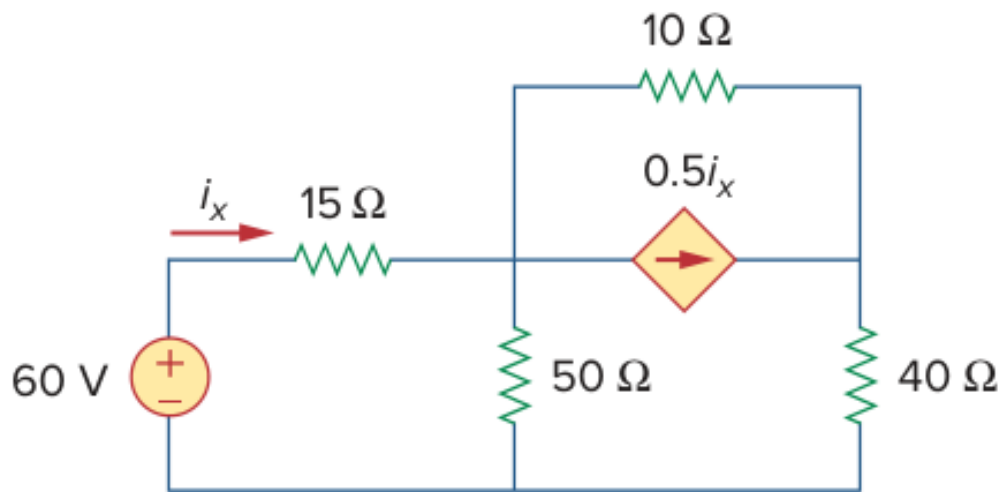


Figure 2: Circuit for Problem 2

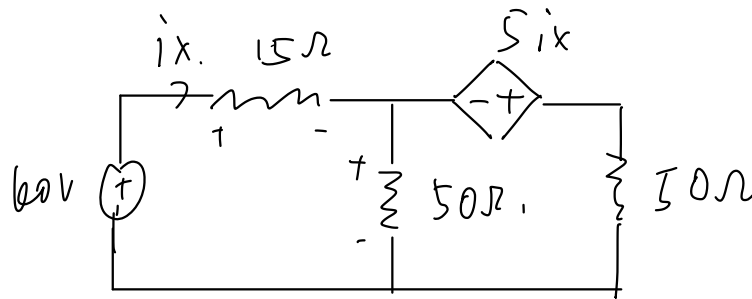


$$\begin{cases} -60 + (5i_x + 50(i_x - i_2)) = 0 \\ -5i_x + 50i_2 + 50(i_2 - i_x) = 0 \end{cases} \quad \begin{cases} 65i_x - 50i_2 = 60 \\ -55i_x + 100i_2 = 0 \end{cases}$$

$$\begin{cases} i_x = 1.6 \text{ A} \\ i_2 = 0.88 \text{ A} \end{cases}$$

Problem 3



Find the Thevenin equivalent of a-b

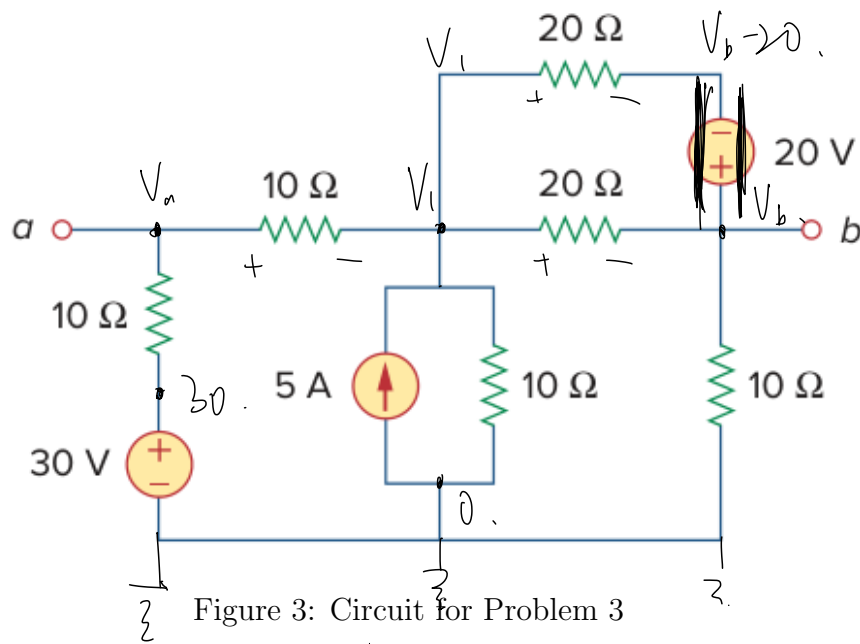

$$\begin{cases} \frac{V_a - V_1}{10} + \frac{V_1}{10} + \frac{V_1 - V_b}{20} + \frac{V_1 - V_b + 20}{20} = 0 \\ \frac{V_1 - V_b + 20}{20} + \frac{V_1 - V_b}{20} = \frac{V_b}{10} \\ \frac{V_a - 20}{10} + \frac{V_a - V_b}{10} = 0 \end{cases}$$

$$\begin{cases} V_a = 20V \\ V_b = 20V \\ V_1 = 20V \end{cases}$$

$$V_{Th} = 20V - 20V = 10V$$

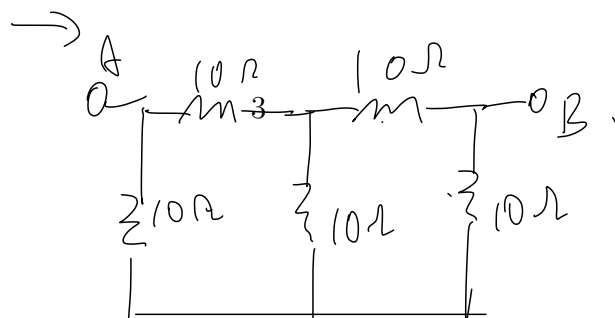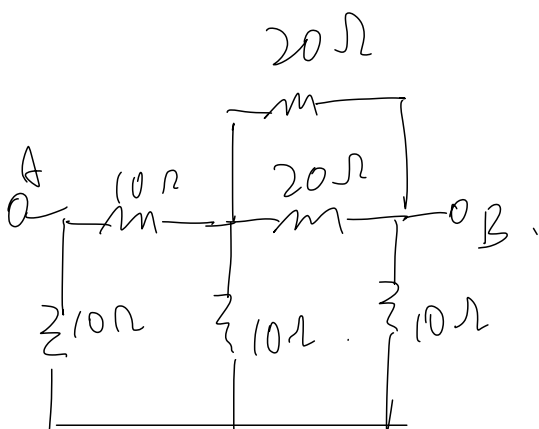

$$R_{Th} = 10\Omega \parallel 10\Omega + 10\Omega \parallel 10\Omega = 10\Omega$$

Problem 4

Find the maximum power transferred to resistor R


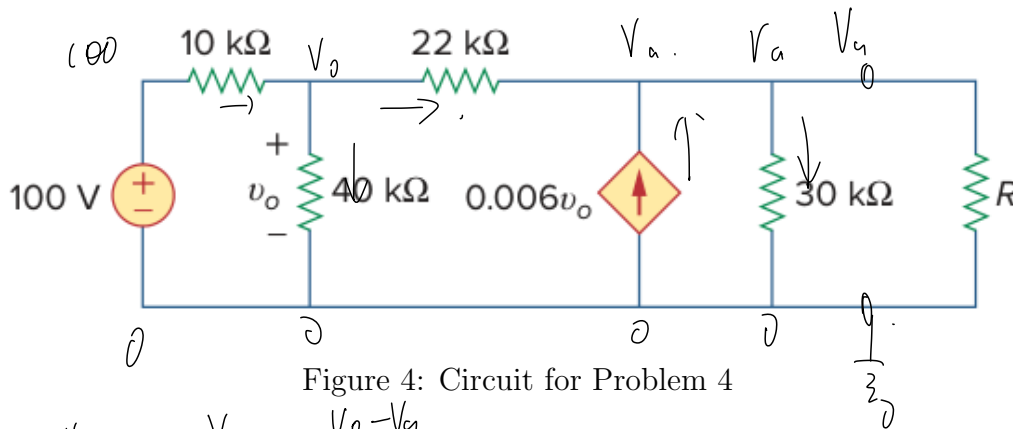


Figure 4: Circuit for Problem 4

$$\left\{ \begin{aligned} \frac{100 - V_o}{10k} &= \frac{V_o}{40k} + \frac{V_o - V_g}{22k} \\ \frac{V_o - V_g}{22k} + 0.006V_o &= \frac{V_g}{30k} \end{aligned} \right.$$
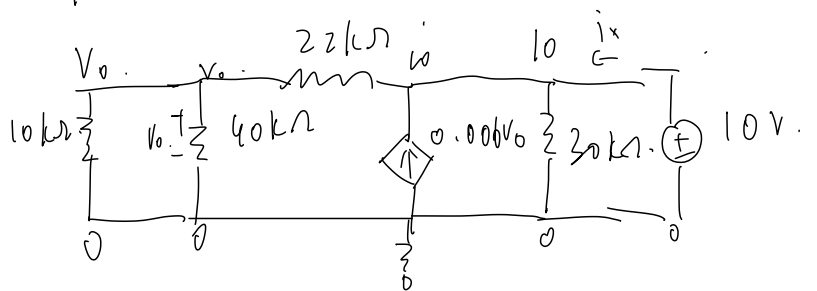
$$\left\{ \begin{aligned} V_a &= -231.3V \\ V_o &= -3.0V \end{aligned} \right. \quad V_{Th} = -231.3V$$




$$\left\{ \begin{aligned} \frac{V_o}{10k} + \frac{V_o}{40k} &= \frac{10 - V_o}{22k} \\ \frac{10 - V_o}{22k} + \frac{V_o}{30k} &= 0.006V_o + i_x \end{aligned} \right.$$

$$\left\{ \begin{aligned} V_o &= \frac{8}{3} \\ i_x &= -0.015A \end{aligned} \right. \quad 4$$

$$R_{Th} = \frac{10}{i_x} = \frac{10}{-0.015} = -666.7\Omega < 0$$

Therefore, $P = \frac{V_{Th}^2}{(R_{Th} + R)^2} \cdot R = \frac{V_{Th}^2}{\frac{R_{Th}^2}{R} + 2R_{Th} + R}$, if $R = -R_{Th} = 666.7\Omega$, P reaches the maximum, $P \rightarrow \infty$, So Pm DNE.

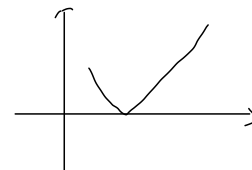

Problem 5

Find v_o and i_o in the circuit

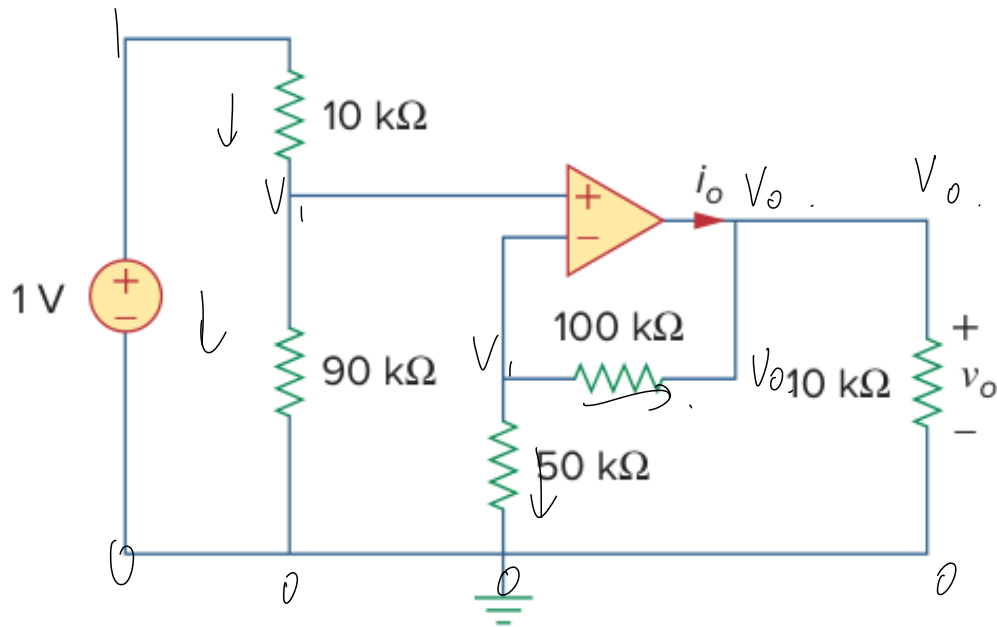


Figure 5: Circuit for Problem 5

$$\begin{cases} \frac{1 - V_1}{10k} = \frac{V_1}{90k} \\ \frac{V_1}{50k} + \frac{V_1 - V_o}{100k} = 0 \end{cases}$$

$$\begin{cases} V_1 = 0.9V \\ V_o = 2.7V \end{cases}$$

$$\begin{aligned} i_o &= \frac{V_o}{10k} + \frac{V_o - V_1}{100k} \\ &= 2.8 \times 10^{-4} A \end{aligned}$$

Problem 6

Find voltage gain v_o/v_i of the circuit

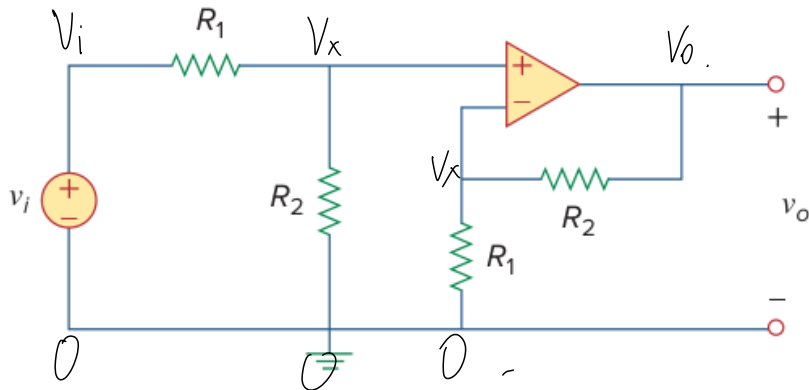


Figure 6: Circuit for Problem 6

$$\left\{ \begin{array}{l} \frac{V_i - V_x}{R_1} = \frac{V_x}{R_2} \\ \frac{V_x}{R_1} + \frac{V_x - V_o}{R_2} = 0 \end{array} \right.$$

$$\frac{V_o}{V_i} = \frac{R_2}{R_1}$$

$$V_i R_2 - V_x R_2 = V_x R_1$$

$$V_x = \frac{V_i R_2}{R_1 + R_2}$$

$$V_x R_2 + V_x R_2 - V_o R_1 = 0$$

$$V_x = \frac{V_o R_1}{R_1 + R_2}$$

$$V_i R_2 = V_o R_1$$

$$\frac{V_o}{V_i} = \frac{R_2}{R_1}$$