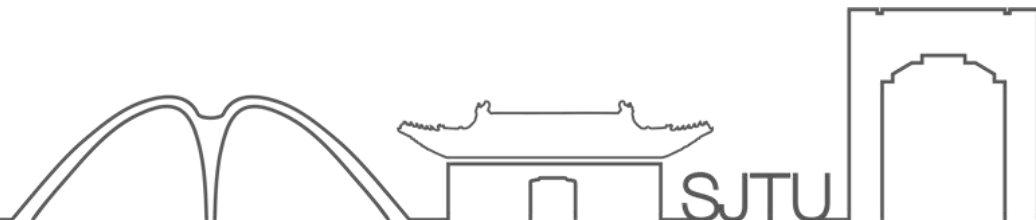




JOINT INSTITUTE
交大密西根学院

VE215 Final RC Part 1

Jiang Naicheng姜乃成
2024/12/9



Contents

Sinusoids and Phasors

Sinusoidal steady-state analysis

Three Phase Circuits



JOINT INSTITUTE
交大密西根学院

Alternating Current(AC) Circuits:

Circuits driven by sinusoidal current or voltage sources

$$v(t) = V_m \sin(\omega t + \phi)$$


where

V_m : amplitude

ω : angular frequency

ϕ : initial phase

Leads & Lags:

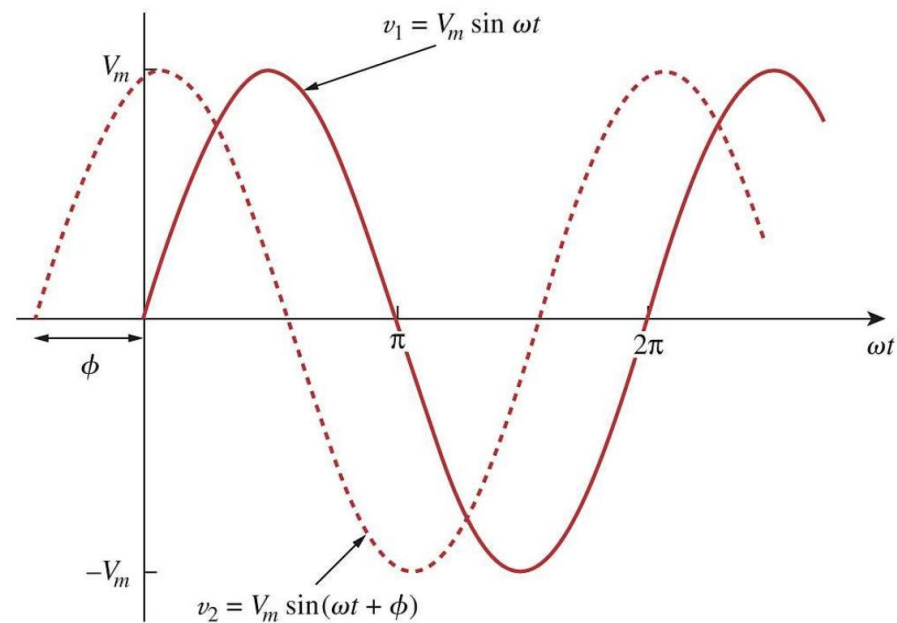

Phasors:

$$v(t) = V_m \cos(\omega t + \phi) = \text{Re}(\tilde{V} e^{j\omega t})$$

where

$$\tilde{V} = V_m e^{j\phi} = V_m \angle \phi$$

is the **phasor** representation, polar form

while $V = a + bj$, is the so called rectangular form

Phasor Diagram:

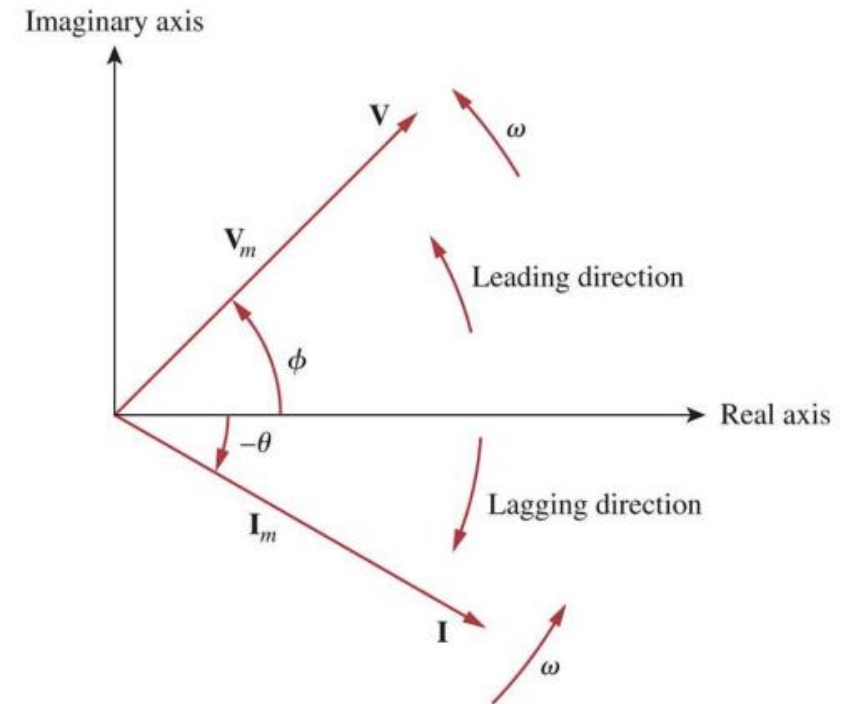


Figure 9.8 A phasor diagram.

$$v(t) = V_m \cos(\omega t + \phi) \Leftrightarrow \tilde{V} = V_m \angle \phi$$

A little more about lag, lead, and in phase: sinusoidal

Let us examine the two sinusoids

$$v_1(t) = V_m \sin \omega t$$

$$v_2(t) = V_m \sin(\omega t + \phi)$$

shown in Fig. 9.2.

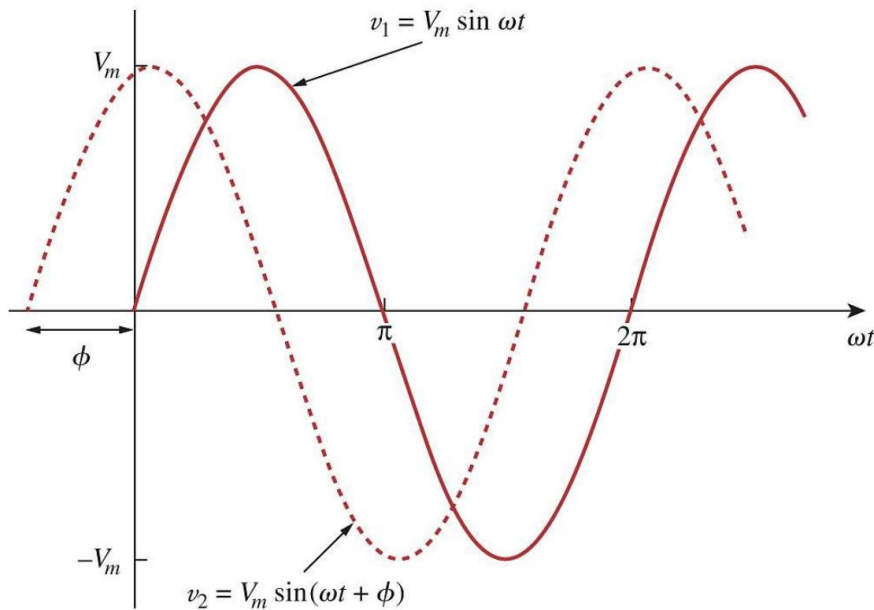


Figure 9.2 Two sinusoids with different phases.

The starting point of v_2 in Fig. 9.2 occurs first in time. Therefore, we say that v_2 leads v_1 by ϕ or that v_1 lags v_2 by ϕ . If $\phi \neq 0$, we say that v_1 and v_2 are *out of phase*. If $\phi = 0$, then v_1 and v_2 are said to be **in phase**.

Recall:

$$\sin(x) = \cos(x - \pi/2)$$

No need to differentiate sine/cosine forms here!

TABLE 9.2

Summary of voltage - current relationships

Element	Time domain	Frequency domain
R	$v = Ri$	$\tilde{V} = R\tilde{I}$
L	$v = L \frac{di}{dt}$	$\tilde{V} = j\omega L\tilde{I}$
C	$i = C \frac{dv}{dt}$	$\tilde{V} = \frac{1}{j\omega C}\tilde{I}$

About admittance and impedance:

$$Y = \frac{\tilde{I}}{\tilde{V}} = \frac{1}{Z}$$

The admittance can be written as

$$Y = G + jB$$

where

G : conductance

B : susceptance

The admittance, conductance, and susceptance are all measured in siemens.

$$Z = R + jX = |Z| \angle \theta$$

where

R : resistance

X : reactance

If $X > 0$, we say that the impedance is inductive or lagging since current lags voltage; If $X < 0$, we say that the impedance is capacitive or leading because current leads voltage.

The impedance, resistance, and reactance are all measured in ohms.

Equivalence Circuits

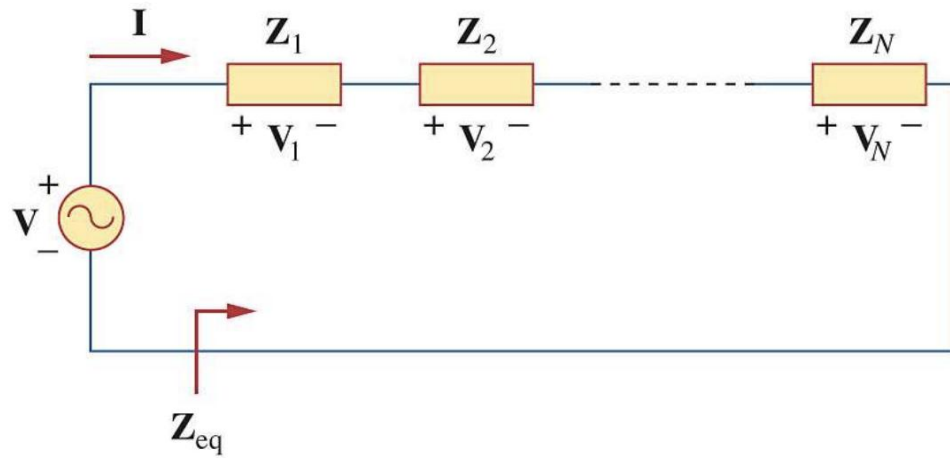


Figure 9.18 N impedances in series.

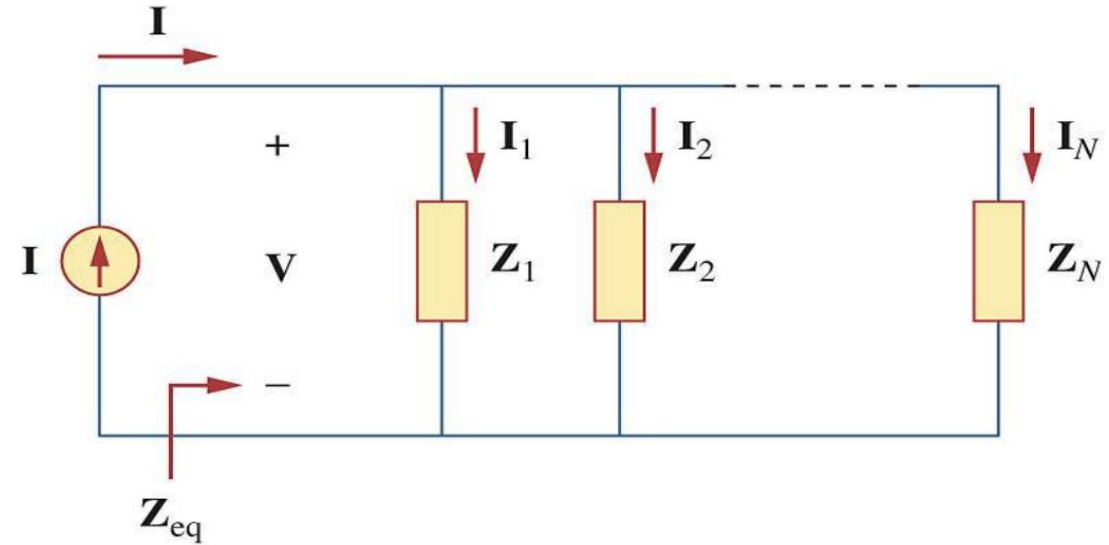


Figure 9.20 N impedances in parallel.

$$Z_{eq} = \frac{\tilde{V}}{\tilde{I}} = \frac{\overset{\text{KVL}}{\sum_{i=1}^N \tilde{V}_i}}{\tilde{I}} = \sum_{i=1}^N \frac{\tilde{V}_i}{\tilde{I}} = \sum_{i=1}^N Z_i$$

$$Y_{eq} = \frac{\tilde{I}}{\tilde{V}} = \frac{\overset{\text{KCL}}{\sum_{i=1}^N \tilde{I}_i}}{\tilde{V}} = \sum_{i=1}^N \frac{\tilde{I}_i}{\tilde{V}} = \sum_{i=1}^N Y_i$$

Exercise 1

Suppose we have following elements: $600\ \Omega$ resistors, $0.1\ \mu\text{F}$ capacitances, 10mH inductances. Please use the above elements to create an impedance of $300 - 400j\ \Omega$ at a frequency of $10,000\ \text{rad/s}$. The number of each elements is adequate.


$$R = 300 \Omega = \frac{600^2}{600+600} \Omega$$

$$\omega L - \frac{1}{\omega C} = 10000 L - \frac{1}{10^4 C} = -400$$

$$L = 10 \text{ mH}$$

$$\Rightarrow \frac{1}{10^4 C} = 100 + 400$$
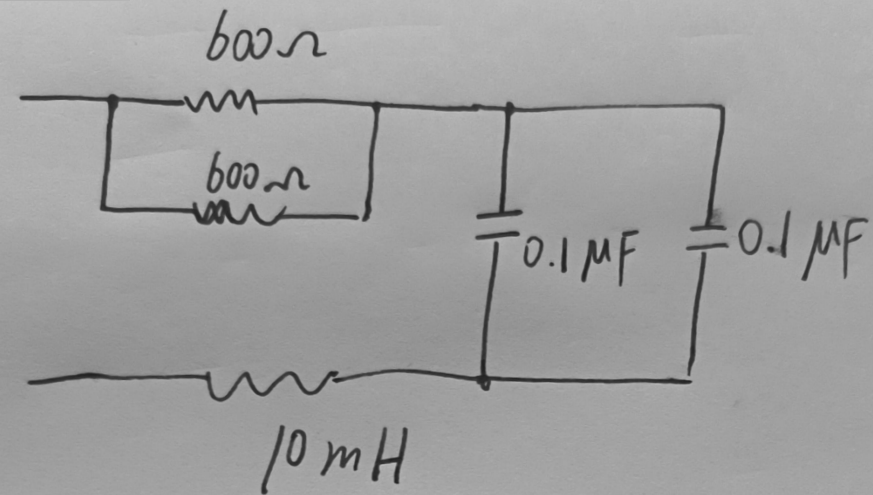
$$\Rightarrow C = 0.2 \mu\text{F}, \text{ two } 0.1 \mu\text{F} \text{ in parallel.}$$



Source Transformation and Equivalence Circuit:


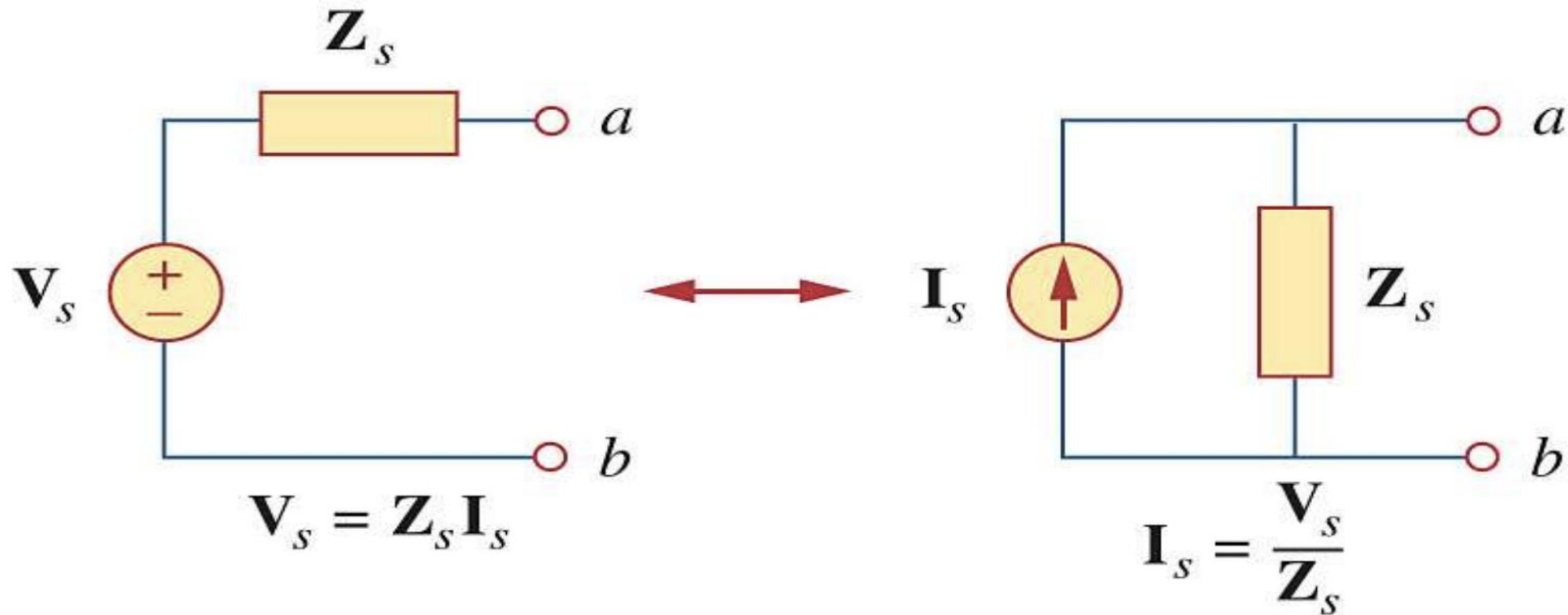


Figure 10.16 Source transformation.


Exercise 2

Find the Norton equivalent circuit with respect to the terminals a,b for the circuit shown in Fig. P9.50 when $\mathbf{V}_s = 5\angle 0^\circ \text{ V}$.

Figure P9.50

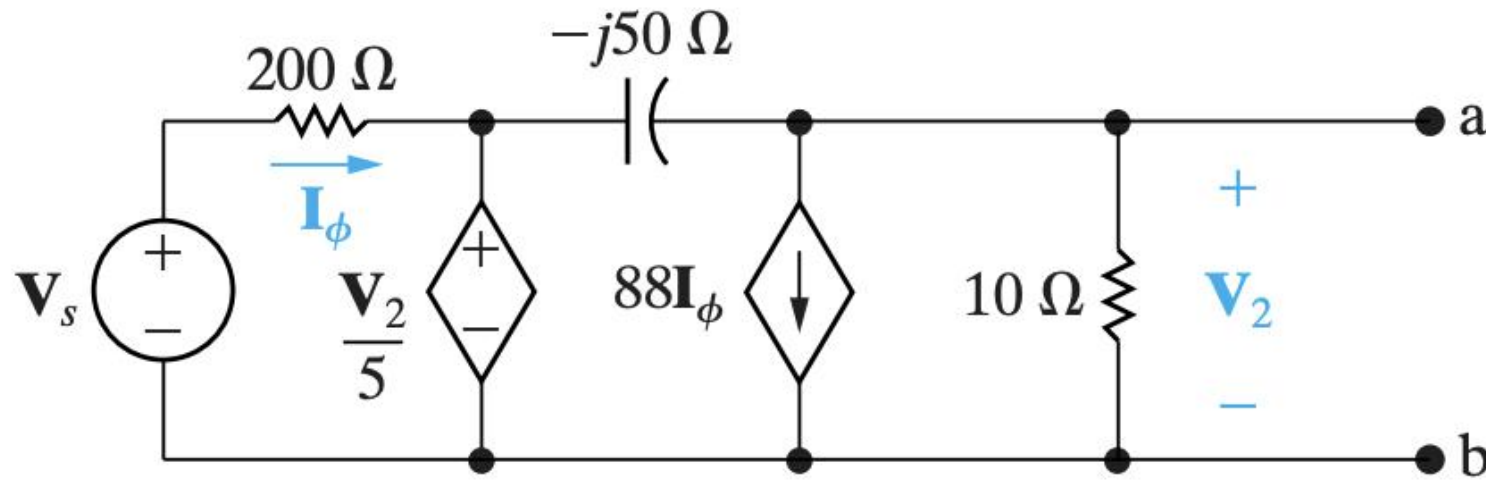

P 9.50 Open circuit voltage:

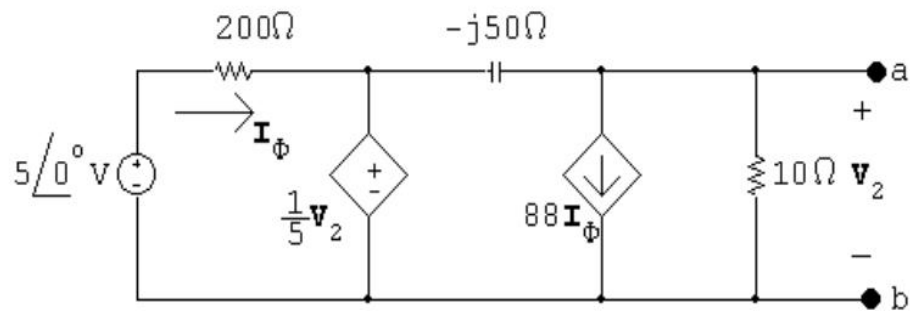


$$\frac{V_2}{10} + 88I_\phi + \frac{V_2 - \frac{1}{5}V_2}{-j50} = 0$$

$$I_\phi = \frac{5 - (V_2/5)}{200}$$

Solving,

$$V_2 = -66 + j88 = 110/\underline{126.87^\circ} \text{ V} = V_{\text{Th}}$$

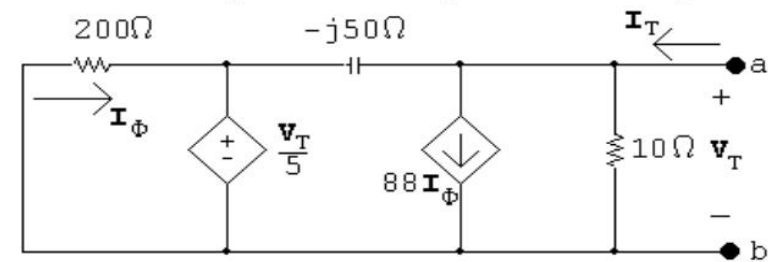Find the Thévenin equivalent impedance using a test source:



$$I_T = \frac{V_T}{10} + 88I_\phi + \frac{0.8V_T}{-j50}$$


$$I_\phi = \frac{-V_T/5}{200}$$

$$I_T = V_T \left(\frac{1}{10} - 88 \frac{V_T/5}{200} + \frac{0.8}{-j50} \right)$$

$$\therefore \frac{V_T}{I_T} = 30 - j40 = Z_{\text{Th}}$$

$$I_N = \frac{V_{\text{Th}}}{Z_{\text{Th}}} = \frac{-66 + j88}{30 - j40} = -2.2 + j0 \text{ A}$$

The Norton equivalent circuit:

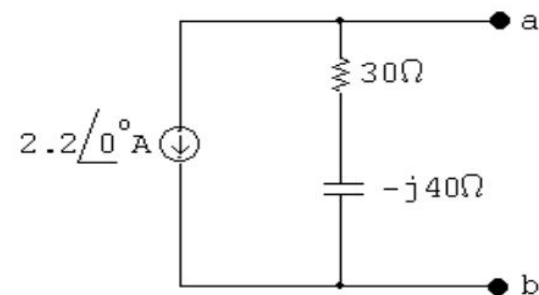

Superposition in AC Circuits:


1. For DC voltage/current sources: take capacitance as an open and inductance as a short circuit.
2. For AC voltage/current sources: transform capacitance and inductance into impedance in frequency domain.
3. In AC circuit, when analyzing one specific source:
 - (1) Handle the capacitance and inductance following 1.&2. above, based on what type of the source is being analyzed.
 - (2) Then, take other voltage sources as a short circuit while other current sources as an open circuit.

Exercise 3

10.48 Find i_o in the circuit of Fig. 10.93 using superposition.




ML

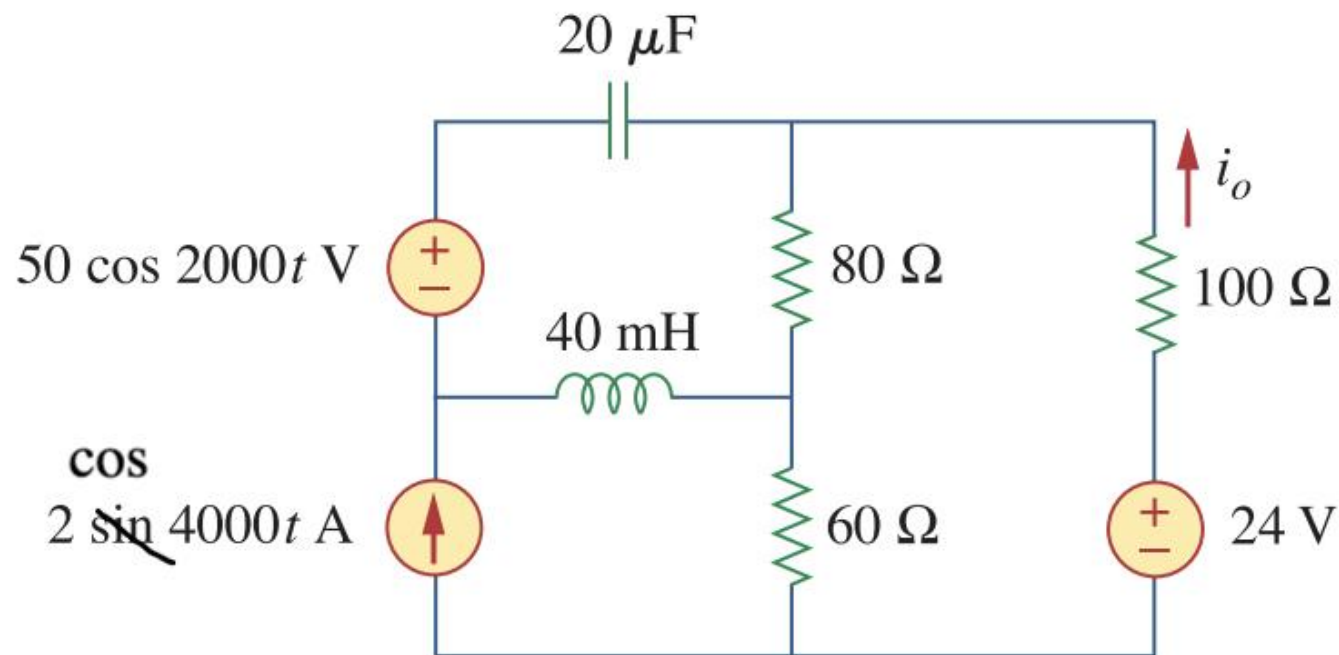

Chapter 10, Solution 48.

Let $i_o = i_{o1} + i_{o2} + i_{o3}$, where i_{o1} is due to the ac voltage source, i_{o2} is due to the dc voltage source, and i_{o3} is due to the ac current source. For i_{o1} , consider the circuit in Fig. (a).
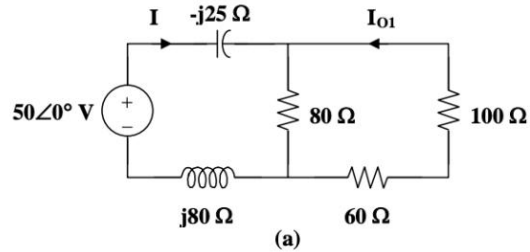
$$\begin{aligned}\omega &= 2000 \\ 50 \cos(2000t) &\longrightarrow 50 \angle 0^\circ \\ 40 \text{ mH} &\longrightarrow j\omega L = j(2000)(40 \times 10^{-3}) = j80 \\ 20 \text{ } \mu\text{F} &\longrightarrow \frac{1}{j\omega C} = \frac{1}{j(2000)(20 \times 10^{-6})} = -j25\end{aligned}$$




$$\begin{aligned}80 \parallel (60 + 100) &= 160/3 \\ \mathbf{I} &= \frac{50}{160/3 + j80 - j25} = \frac{30}{32 + j33}\end{aligned}$$

Using current division,

$$\begin{aligned}\mathbf{I}_{o1} &= \frac{-80\mathbf{I}}{80 + 160} = \frac{-1}{3}\mathbf{I} = \frac{10 \angle 180^\circ}{46 \angle 45.9^\circ} \\ \mathbf{I}_{o1} &= 0.217 \angle 134.1^\circ\end{aligned}$$

Hence, $i_{o1} = 0.217 \cos(2000t + 134.1^\circ) \text{ A}$

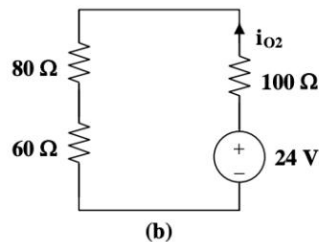
For i_{o2} , consider the circuit in Fig. (b).



$$i_{o2} = \frac{24}{80 + 60 + 100} = 0.1 \text{ A}$$

For i_{o3} , consider the circuit in Fig. (c).
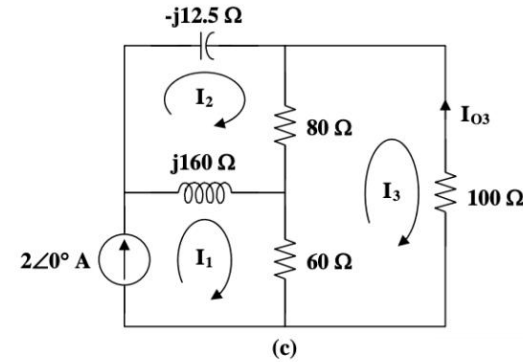
$$\begin{aligned}\omega &= 4000 \\ 2 \cos(4000t) &\longrightarrow 2 \angle 0^\circ \\ 40 \text{ mH} &\longrightarrow j\omega L = j(4000)(40 \times 10^{-3}) = j160 \\ 20 \text{ } \mu\text{F} &\longrightarrow \frac{1}{j\omega C} = \frac{1}{j(4000)(20 \times 10^{-6})} = -j12.5\end{aligned}$$



For mesh 1,

$$\mathbf{I}_1 = 2 \quad (1)$$

For mesh 2,

$$(80 + j160 - j12.5)\mathbf{I}_2 - j160\mathbf{I}_1 - 80\mathbf{I}_3 = 0$$

Simplifying and substituting (1) into this equation yields

$$(8 + j14.75)\mathbf{I}_2 - 8\mathbf{I}_3 = j32 \quad (2)$$

For mesh 3,

$$240\mathbf{I}_3 - 60\mathbf{I}_1 - 80\mathbf{I}_2 = 0$$

Simplifying and substituting (1) into this equation yields

$$\mathbf{I}_2 = 3\mathbf{I}_3 - 1.5 \quad (3)$$

Substituting (3) into (2) yields

$$\begin{aligned}(16 + j44.25)\mathbf{I}_3 &= 12 + j54.125 \\ \mathbf{I}_3 &= \frac{12 + j54.125}{16 + j44.25} = 1.1782 \angle 7.38^\circ\end{aligned}$$

$$\mathbf{I}_{o3} = -\mathbf{I}_3 = -1.1782 \angle 7.38^\circ$$

Hence, $i_{o3} = -1.1782 \sin(4000t + 7.38^\circ) \text{ A}$

Therefore,


$$i_o = \{0.1 + 0.217 \cos(2000t + 134.1^\circ) - 1.1782 \sin(4000t + 7.38^\circ)\} \text{ A}$$

Three-phase Circuits

A three-phase system is produced by a generator consisting of three sources having **the same amplitude and frequency** but **out of phase with each other by 120 degrees**. **Voltage sources meeting this condition is called balanced sources.**

$$\text{i.e., } \tilde{V}_{an} + \tilde{V}_{bn} + \tilde{V}_{cn} = 0$$


Physical illustration of three-phase

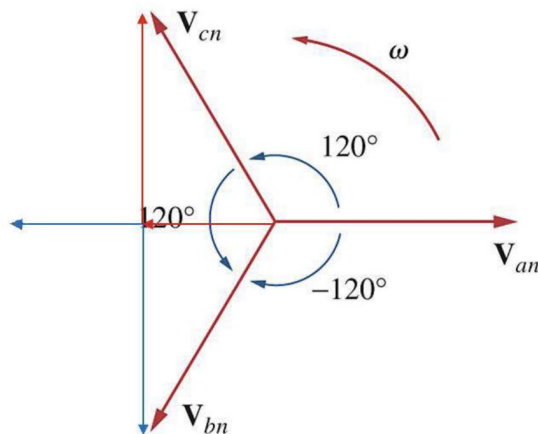


▼ Balanced Three-Phase Voltage Sources

▼ Different Types

▪ Y-Type

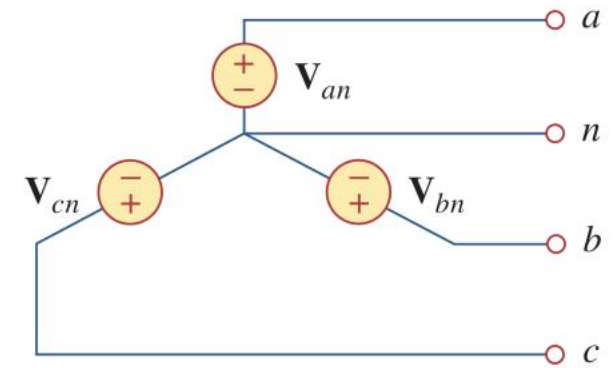

▪ Δ -Type

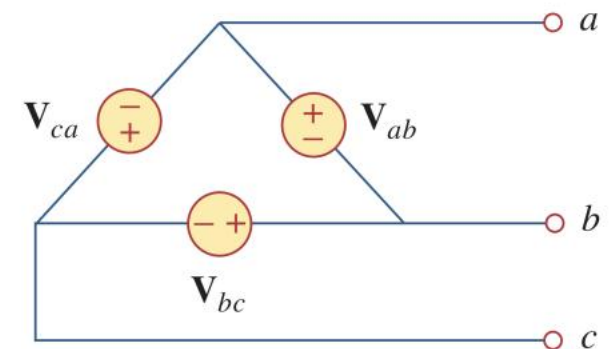

A load is said to be balanced if the phase impedances **are equal in magnitude and phase**


For a balanced wye-connected load,

$$Z_1 = Z_2 = Z_3 = Z_Y$$

For a balanced delta-connected load,

$Z_A = Z_B = Z_C = Z_\Delta$
If loads are balanced, the relationship below holds:
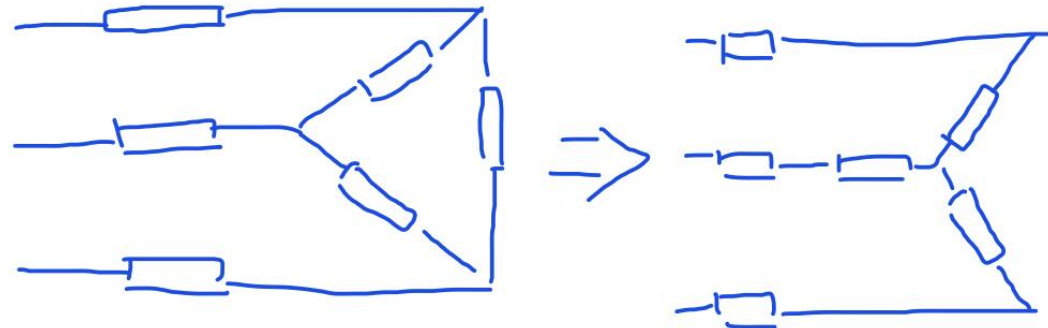
$$Z_\Delta = 3Z_Y \text{ or } Z_Y = \frac{1}{3} Z_\Delta$$



Some concepts to be emphasized:

Line:

Conductors connecting loads and sources

Line voltage:

voltage measured between two different lines

Line currents:

The current passing along each line

Phase:

Connected between any pair of line terminals (an element)

Phase voltage:

The voltage measured across any phase. In delta-delta system, $V_P = V_L$.

Phase currents:

The current passing through the phase. In Y-Y system, $I_P = I_L$.

Also, abc/acb, positive/negative sequence, check them in your slides!

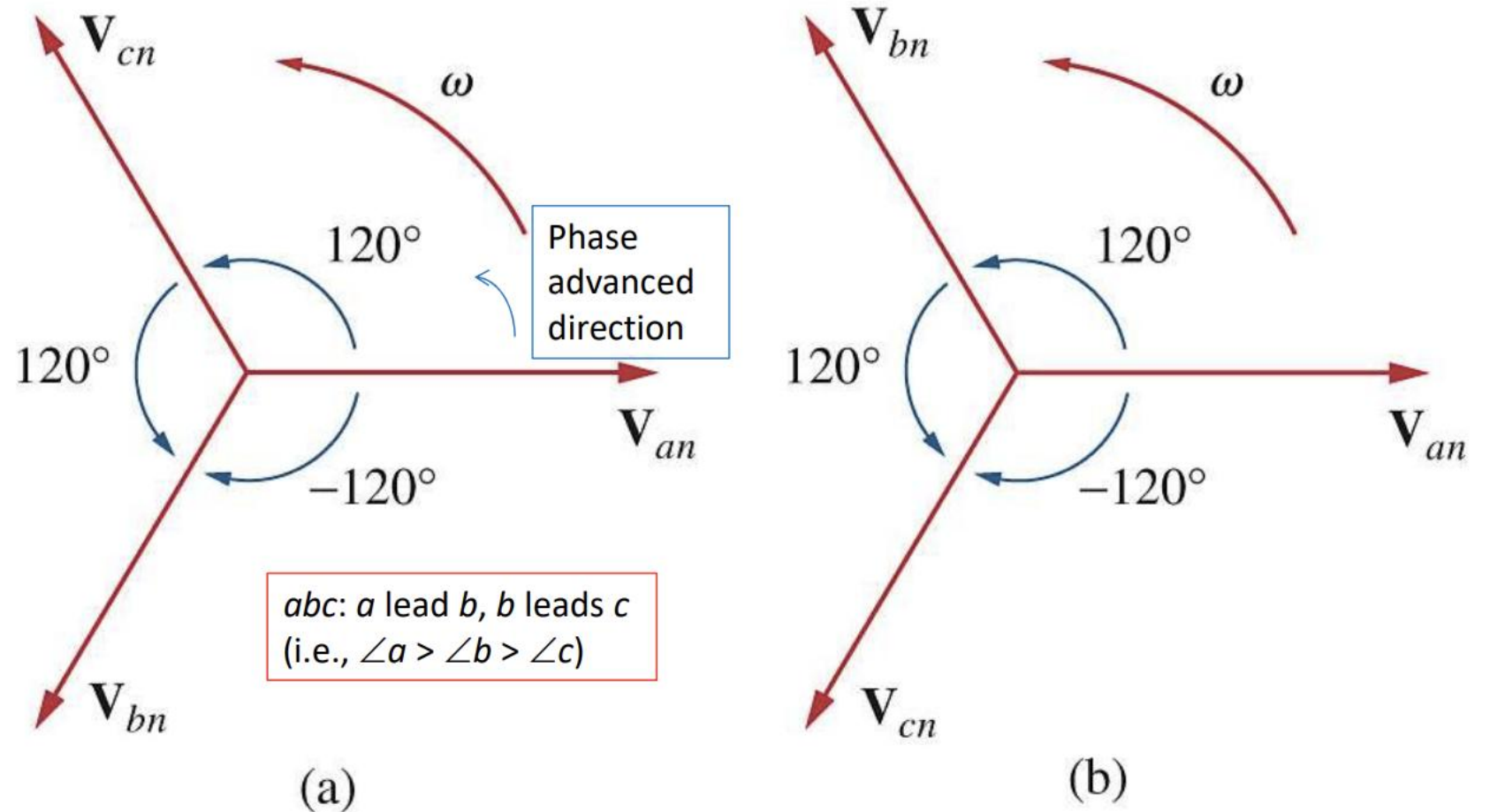


Figure 12.7 Phase sequences: (a) *abc* or positive sequence, (b) *acb* or negative sequence.

Take-aways: V_p is the effective or rms value of phase voltage

Y-Y

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle +120^\circ$$

Same as line currents

$$V_{ab} = \sqrt{3}V_p \angle 30^\circ$$


$$V_{bc} = V_{ab} \angle -120^\circ$$

$$V_{ca} = V_{ab} \angle +120^\circ$$

$$I_a = V_{an} / Z_Y$$

$$I_b = I_a \angle -120^\circ$$

$$I_c = I_a \angle +120^\circ$$

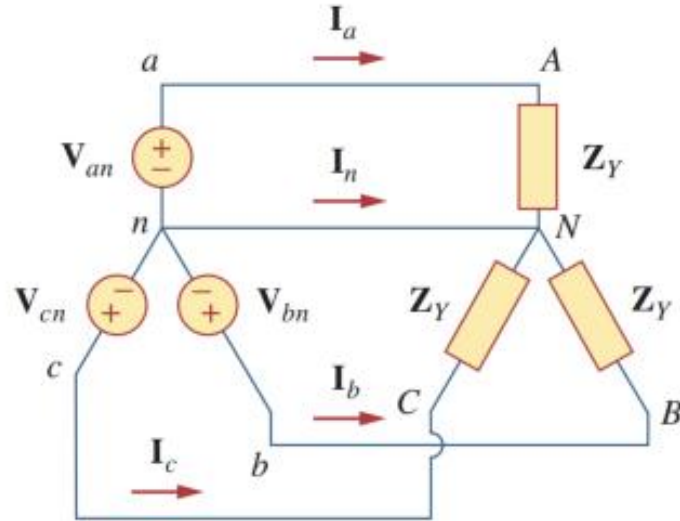

Y-Δ

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle +120^\circ$$

$$I_{AB} = V_{AB} / Z_\Delta$$

$$I_{BC} = V_{BC} / Z_\Delta$$

$$I_{CA} = V_{CA} / Z_\Delta$$

$$V_{ab} = V_{AB} = \sqrt{3}V_p \angle 30^\circ$$


$$V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$$

$$V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$$

$$I_a = I_{AB} \sqrt{3} \angle -30^\circ$$

$$I_b = I_a \angle -120^\circ$$

$$I_c = I_a \angle +120^\circ$$

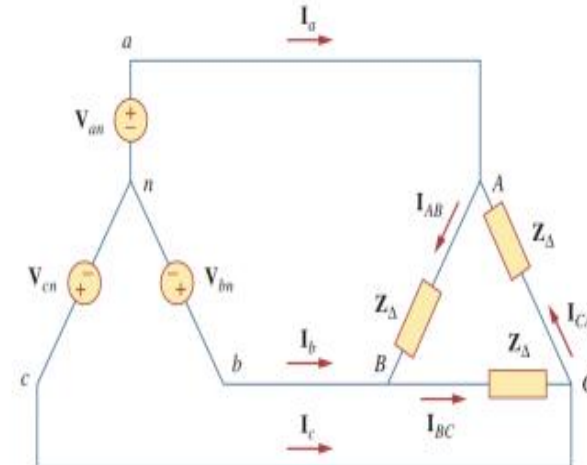

Take-aways: V_p is the effective or rms value of phase voltage


Δ -Y

$$\begin{aligned} \mathbf{V}_{ab} &= V_p \angle 0^\circ \\ \mathbf{V}_{bc} &= V_p \angle -120^\circ \\ \mathbf{V}_{ca} &= V_p \angle +120^\circ \end{aligned}$$

Same as line currents

Same as phase voltages
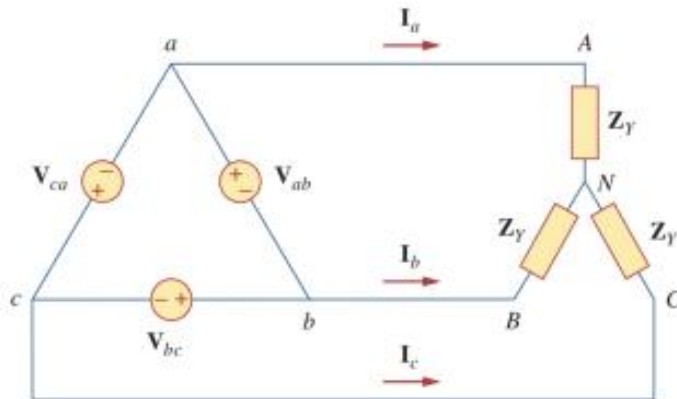
$$\begin{aligned} \mathbf{I}_a &= \frac{V_p \angle -30^\circ}{\sqrt{3} \mathbf{Z}_Y} \\ \mathbf{I}_b &= \mathbf{I}_a \angle -120^\circ \\ \mathbf{I}_c &= \mathbf{I}_a \angle +120^\circ \end{aligned}$$




Δ - Δ

$$\begin{aligned} \mathbf{V}_{ab} &= V_p \angle 0^\circ \\ \mathbf{V}_{bc} &= V_p \angle -120^\circ \\ \mathbf{V}_{ca} &= V_p \angle +120^\circ \end{aligned}$$

Same as phase voltages

$$\begin{aligned} \mathbf{I}_{AB} &= \mathbf{V}_{ab} / \mathbf{Z}_\Delta \\ \mathbf{I}_{BC} &= \mathbf{V}_{bc} / \mathbf{Z}_\Delta \\ \mathbf{I}_{CA} &= \mathbf{V}_{ca} / \mathbf{Z}_\Delta \end{aligned}$$
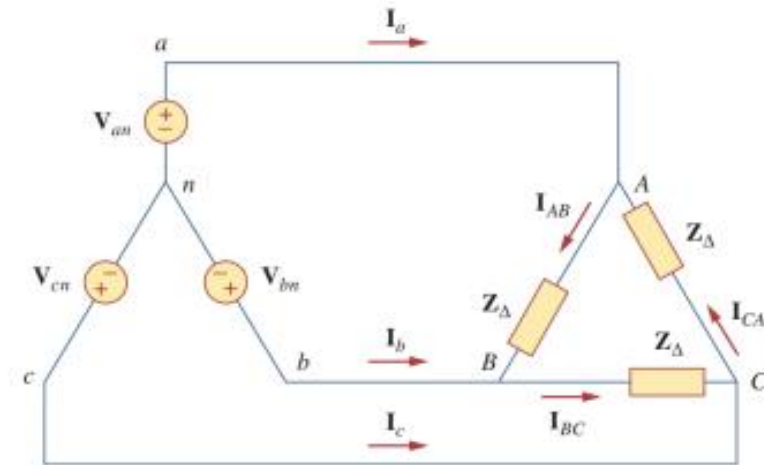
$$\begin{aligned} \mathbf{I}_a &= \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ \\ \mathbf{I}_b &= \mathbf{I}_a \angle -120^\circ \\ \mathbf{I}_c &= \mathbf{I}_a \angle +120^\circ \end{aligned}$$



Take-aways:

Power analysis in Three-phase circuits

- Total instantaneous/average power
- $P = 3V_{Prms}I_{Prms} \cos(\angle Z)$
- Total reactive power
- $Q = 3V_{Prms}I_{Prms} \sin(\angle Z)$
- Total complex power
- $S = 3\widetilde{V_{Prms}}\widetilde{I_{Prms}}^*$
- In particular, for Y-Y and Δ - Δ structures:
- $P = 3V_{Prms}I_{Prms} \cos(\angle Z) = \sqrt{3}V_{Lrms}I_{Lrms} \cos(\angle Z)$

Exercise 4

(Prof.Chen's slides, chapter 12, example 12.8)

Two balanced loads are connected to a 240-kV rms 60-Hz line, as shown in Fig. 12.22(a).


Load 1 draws 30 kW at a power factor of 0.6 lagging, while load 2 draws 45 kVAR at a power factor of 0.8 lagging.

Assuming the **abc** sequence, determine:

(a) the complex, real, and reactive powers absorbed by the combined load,

(b) the line current

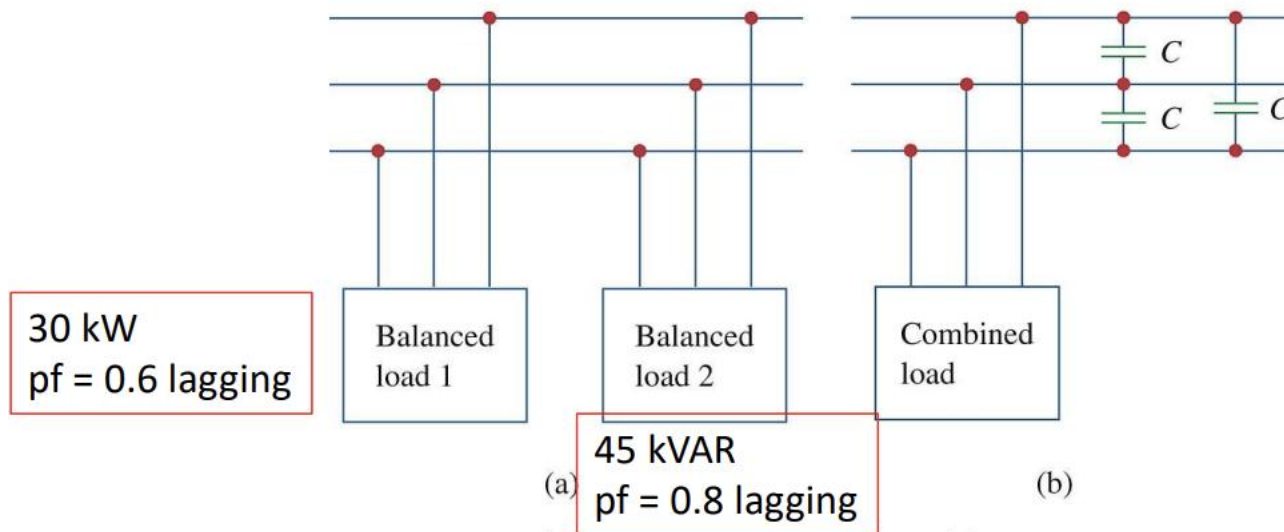(c) the kVAR rating of the three capacitors -connected in parallel with the load that will raise the power factor to 0.9 lagging and the capacitance of each capacitor.



(a) $V_L = 240 \text{ kV}$

$$\cos \theta_1 = 0.6 \Rightarrow \tan \theta_1 = \frac{4}{3}$$

$$S_1 = P_1 + jQ_1$$

$$= P_1 + jP_1 \tan \theta_1$$

$$= 30 + j40 \text{ (kVA)}$$

Similarly, $S_2 = P_2 + jQ_2 = 60 + j45 \text{ (kVA)}$

$$S = S_1 + S_2 = 90 + j85 \text{ (kVA)}$$

$$S = 90 + j85 \text{ (kVA)}$$

$$P = 90 \text{ (kW)}$$

$$Q = 85 \text{ (kVAR)}$$

pay attention to the units!

(b) phase as whole: $\theta = \tan^{-1} \left(\frac{85}{90} \right) = 43.36^\circ$ ** clarify degrees & radians*

$$I_L = \frac{P}{\sqrt{3} V_L \cos \theta} = \frac{90 \times 10^3}{\sqrt{3} \times 240 \times 10^3 \times \cos 43.36^\circ} = 0.298 \text{ (A)}$$

(c) new phase: $\theta_2 = \cos^{-1} 0.9 = 25.84^\circ$

ΔQ contributed by capacitors:

$$\Delta Q = P(\tan \theta_1 - \tan \theta_2) = 90 \times (\tan 43.36^\circ - \tan 25.84^\circ) = 41.40 \text{ (kVAR)}$$

for a single Capacitor: $\Delta Q' = \Delta Q / 3 = 13.80 \text{ (kVAR)}$

Recall $|Q_C| = |I^2 X| = |V^2 / X^*| = \omega C V^2$, if purely capacitive.

$$\Rightarrow C = \frac{|Q_C|}{\omega V^2} = \frac{13.8 \times 10^3}{2\pi \times 60 \times (240 \times 10^3)^2} = 635.51 \text{ pF}$$

pay attention to the difference between f and ω

Tips for exams:

1. Get familiar with basic concepts
2. Get familiar with your calculator

Reference

- [1] 2024 Fall VE215 slides, Songliang Chen
- [2] 2024 Fall RC6, Yuting Cao
- [3] 2023 Fall Final RC
- [4] Fundamentals of Electric Circuits, 5th e, Sadiku, Matthew

THANK YOU