

ECE2150J Homework 4

Deadline: 7th December 2024

Problem 1

- (a) (10%) Obtain the equivalent admittance Y_{in} of the circuit at $\omega = 100 \text{ rad/s}$.
- (b) (10%) Obtain the equivalent impedance Z_{in} of the circuit.
- (c) (10%) Obtain the equivalent impedance Z_{ab} of the circuit.

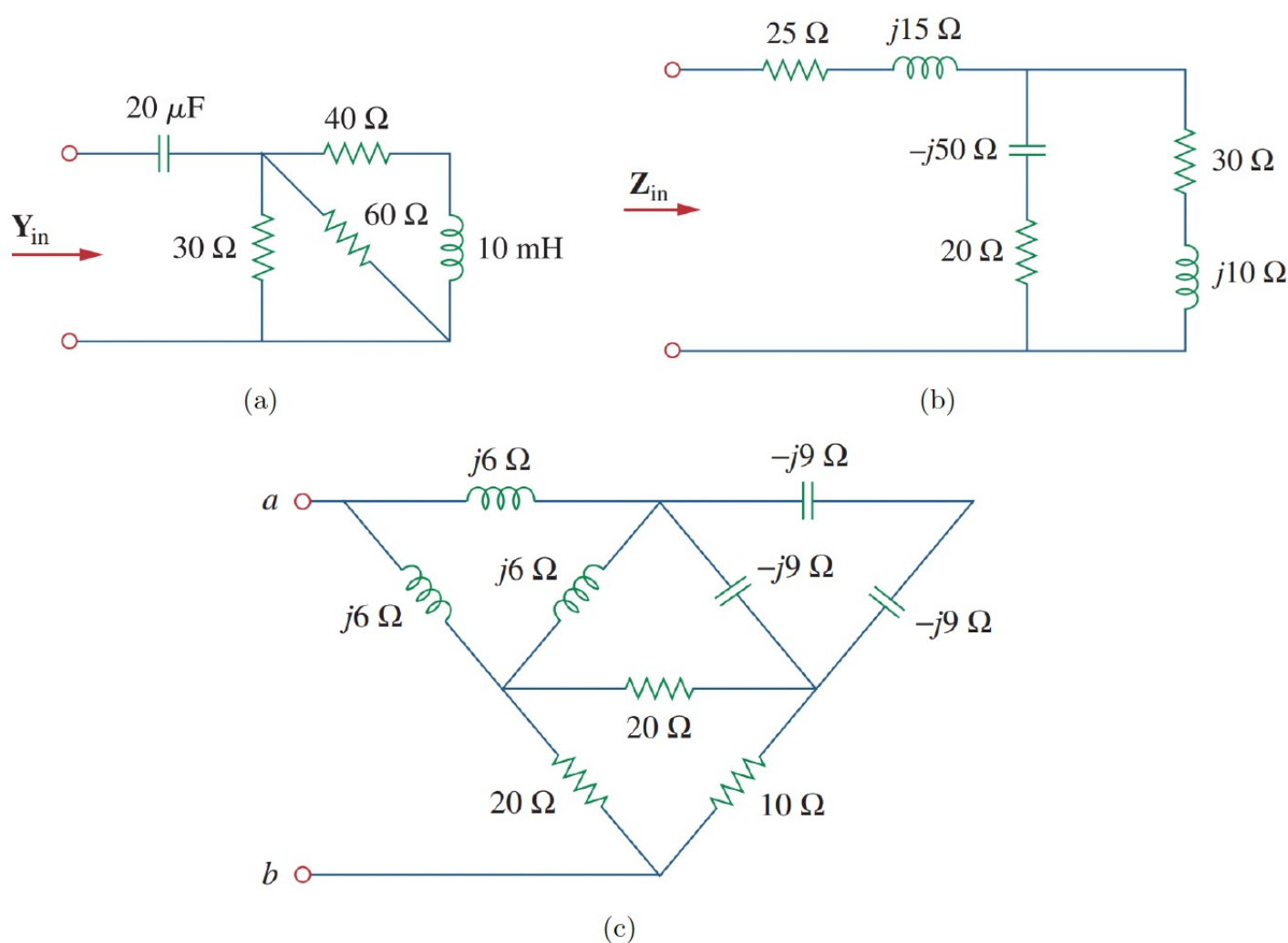


Figure 1: Circuit for Problem 1

Problem 2

- (a) (30%) Please find the Thevenin equivalent circuits between terminal a and b under $\omega = 2000 \text{ rad/s}$ and $\omega = 4000 \text{ rad/s}$.
- **Hint:** Consider whether to turn on or turn off the voltage source and current source based on the frequency you choose.
- (b) (10%) Please draw two phasor diagrams of the two Thevenin equivalent impedances under the two frequencies ($\omega = 2000 \text{ rad/s}$ and $\omega = 4000 \text{ rad/s}$).

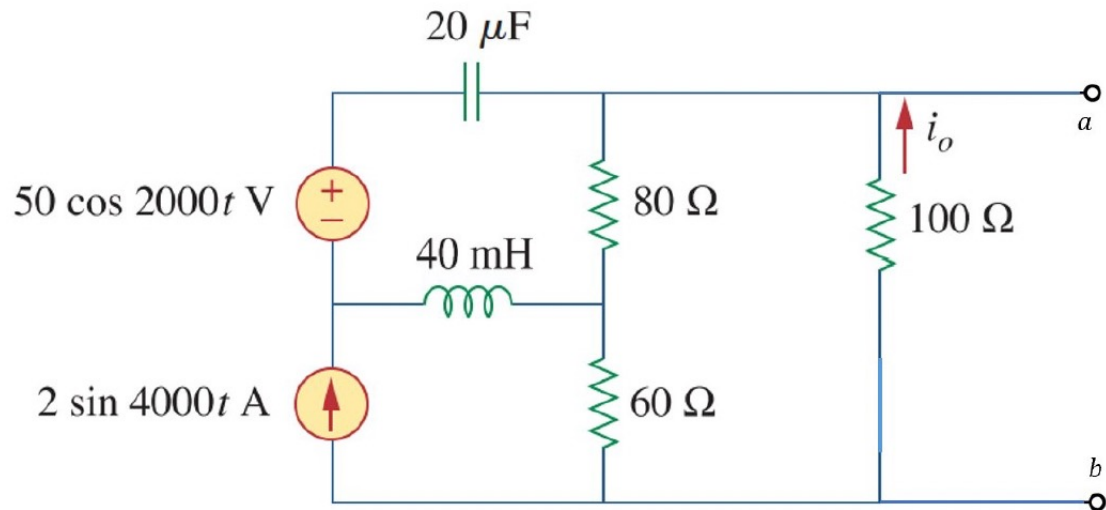


Figure 2: Circuit for Problem 2

Problem 3

Given the circuit below, calculate the equivalent impedance in each of the blocks. Also find I_o and the overall complex power supplied.

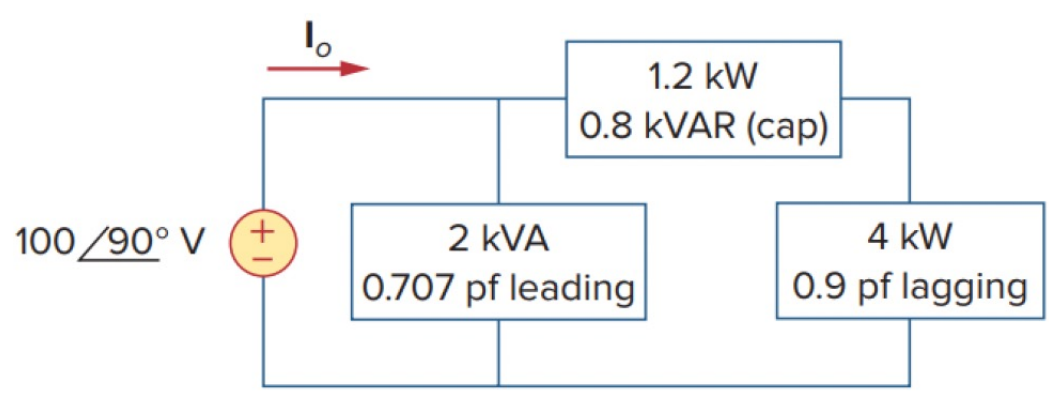


Figure 3: Circuit for Problem 3

