

上 海 交 通 大 学 试 卷

(2021~2021~1 Academic Year/Fall Semester)

Class No. _____ Name in English or Pinyin: _____

Student ID No. _____ Name in Hanzi (if applicable): _____

VE215 Introduction to Circuits**Final Exam****8:00 – 9:40 am 13th December**The exam paper has **16 pages** in total.

You are to abide by the University of Michigan-Shanghai Jiao Tong University Joint Institute (UM-SJTU JI) honor code. Please sign below to signify that you have kept the honor code pledge.

THE UM-SJTU JI HONOR CODE**I accept the letter and spirit of the honor code:**

I have neither given nor received unauthorized aid on this examination, nor have I concealed any violations of the Honor Code by myself or others.

Signature:_____

Please enter grades here:

Exercises No.		Points	Grader's Signature
题号		得分	流水批阅人签名
1	1-1		
	1-2		
	1-3		
	1-4		
	1-5		
	1-6		
2			
3			
4			
5			
Total 总分			

Instructions:

- **Chapter 9-14** are covered in this exam.
- Closed book, scientific calculator and one page of summary in A4 size, double sided is allowed.
- There are **16 pages** in total.
- There are **5 questions** in total.
- Please write your **partial steps** and that will be counted.
- Please manage your time properly. If you encounter some questions and feel hard, please move on and go back after finishing all the rest.
- **No tolerance to cheating!** Any intentional violations of the SJTU exam rule of a vile nature will be assigned an “F” as course grade.


Fingers crossed!

Exam questions A type:

Q1. Please answer Questions 1-1 to 1-6. [Total 34 points]

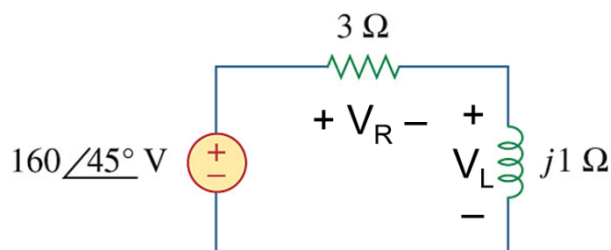1-1. Input voltage (V_i) is $160\angle 45^\circ$. Please choose **one right** answer. [5 points]



Your answer: (a)(d)(e). Due to an error both (a) and (d) are right answers. And, we gave full marks for those who chose (e) by thinking that there is no one right answer.



- (a) V_i leads V_R .
- (b) V_i lags V_R .
- (c) V_i leads V_L .
- (d) V_i lags V_L .
- (e) None of the above.

1-2. Below show polarities of turns ratio n with respect to voltage and current in an ideal transformer. Choose **one wrong** description. [5 points]



Your answer: (d)

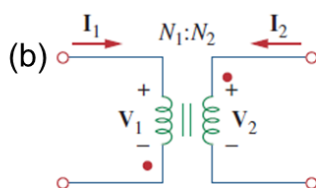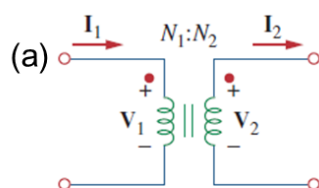

(a) $\frac{V_2}{V_1} = \frac{N_2}{N_1}, \frac{I_2}{I_1} = \frac{N_1}{N_2}$

(b) $\frac{V_2}{V_1} = -\frac{N_2}{N_1}, \frac{I_2}{I_1} = \frac{N_1}{N_2}$

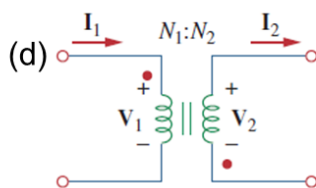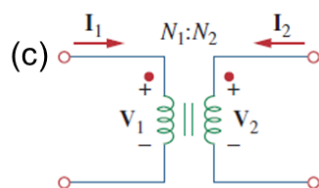(c) $\frac{V_2}{V_1} = \frac{N_2}{N_1}, \frac{I_2}{I_1} = -\frac{N_1}{N_2}$




(d) $\frac{V_2}{V_1} = -\frac{N_2}{N_1}, \frac{I_2}{I_1} = \frac{N_1}{N_2}$

(e) None of the above

1-3. Choose **one wrong** description about the circuit below. All values are in **rms**. Please allow $\pm 10\%$ calculation differences. [6 points]


Your answer: (c)

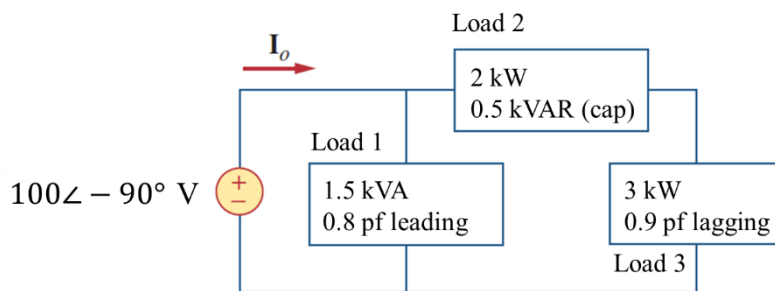

- (a) Magnitude of I_o is 65.04.
- (b) Angle of I_o is -88.02° .
- (c) Current at the Load 1 is $18.75\angle 53.13^\circ$.
- (d) Current at the Load 2 is $50.9\angle -100.79^\circ$.
- (e) None of the above.

1-4. Please choose **one wrong** description about the circuit below. Please allow $\pm 10\%$ calculation differences. [6 points]

Your answer: (d)

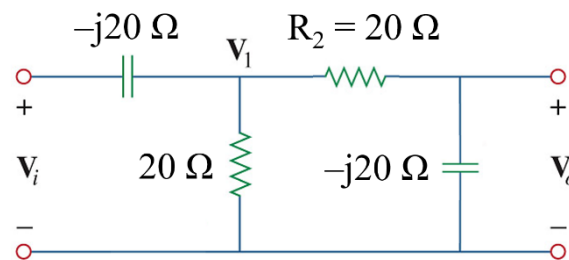

- (a) Phase of voltage V_1 leads V_i .
- (b) Phase of output voltage V_o lags V_1 .
- (c) The total phase shift in this circuit is 0 degree.
- (d) If we change the value of R_2 from 20 to 10 Ω , V_o leads V_i approximately by $+18.4^\circ$.
- (e) None of the above.


1-5. When connected to a 240 V_{rms} , 60 Hz power line, a load has apparent power of 6 kVA and a lagging pf of 0.750. Find the value of capacitance necessary to raise the pf to 0.980. [6 points].

Your answer: 1.41×10^{-4} [F]

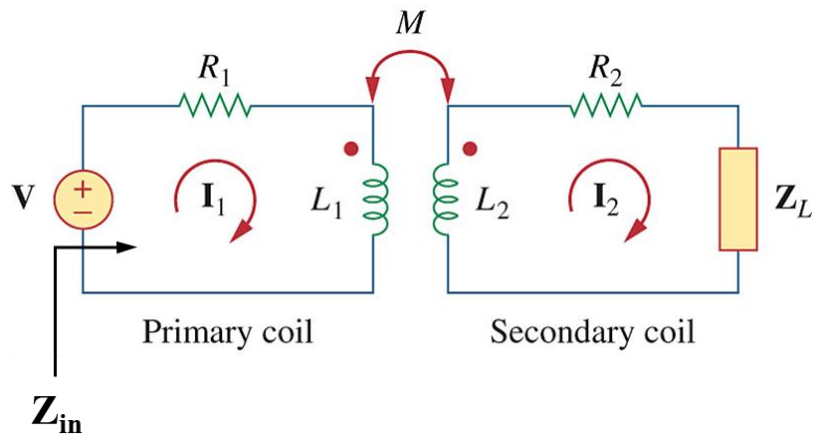1-6. Find the input impedance Z_{in} in the linear transformer circuit below. [6 points]



Your answer:

$$R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$




***Q2-Q4. Please write phasor forms for all answers.**

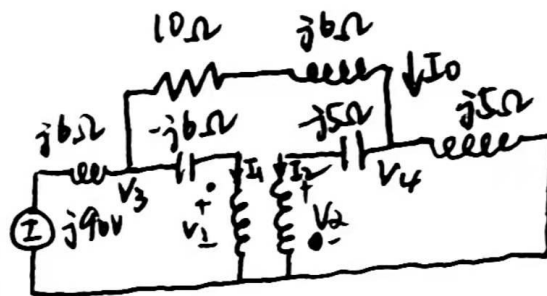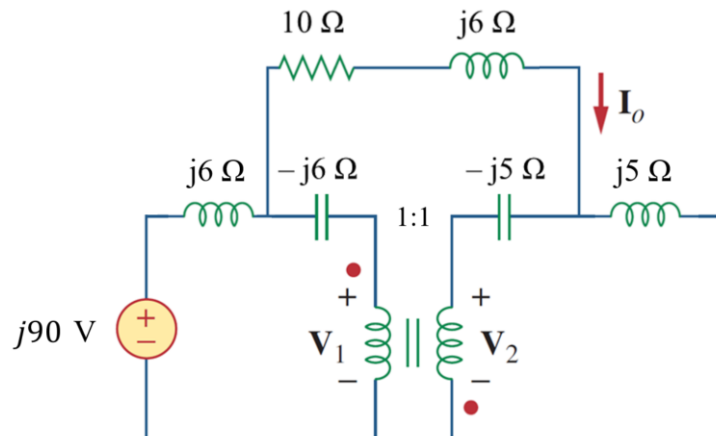Q2. Find I_o of the circuit below. The transformer is ideal. [Total 12 points]



$$\begin{aligned}
 & \begin{cases} V_1 = -V_2 & 2' \\ \frac{V_3 - j90}{j6} + \frac{V_3 - V_4}{10 + j6} + \frac{V_3 - V_1}{-j6} = 0 & 2' \\ \frac{V_4 - V_2}{-j5} + \frac{V_4 - V_3}{10 + j6} + \frac{V_4}{j5} = 0 & 2' \end{cases} \\
 & \frac{V_1 - V_3}{-j6} + I_1 = 0 & 1' \\
 & \frac{V_2 - V_4}{-j5} + I_2 = 0 & 1' \\
 & V_3 - V_4 = 90 + j540 & 2' \\
 & I_o = \frac{V_3 - V_4}{10 + j6} = 90 = 90 \angle 0^\circ & 2'
 \end{aligned}$$

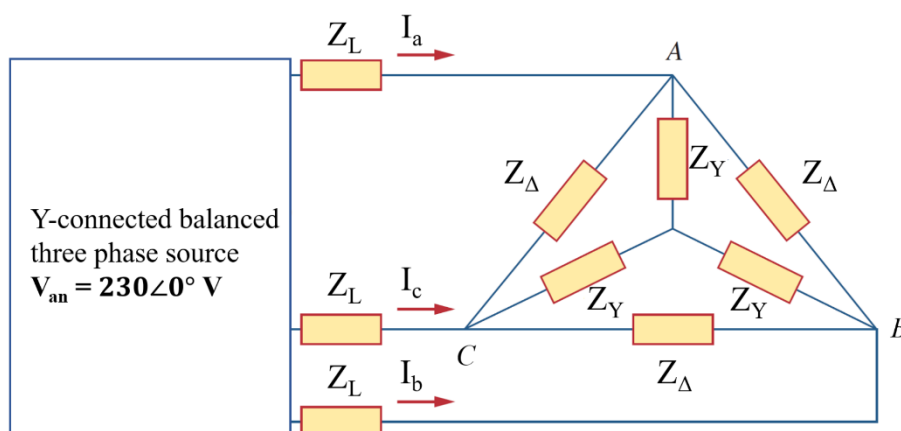Q3. Please find (1) Line current $\mathbf{I_a}$, $\mathbf{I_c}$, and $\mathbf{I_b}$ [10 points] and (2) **total complex power** at the loads, (combined $\mathbf{Z_\Delta + Z_Y}$). [6 points] Take $\mathbf{Z_L = 1 + j0.6 \, \Omega}$, $\mathbf{Z_\Delta = 6 - j9 \, \Omega}$, $\mathbf{Z_Y = 3 + j4 \, \Omega}$. All values are in **rms**. Assume **acb sequence**. [Total 16 points]



Summary of phase and line V and I for balanced three-phase systems (**abc** sequence).


Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ <p>Same as line currents</p>	$\mathbf{V}_{ab} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{V}_{an} / \mathbf{Z}_Y$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Y-Δ	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{AB} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{BC} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{CA} / \mathbf{Z}_\Delta$	$\mathbf{V}_{ab} = \mathbf{V}_{AB} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{BC} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{CA} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Δ-Δ	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{ab} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{bc} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{ca} / \mathbf{Z}_\Delta$	<p>Same as phase voltages</p> $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Δ-Y	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ <p>Same as line currents</p>	<p>Same as phase voltages</p> $\mathbf{I}_a = \frac{V_p \angle -30^\circ}{\sqrt{3} \mathbf{Z}_Y}$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$

1) Δ Load and Y load are in parallel.

Apply Δ - Y transform on Δ load: $Z_{Ye} = \frac{Z_{\Delta}}{3} = 2 - 3j$ ^{2'}

$$Z_t = Z_{Ye} \parallel Z_Y = (2 - 3j) \parallel (3 + 4j) = \frac{89}{26} - \frac{23}{26}j \quad (3.423 - 0.885j) / 3.5355 \angle -14.49^\circ / \frac{\sqrt{2}}{2} \angle -14.49^\circ$$

we get

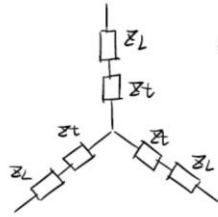

since acb sequence: $V_{an} = 230 \angle 0^\circ$, $V_{bn} = 230 \angle 120^\circ$, $V_{cn} = 230 \angle -120^\circ$


$$I_a = \frac{V_{an}}{Z_L + Z_t} = 51.7856 + 3.3323j \quad (51.8927 \angle 3.6818^\circ) \quad 2'$$

$$I_b = -28.7786 + 43.1815j \quad (51.8927 \angle 123.6818^\circ) \quad 2'$$

$$I_c = -23.0069 - 46.5132j \quad (51.8927 \angle -116.3182^\circ) \quad 2'$$

$$2) \quad S = 3 |I_p|^2 Z_t = 27653.49675 - 7146.40927j \quad (28361.9861 \angle -14.4898^\circ) \quad 6'$$

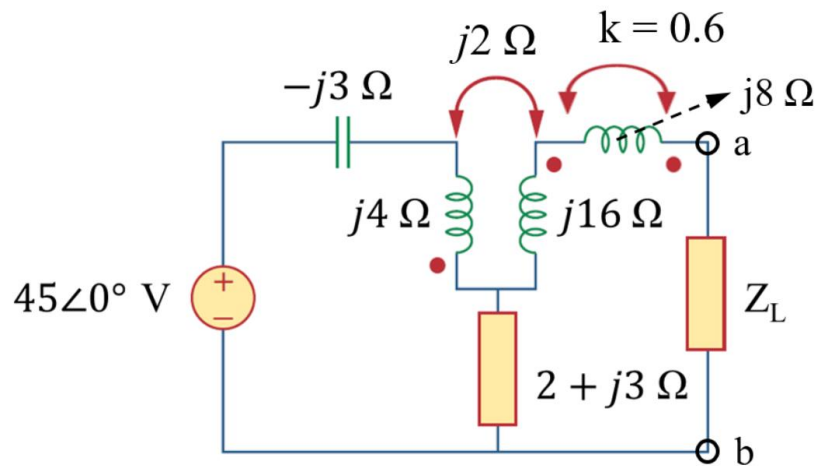
Q4. Below is the circuit with the magnetically coupled inductors. (1) Find the **Thevenin Equivalent** circuit between terminals a and b [10 points], and (2) $\mathbf{Z_L}$ to transfer maximum average power. [2 points] (3) If $\mathbf{Z_L} = 6 + j4$, what is the **complex power** at the load $\mathbf{Z_L}$? Please draw the **power triangle** and define **pf** at the $\mathbf{Z_L}$. [8 points] Please note that the values are **NOT in rms**. [Total 20 points]



Q4:

$$i) \ jWM = j \cdot \sqrt{WL_1 WL_2} = j \cdot 0.6 \sqrt{8 \times 16} = j \ 6.79 \quad |'$$

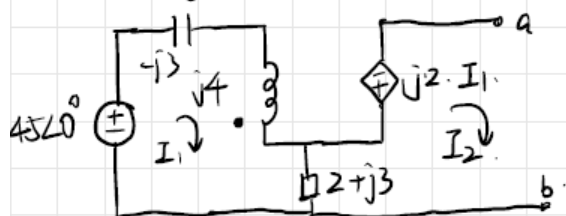To find V_{Th} , make terminal a-b open circuit.




$$I_1 \cdot (-j3 + j4 + 2 + j3) = 45 \angle 0^\circ \quad |'$$

$$I_1 (2 + j4) = 45 \angle 0^\circ \Rightarrow I_1 = 10 \angle -63^\circ \quad |'$$

$$\Rightarrow V_{Th} = (2 + j3) I_1 - j2 I_1 = (2 + j) I_1 = 22.5 \angle -36.9^\circ \quad |'$$

Then find R_{Th} .

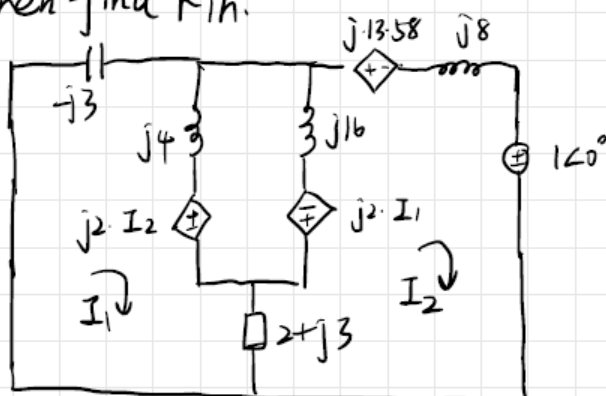

From mesh analysis:

$$\begin{cases} (-j3 + j4) \cdot I_1 + j2 \cdot I_2 + (I_1 - I_2)(2 + j3) = 0 & \textcircled{1} \\ (2 + j3)(I_2 - I_1) + j2 I_1 + j16 \cdot I_2 + j13.58 I_2 + I_2 j8 + 1 = 0 & \textcircled{2} \end{cases} \quad |'$$

$$\text{From ① } I_1 = \frac{2+j}{2+j4} I_2. \quad 1'$$

$$\text{From ② } (2+j40.58) I_2 - (2+j) I_1 + 1 = 0. \quad 1'$$

$$\Rightarrow Z_{th} = -\frac{1}{I_2} = 40.78 \angle 88.7^\circ \quad 2'$$


$$2) \quad Z_L = \underline{Z_{th}^*} = 40.78 \angle -88.7^\circ \quad 1'$$

$$3) \quad S = \frac{1}{2} I^2 Z = \frac{1}{2} \left| \frac{22.5}{6+j4 + 40.78 \angle 88.7^\circ} \right|^2 (6+j4).$$

$$= 0.5 \cdot \frac{22.5^2}{45.3^2} (6+j4) = 0.88 \angle 33.7^\circ \quad 3'$$


$$pf = 0.83 \quad 4'$$

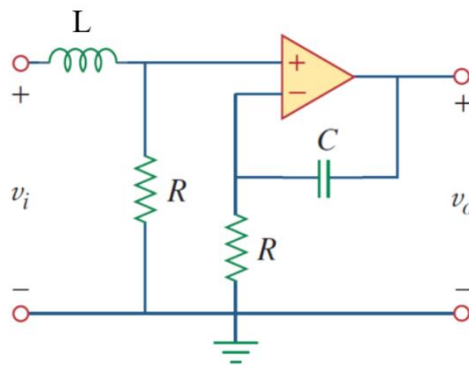Q5. Please draw a **Bode plot** of the transfer function $H(\omega) = V_o/V_i$ [Total 18 points]



Factor	Magnitude	Phase
K	$20 \log_{10} K$ 	
$(j\omega)^N$	$20N \text{ dB/decade}$ 	$90N^\circ$
$\frac{1}{(j\omega)^N}$	$-20N \text{ dB/decade}$ 	$-90N^\circ$
$\left(1 + \frac{j\omega}{z}\right)^N$	$20N \text{ dB/decade}$ 	0° to $90N^\circ$
$\frac{1}{(1 + j\omega/p)^N}$	$-20N \text{ dB/decade}$ 	0° to $-90N^\circ$
$\left[1 + \frac{2j\omega\zeta}{\omega_n} + \left(\frac{j\omega}{\omega_n}\right)^2\right]^N$	$40N \text{ dB/decade}$ 	0° to $180N^\circ$
$\frac{1}{[1 + 2j\omega\zeta/\omega_k + (j\omega/\omega_k)^2]^N}$	$-40N \text{ dB/decade}$ 	0° to $-180N^\circ$

Question 5

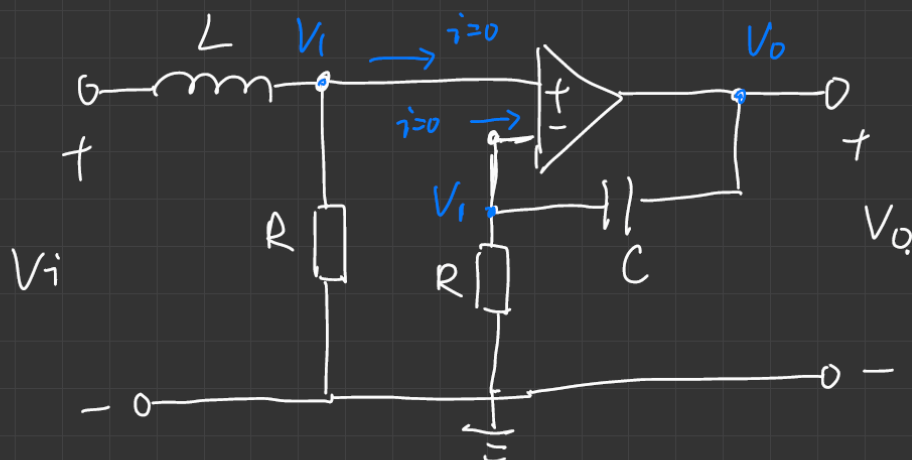


$$\begin{cases} \frac{V_1 - V_i}{j\omega L} + \frac{V_1}{R} = 0 \\ \frac{V_1}{R} + \frac{V_1 - V_o}{\frac{1}{j\omega C}} = 0 \end{cases} \Rightarrow \begin{aligned} V_i &= V_1 + \frac{j\omega L}{R} V_1 \\ V_o &= V_1 + \frac{V_1}{j\omega C R} \end{aligned}$$

$$H(j\omega) = \frac{V_o}{V_i} = \frac{V_1 + \frac{V_1}{j\omega C R}}{V_1 + \frac{j\omega L}{R} V_1} = \frac{1 + \frac{1}{j\omega C R}}{1 + \frac{j\omega L}{R}}$$

$$= \frac{j\omega C R + 1}{j\omega C R + (j\omega)^2 C L} = \frac{(1 + \frac{j\omega}{C R})}{R C \times (j\omega) \times (1 + \frac{j\omega}{\frac{R}{L}})}$$

$$H_{dB}(\omega) = 20 \log_{10} \frac{1}{R C} - 20 \log_{10} |j\omega| - 20 \log_{10} \left| 1 + \frac{j\omega}{\frac{R}{L}} \right| - 10 \log_{10} \left| 1 + \frac{j\omega}{C R} \right|$$
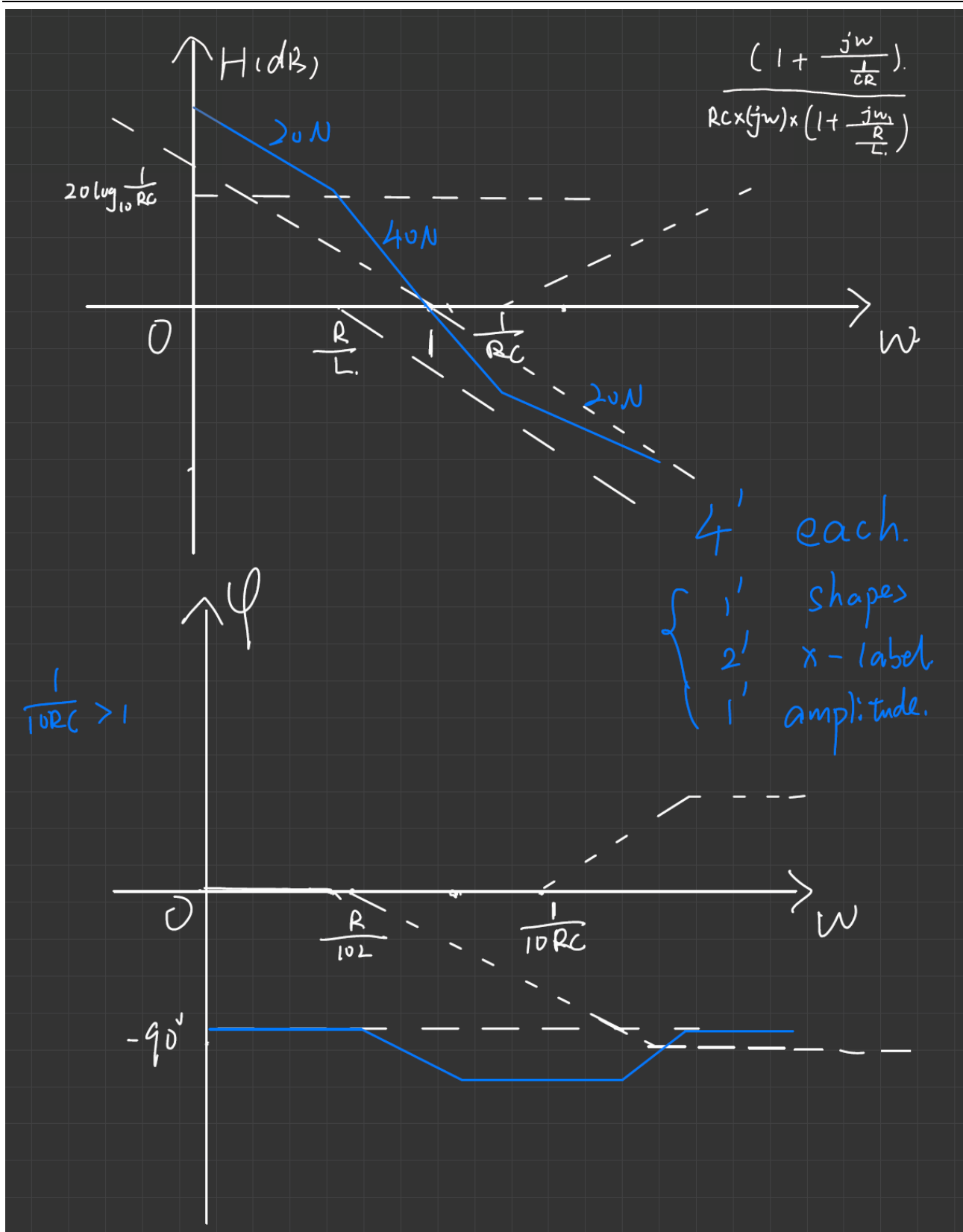
$$\phi(\omega) = \arctan C R - 90^\circ - \arctan \frac{L}{R}$$



Mathematics Formula Sheet:

• Phasor and Complex number

$$j^2 = -1$$

$$\frac{a + jb}{c + jd} = \frac{(a + jb)(c - jd)}{(c + jd)(c - jd)} = \frac{(ac + bd) + j(bc - ad)}{c^2 + d^2}$$

$$A + jB = \sqrt{A^2 + B^2} \angle \left[\arctan \frac{B}{A} \right] = \sqrt{A^2 + B^2} e^{j \arctan \frac{B}{A}}$$

$$\frac{A \angle \theta_1}{B \angle \theta_2} = \frac{A}{B} \angle (\theta_1 - \theta_2), \quad A \angle \theta_1 \times B \angle \theta_2 = AB \angle (\theta_1 + \theta_2)$$

$$e^{j\theta} = \cos\theta + j\sin\theta$$

Introduction to CASIO fx-991 calculator:

Complex number calculation: You may press “**menu**” button and select the “complex number” to do the complex number calculation.

For the unit imaginary “j”, the button “**ENG**” stands for that.

For the phasor angle “ \angle ”, please press “**SHIFT**”, and then press “**ENG**” button.

Mention: It's invalid to input $\angle\theta$, like $\angle 60$! You must input a number before that, such as “ $1\angle 60$ ” or “ $2\angle 60$ ”

Complex number and Phasor Transformation: Please press “**SHIFT**” and then press “**menu**”, you can select the “Complex” and then choose its form (“ $a+bi$ ” or “ $r\angle\theta$ ”)

Angle unit: Please press “**SHIFT**” and then press “**menu**”, you can select the “angle unit” and then choose the unit of angle (“degrees” or “rad”)