

ECE2150J 2024 FA Assignment 6


Due Date: 23:59 December 20th

In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated.

Exercise 6.1 (25%)

$V_s = 10\cos(4t + \pi/4)$, $R_1 = R_2 = 5\Omega$, $R_3 = 10\Omega$, $X_{L1} = 15\Omega$, $X_{L2} = 20\Omega$, $X_M = 2\Omega$, $X_C = 0.5\Omega$.


Find I_1 and I_2 .

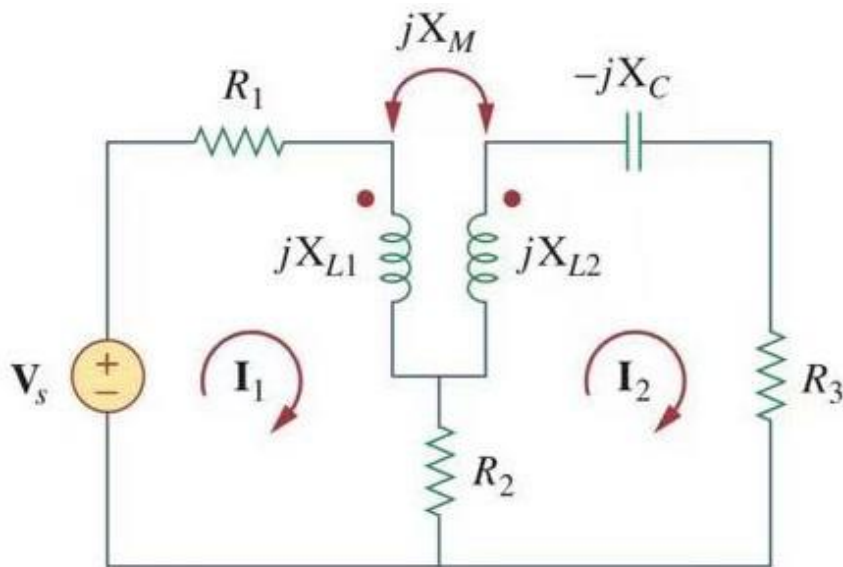

ECE2150J 2024 FA Assignment 6

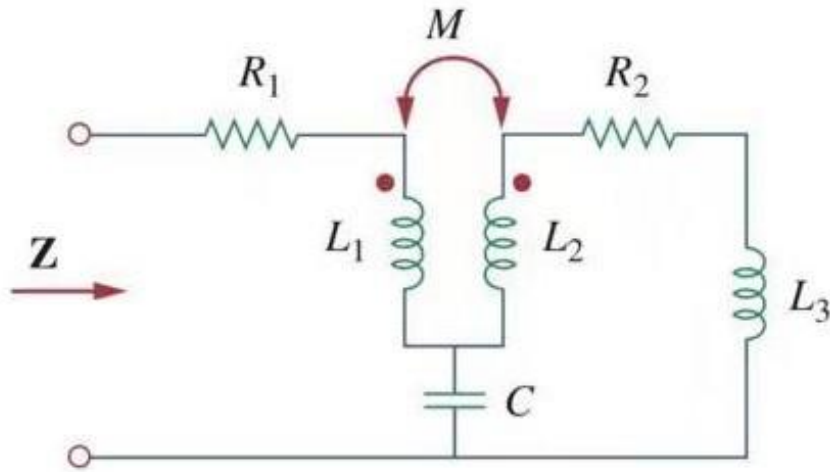Exercise 6.2 (25%)


$R_1 = R_2 = 5\text{ k}\Omega$, $M = 20\text{ H}$, $L_1 = 10\text{ H}$, $L_2 = 5\text{ H}$, $L_3 = 10\text{ H}$, $C = 0.1\text{ F}$. Suppose frequency of source is $\omega = 10\text{ kHz}$. Find the equivalent impedance Z . All currents flow clockwise.



ECE2150J 2024 FA Assignment 6

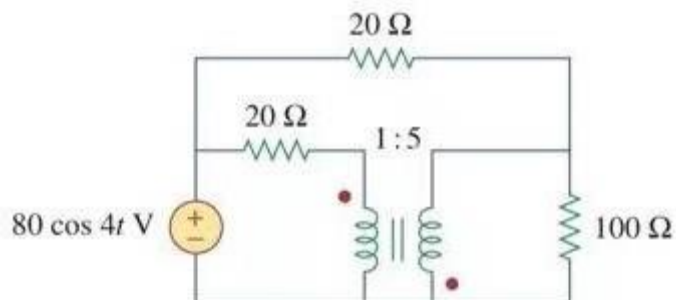Exercise 6.3 (25%)

Determine the average power absorbed by each resistor in this circuit. All currents flow clockwise.



ECE2150J 2024 FA Assignment 6

Exercise 6.4 (25%)

Determine I_1, I_2, I_3 in this circuit.

